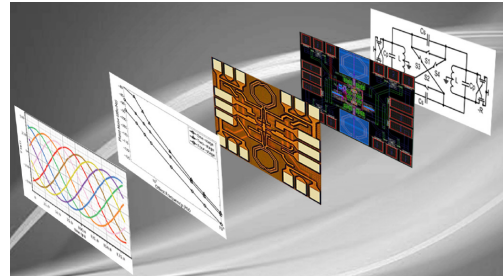


A text book on

Analog Circuits



Useful for IAS, IES, GATE, PSUs and other competitive examinations

A. RAJKUMAR

M. Tech. (JNTU Kakinada)

(Ph.D) JNTU Hyderabad

Expert Faculty, MADE EASY



Corporate Office: 44-A/4, Kalu Sarai, New Delhi-16

Website: www.madeeasypublications.org | **Phone:** 011-45124660, 08860378007



MADE EASY Publications

Corporate Office: 44-A/4, Kalu Sarai, New Delhi-110016

Website: www.madeeasypublications.org | Phone: 9021300500

E-mail: infomep@madeeasy.in

A text book on Analog Circuits

© Copyright, by MADE EASY Publications.

All rights are reserved. No part of this publication may be reproduced, stored in or introduced into a retrieval system, or transmitted in any form or by any means (electronic, mechanical, photocopying, recording or otherwise), without the prior written permission of the above mentioned publisher of this book.

First Edition: 2012

Reprint: 2013

Reprint: 2014

Reprint: 2015

Reprint: 2016

Reprint: 2019

Reprint: 2022

Dedicated to

My Wife

A. Smitha

who believes, in



*The best teacher teaches from the heart,
....not from the book....*



PREFACE

I have great pleasure in writing the book of core subject of Electronics Engineering viz. **Analog Circuits**. A thorough understanding of the concepts developed in this book will prepare the reader for more advanced course on the subject. The entire syllabus of Analog circuits is presented in a simple and lucid style to make it comprehensible to an average student. This text book has been written to meet the requirements for the students of B.E./B.Tech., ECE, EEE, EIE.

In this book, I have tried to present the approach for competitive examinations like GATE, IES and IAS. While teaching various categories of students, I understood that, it becomes very easy for the students when things are explained by going through the fundamentals. So in the present book, I tried to explain most of the topics through the basics. The **Questions with Solutions** which already appeared in competitive examinations like GATE, IES are incorporated in each chapter.

First, I would like to thank **Mr. B. Singh** (Chief Managing Director, MADE EASY Group) for giving me the opportunity for writing the text book. His constructive suggestions and support helped me a lot.

I express my heartfelt regard and gratitude to my teacher Dr. Srinivas Rao from whom I have learnt the subject matter and which gave me inspiration to write this book.

I would also like to thank my H.O.D. Dr. Koteswara Rao and Principal Dr. Chinna Keshava Rao (CBIT), Mr. Sudarshan Reddy (Associate Prof. in CBIT) who always inspire me in discipline and hard work.

A special thanks to Mr. Sai Prasad who always, encourages me and gave me the first opportunity to teach for competitive exams.

I express my sincere gratitude to my favorite Sir, Mr. Prem R. Chadha, friends M.V. Kiran Kumar, Ramana Reddy, Krishna Kumar, Jagan, Krishna who always direct me in a right path.

Last but not the least, I also thank MADE EASY staff especially Vinod Kumar and Md. Asim who put their sincere efforts to develop this book in time.

Any comments and suggestions for the improvement of this book will be thankfully acknowledged and incorporated in the next edition.

A. Rajkumar

CONTENTS

1

BJT Biasing and Thermal Stabilization

- 1.1 Operating Point and DC Load Line 2
- 1.2 Temperature Dependence on Transistor Parameters 5
- 1.3 Stability Factor 6
- 1.4 Biasing Techniques 7
- 1.5 Fixed Bias Circuit 7
- 1.6 Collector to Base Bias 8
- 1.7 Voltage Divider Bias or Self Bias 10
- 1.8 Bias Compensation by Diode 12
- 1.9 Bias Compensation by Thermistor 12
- 1.10 Bias Compensation by Sensistor 12
- 1.11 Thermal Run away 13

2

Small Signal Analysis of BJT

Low Frequency Analysis

- 2.1 Introduction 32
- 2.2 Two Port Network 32
- 2.3 Hybrid Model of BJT 34
- 2.4 Hybrid Model in Different Configurations 34
- 2.5 Typical Values of H-Parameters 35
- 2.6 Conversion Formulas of H Parameters in Different Configuration 35
- 2.7 Transistor Amplifier Analysis Using Exact Model 35
- 2.8 Transistor Amplifier Analysis Using Approximate Model 38

High Frequency Analysis

- 2.9 Introduction 41
- 2.10 Hybrid- π Model 41
- 2.11 Typical Values of Hybrid- π Parameters 42
- 2.12 Expressions for Hybrid- π Parameters 43
- 2.13 Variation of Hybrid π Parameters With I_c , V_{CE} and Temperature 48
- 2.14 Common Emitter Short Circuit Current Gain 48
- 2.15 High Frequency Current Gain with Resistive Load 50

Frequency Response of an Amplifier

- 2.16 Low Frequency Range 52
- 2.17 High Frequency Range 52
- 2.18 Midband Range 52
- 2.19 Application of Bodeplot in Frequency Response of Amplifier 53

3

Feedback Amplifiers

- 3.1 Introduction **66**
- 3.2 Limitations of Basic Amplifier **66**
- 3.3 Feedback Principle **66**
- 3.4 Classification of Amplifiers **67**
- 3.5 General Theory of Feedback **69**
- 3.6 Concept of Positive Feedback and Negative Feedback **71**
- 3.7 Advantages of Negative Feedback Amplifiers **72**
- 3.8 Topologies of Feedback **76**
- 3.9 Voltage Series Feedback **79**
- 3.10 Voltage Shunt Feedback **79**
- 3.11 Current Series Feedback **81**
- 3.12 Current Shunt Feedback **82**
- 3.13 Method of Analysis of a Feedback Amplifier **83**

4

Oscillators

- 4.1 Introduction **96**
- 4.2 Types of Oscillators **96**
- 4.3 Essentials of Transistor Oscillator **97**
- 4.4 Barkhausen Criterion **98**
- 4.5 RC Phase Shift Oscillator **99**
- 4.6 Wien Bridge Oscillator **103**
- 4.7 Comparison of RC Oscillators **105**
- 4.8 LC Oscillators **106**
- 4.9 Hartley Oscillator **107**
- 4.10 Colpitts Oscillator **109**
- 4.11 Clapp Oscillator **111**
- 4.12 Crystal Oscillator **112**

5

Power Amplifiers

- 5.1 Introduction **124**
- 5.2 Difference Between Voltage Amplifier and Power Amplifier **124**
- 5.3 Power Amplifiers **126**
- 5.4 Power Amplifier Classes **126**
- 5.5 Comparison of Amplifier Classes **128**
- 5.6 Class-A Power Amplifier **128**
- 5.7 Distortion in Amplifiers **133**
- 5.8 Class-B Power Amplifier **134**
- 5.9 Class-B Push Pull Amplifier **136**
- 5.10 Complementary Symmetry Class-B Amplifier **140**

- 5.11 Comparison Between Push Pull and Complementary Symmetry **140**
- 5.12 Cross Over Distortion **141**
- 5.13 Class-AB Amplifier **141**
- 5.14 Safe Operating Area (SOA) For a Transistor **142**
- 5.15 Thermal Analogy of Power Transistors **143**
- 5.16 Class-C Power Amplifier **144**
- 5.17 Class-D Amplifiers **145**
- 5.18 Class-S Power Amplifier **146**

6

Multistage Amplifiers

- 6.1 Introduction **154**
- 6.2 Characteristics of Cascaded Amplifier **154**
- 6.3 Gain in Decibels **155**
- 6.4 Selection of an Amplifier Configuration For Cascade Connection **156**
- 6.5 Methods of Coupling in Multistage Amplifiers **156**
- 6.6 RC Coupled Amplifiers **157**
- 6.7 Transformer Coupled Amplifier **158**
- 6.8 Direct Coupled Amplifiers **160**
- 6.9 Comparison of Different Coupling Techniques **161**
- 6.10 Rise Time-bandwidth Relation **161**
- 6.11 Cascode Amplifier (CE-CB) **163**
- 6.12 Darlington Pair (CC-CC) **163**
- 6.13 Bootstrap Emitter Follower **164**
- 6.14 Millers Theorem **165**
- 6.15 Effect of Cascading on Bandwidth (identical stages) **166**
- 6.16 Effect of Cascading on Bandwidth (non identical stages) **168**

7

Linear and Non Linear Wave Shaping

Linear Wave Shaping

- 7.1 Introduction **176**
- 7.2 High Pass RC Circuit **176**
- 7.3 RC Differentiator **177**
- 7.4 Sinusoidal Input **178**
- 7.5 Response of Step, Pulse, Square, Ramp, Exp. for High Pass ckt **179**
- 7.6 Low Pass RC Circuit **180**
- 7.7 Low Pass RC Circuit as Integrator **181**
- 7.8 Sinusoidal Input **181**
- 7.9 Response of Step, Pulse, Square, Ramp and Exp. for Low Pass ckt **183**

Non Linear Wave Shaping

- 7.10 Clippers **184**
- 7.11 Shunt Clipper Models **184**
- 7.12 Series Clipper Models **189**
- 7.13 Clipping at Two Independent Levels **195**
- 7.14 Clamping Circuits **199**

8

Rectifiers, Filters and Voltage Regulators

Rectifiers

- 8.1 Introduction 216
- 8.2 Rectifier Parameters 216
- 8.3 Half Wave Rectifier 217
- 8.4 Full Wave Rectifier 222
- 8.5 Bridge Rectifier 226

Filters

- 8.6 Introduction 227
- 8.7 Capacitor Filter 228
- 8.8 Inductor Filter 231
- 8.9 L Section Filter 234
- 8.10 π Section Filter 235
- 8.11 Bleeder Resistor 236

Voltage Regulators

- 8.12 Introduction 236
- 8.13 Block Diagram of Power Supply 236
- 8.14 Load Regulation 237
- 8.15 Line Regulation 237
- 8.16 Series Voltage Regulator 237
- 8.17 Shunt Voltage Regulator 238
- 8.18 Limitations of Series and Shunt Voltage Regulators 238

9

Operational Amplifiers

Differential Amplifiers

- 9.1 Introduction 248
- 9.2 Differential Amplifier 248
- 9.3 Circuit Configurations 249
- 9.4 Circuit Diagrams 250
- 9.5 Operating Point (Q) for a Differential Amplifier 252
- 9.6 Practical Design Problems in Differential Amplifiers 253
- 9.7 Swamping Resistor Technique 254
- 9.8 Constant Current Source Circuits 255
- 9.9 Current Mirror Circuits 257
- 9.10 Common-Mode Voltage Gain 260
- 9.11 Differential Amplifier With Active Load 262

Operational Amplifiers

- 9.12 Block Diagram of Operational Amplifier 263
- 9.13 Symbol Representation of Op-Amp 263

- 9.14 Equivalent Circuit of an Op-Amp **264**
- 9.15 Ideal Voltage Transfer Characteristics **264**
- 9.16 Pin Diagram of 741 IC **265**
- 9.17 Op-amp Characteristics **265**
- 9.18 Importance of Negative Feedback in Op-Amp **270**
- 9.19 Virtual Ground **271**

Applications of Operational Amplifier

- 9.20 Inverting Amplifier **271**
- 9.21 Non-Inverting Amplifier **272**
- 9.22 Phase Shifter **273**
- 9.23 Voltage Follower **273**
- 9.24 Differential Amplifier **274**
- 9.25 Subtractor **275**
- 9.26 Inverting Adder **275**
- 9.27 Non Inverting Adder **276**
- 9.28 Current to Voltage Converter **277**
- 9.29 Voltage to Current Converter **278**
- 9.30 Voltage to Current Converter (with load) **278**
- 9.31 Op-Amp Integrator **279**
- 9.32 Op-Amp Differentiator **280**
- 9.33 Precision Rectifiers **281**
- 9.34 Current Amplifiers **285**
- 9.35 Instrumentation Amplifier **286**
- 9.36 Voltage Limiters **287**
- 9.37 Log Amplifiers **289**
- 9.38 Anti Log Amplifiers **289**
- 9.39 Analog Multiplier **290**
- 9.40 Analog Divider **291**
- 9.41 Peak Detector **292**
- 9.42 Sample and Hold Circuit **292**
- 9.43 Op-amp Comparator **293**
- 9.44 Schmitt Trigger **295**
- 9.45 Astable Multivibrator (free-running oscillator) **297**
- 9.46 Triangular-Wave Generator **298**
- 9.47 Monostable Multivibrator (pulse generator) **299**

Active Filters

- 9.48 Introduction **301**
- 9.49 Classification of Active Filters **301**
- 9.50 Butterworth Filter **303**
- 9.51 First Order Low Pass Butterworth Filter **304**
- 9.52 First Order High Pass Butterworth Filter **306**
- 9.53 Band Pass Filters **309**

9.54 Band Stop Filter **313**

9.55 All Pass Filter **315**

555 Timer

9.56 Introduction **318**

9.57 555 Timer Pin Configuration **318**

9.58 Block Diagram of 555 Timer **319**

9.59 555 Timer as Monostable Multivibrator **320**

9.60 555 Timer as Astable Multivibrator **323**

10

FET Biasing and Small Signal Analysis

FET Biasing

10.1 Introduction **370**

10.2 DC-Load Line and Bias Point **370**

10.3 Fixed Bias Circuit **372**

10.4 Self Bias **373**

10.5 Voltage Divider Bias **374**

Small Signal Analysis

10.6 Introduction **376**

10.7 Common Source Bypass JFET Amplifier **377**

10.8 Common Source Unbypass JFET Amplifier **379**

10.9 Common Drain JFET Amplifier **381**

10.10 Common Gate JFET Amplifier **382**

10.11 Comp. Between CS Bypass, CS Unbypass, CD, CG Amplifiers **385**

11

Multivibrators and Time Base Generators

Multivibrators

11.1 Introduction **394**

11.2 Bistable Multivibrator **395**

11.3 Schmitt Trigger **397**

11.4 Mono Stable Multivibrator **399**

11.5 Astable Multivibrator **401**

Time Base Generators

11.6 Introduction **404**

11.7 Sweep Voltage **404**

11.8 Methods of Generating a Time Base Waveform **405**

11.9 Exponential Sweep Circuit **406**

11.10 UJT Sweep Generator **406**

11.11 Bootstrap Sweep Generator **408**

11.12 Miller Sweep Circuit **410**



CHAPTER 1

BJT BIASING & THERMAL STABILIZATION

About This Chapter

- Operating point and DC load line.
- AC load line.
- Stability factors S , S' and S'' .
- Various biasing circuits like fixed bias, collector to base bias and self bias.
- Compensation circuits.
- Thermal run-away and conditions to maintain thermal stability.

1

BJT Biasing & Thermal Stabilization

1.1 Operating Point and DC Load Line

- It is clear that the transistor functions most linearly when it is constrained to operate in its active region.
- To establish an operating point in this region it is necessary to provide appropriate direct potentials and currents, using external sources.
- Once an operating point Q is established as shown below:

ANALYSIS

Assume common emitter amplifier circuit

In DC analysis,

(i) ac should be grounded

(ii) $X_c \propto \frac{1}{f}$, as $f \rightarrow 0$, $X_c \rightarrow \infty$

\therefore Capacitor is open.

DC Equivalent Model

The output loop equation is given by

$$V_{CC} = I_C (R_C + R_e) + V_{CE}$$

$$I_C = \frac{V_{CC}}{R_C + R_e} - \frac{V_{CE}}{R_C + R_e}$$

Above equation represents like a straight line $y = mx + C$

When

$$I_C = 0, (V_{CE})_{\max} = V_{CC}$$

$$V_{CE} = 0, (I_C)_{\max} = \frac{V_{CC}}{R_C + R_e}$$

$$\text{Slope of DC load line} = - \frac{1}{R_C + R_e}$$


 


Figure 1.1 Common emitter amplifier

 

Output Characteristics of Common Emitter

 


Fig. 1.2 DC load line and Q point

Q Point

“The intersection point between the dc load line and sample graph of I_C is called as operating point (or) Quiescent point”.

DC Load Line

“The locus of all the Q points are concentrated on a line called as DC load line”.

- When time varying excursions of the input signal (base current, for example) is applied to common emitter amplifier, should cause an output signal (collector voltage or collector current) of the same wave form.
- If the output signal is not a faithful reproduction of the input signal, for example, if it is clipped on one side. The operating point is unsatisfactory and should be relocated on the collector characteristics.
- The question now naturally arises as, how to choose the operating point.
- Note that even if we are free to choose R_C , R_L , R_b and V_{CC} , we may not operate the transistor every where in the active region, because the various transistor ratings limit the range of useful operation.
- These ratings are

$$(i) (V_{CE})_{\max} \quad (ii) (I_C)_{\max} \quad (iii) P_{C \max}$$

Capacitive Coupling

- The capacitor C_{b1} is to couple the input signal to the transistor, as indicated in the Figure (1.3).
- In this diagram, one end of V_i is at ground potential, and the collector supply V_{CC} also provides the biasing base current I_B .
- Under quiescent conditions (no input signal), C_{b1} (called a blocking capacitor) acts as an open circuit because the reactance of a capacitor is infinite at zero frequency (dc).

 


Figure 1.3 Fixed bias circuit

- The capacitances C_{b1} and C_{b2} are chosen large enough so that, at the lowest frequency of excitation their reactances are small enough so that they can be considered to be short circuits.
- These coupling capacitors block dc voltages but freely pass signal voltages.
For example, the quiescent collector voltage does not appear at the output, but V_o is an amplified replica of the input signal V_i .
- The ac output signal voltage may be applied to the input of another amplifier without affecting its bias, because of the blocking capacitor C_{b2} .

DC and AC Load Lines

- We noted that under dc conditions C_{b2} acts as an open circuit. Hence the quiescent collector current and voltage are obtained by drawing a static (dc) load line.
- If $R_L = \infty$ and if the input signal (base current) is large and symmetrical, we must locate the operating point Q_1 at the centre of the DC load line. In this way the collector voltage and current may vary approximately symmetrically around the quiescent values V_C and I_C respectively.
- If $R_L \neq \infty$, however, a dynamic (ac) load line must be drawn.
- Since, we have assumed that, at the signal frequency, C_{b2} acts as a short circuit, the effective load R'_L at the collector is R_C in parallel with R_L .

 


Figure 1.4 DC and AC load line


AC Load Line Analysis



Assume CE amplifier circuit:

AC Analysis

- DC should be grounded.
- $X_C \propto \frac{1}{f}$, as $f \rightarrow \infty \therefore X_C \rightarrow 0$

i.e. capacitor acts as short circuit.

 

  AC Equivalent Model**AC Load Line**

$$\text{Slope of ac load line is } -\frac{1}{R'_L} = -\frac{1}{R_C \parallel R_L}$$

- We observe that the input signal may swing a maximum of approximately 20 μA around Q_1 because, if the base current decreases by more than 20 μA , the transistor is driven off.
- If a larger input swing is available, then in order to avoid cut-off during a part of the cycle. The quiescent point must be located at a higher current.
- Suppose we locate Q_2 on the dc load line such that a line with a slope corresponding to the ac resistance R'_L and drawn through Q_2 gives as large as output as possible with out too much distortion.
- The choice of Q_2 allows an input peak current swing of about 30 μA .

1.2 Temperature Dependence on Transistor Parameters

The sources of instability of I_C are essentially three:

- Reverse saturation current I_{CO}
- Base-emitter voltage V_{BE}
- Current gain β

- **I_{CO} Versus Temperature**

" I_{CO} increases by 7%/°C rise in temperature".

(or)

" I_{CO} doubles for every 10°C rise in temperature".

i.e. as temperature increases, I_{CO} also increases.

- **V_{BE} Versus Temperature**

"The base to emitter voltage V_{BE} , which decreases at the rate of 2.5 mV/°C for both Ge and Si transistors."

$$\frac{dV_{BE}}{dT} = -2.5 \text{ mV/}^\circ\text{C}$$

i.e. as temperature increases, V_{BE} decreases.

- **β Versus Temperature**

(a) β increases with temperature

 


Figure 1.5 DC load line and Q point

(b) Replacement of Transistor

- We see that the spacing of the output characteristics will increase or decrease as β increases or decreases.
- Though transistors are identified by a type number, but even for a given type, the characteristics differ from piece to piece.
- β is the ratio of collector current I_C and base current I_b . As for the same base current, the collector current of the transistor will vary from replacement of the device.
- Generally β is greater for the replacement of transistor.

 


Figure 1.6 Common emitter characteristics

1.3 Stability Factor

"It is a measure of variation in the operating point with respect to the temperature is called as stability factor".

I_C is a function of I_{CO} , V_{BE} and β . It is convenient to introduce the three partial derivatives of I_C with respect to these variables. These derivatives are called the stability factors S , S' and S'' .

$$S = \left. \frac{\partial I_C}{\partial I_{CO}} \right|_{V_{BE}, \beta \text{ constant}}$$

$$S' = \left. \frac{\partial I_C}{\partial V_{BE}} \right|_{I_{CO}, \beta \text{ constant}}$$

$$S'' = \left. \frac{\partial I_C}{\partial \beta} \right|_{I_{CO}, V_{BE} \text{ constant}}$$

Expression for Stability Factor

$$I_C = \beta I_b + (1 + \beta) I_{CO} \quad \text{d.w.r.t } I_C$$

$$I = \beta \frac{\partial I_b}{\partial I_C} + (1 + \beta) \frac{\partial I_{CO}}{\partial I_C}$$

$$S = \frac{\partial I_C}{\partial I_{CO}} = \frac{1 + \beta}{1 - \beta \frac{\partial I_b}{\partial I_C}}$$

Conclusion:

- Ideally the stability factor should be zero.
- Practically stability factor should be very very less.

$$P_C = V_{CC}I_C - I_C^2(R_C + R_E)$$

Taking derivative w.r.t. I_C

$$\frac{\partial P_C}{\partial I_C} = V_{CC} - 2I_C(R_C + R_E)$$

Stability factor S ,

$$S = \frac{\partial I_C}{\partial I_{CO}} = \frac{\partial I_C}{\partial T_j} \times \frac{\partial T_j}{\partial I_{CO}}$$

We know that I_{CO} increases at the rate of 7% per°C

$$\frac{\partial I_{CO}}{\partial T_j} = 0.07 I_{CO}$$

$$\text{or } \frac{\partial T_j}{\partial I_{CO}} = \frac{1}{0.07 I_{CO}}$$

$$\frac{\partial I_C}{\partial T_j} = S \times 0.07 I_{CO}$$

$$\{V_{CC} - 2I_C(R_C + R_E)\} \times S \times 0.07 I_{CO} < \frac{1}{\theta}$$

Conclusion

The following three conditions leads to thermal run-away:

$$(i) \quad \frac{\partial P_C}{\partial T_j} < \frac{\partial P_D}{\partial T_j}$$

$$(ii) \quad \frac{\partial P_C}{\partial T_j} < \frac{1}{\theta}$$

$$(iii) \quad \{V_{CC} - 2I_C(R_C + R_E)\} \times S \times 0.07 I_{CO} < \frac{1}{\theta}$$

SUMMARY

- ✖ The collector current of a transistor varies with I_{CO} , β and V_{BE} which in turn are dependent on temperature variation.
- ✖ Stability factor S is given by

$$S = \frac{\partial I_C}{\partial I_{CO}} = \frac{1 + \beta}{1 - \beta \frac{\partial I_B}{\partial I_C}}$$

- ✖ Fixed bias circuit is the simplest biasing arrangement and has a stability factor $S = 1 + \beta$.
- ✖ Collector to base bias circuit is an improvement over fixed bias circuit and has a stability factor

$$S = \frac{1 + \beta}{1 + \beta \frac{R_C}{R_B + R_C}}$$

- ✖ The self bias circuit consists of three resistors R_1 , R_2 , R_e , usually. The R_e is bypassed with a large value capacitor C_E . The stability factor,

$$S = \frac{1 + \beta}{1 + \beta \frac{R_e}{R_b + R_e}}$$

for obtaining low value of S , it is necessary to choose a low value of $\frac{R_b}{R_e}$.

- ✖ Bias compensation can be achieved either by use of diode, thermistor or sensistor.

- ✖ Stability factor $S' = \frac{\partial I_C}{\partial V_{BE}}$ and stability factor $S'' = \frac{\partial I_C}{\partial \beta}$ can both be reduced if stability factor S is

reduced.

- ✖ Condition for thermal stability or avoiding thermal runaway are

$$\Rightarrow \frac{\partial P_C}{\partial T_j} < \frac{\partial P_D}{\partial T_j} \quad (\text{or}) \quad \frac{\partial P_C}{\partial T_j} < \frac{1}{\theta} \quad (\text{or}) \quad [V_{CC} - 2I_C(R_C + R_e)] \times S \times 0.07 I_{CO} < \frac{1}{\theta}$$

where θ = thermal resistance.

- ✖ Best possible of choosing the operating point is $V_{CE} = \frac{V_{CC}}{2}$.

GATE AND IES QUESTIONS


- Q.1** Introducing a resistor in the emitter of a common emitter amplifier stabilizes the dc operating point against variations in

- | | |
|----------------------------------|----------------------|
| (a) only the temperature | (b) only the β |
| (c) Both temperature and β | (d) none |

Exp. (c)

R_e resistor works as a negative feedback which gives stability of the circuit. Therefore it stabilizes against the variation of both temperature and β .

 - Q.2** In the circuit of the figure, assume that the transistor is in the active region. It has a large β and its base-emitter voltage is 0.7 V. The value of I_C is



- | | |
|--|-----------|
| (a) Indeterminate since R_C is not given | (b) 1 mA |
| (c) 5 mA | (d) 10 mA |

Exp. (d)

The Thevenin equivalent is shown below:

$$V_T = \frac{R_2}{R_1 + R_2} V_{CC}$$


$$= \frac{5}{10 + 5} \times 15 = 5 \text{ V}$$

Since β is large

$$I_C \approx I_E, I_B \approx 0 \text{ and}$$

$$I_E = \frac{V_T - V_{BE}}{R_E}$$
 
$$= \frac{5 - 0.7}{0.430 \text{ k}\Omega} = \frac{4.3}{0.430 \text{ k}\Omega} = 10 \text{ mA}$$




Q.3 In the amplifier circuit shown in the figure, the values of R_1 and R_2 are such that the transistor is operating at $V_{CE} = 3 \text{ V}$ and $I_C = 1.5 \text{ mA}$, when its β is 150. For a transistor with β of 200, the operating point (V_{CE} , I_C) is

(a) (2 V, 2 mA)

(b) (3 V, 2 mA)

(c) (4 V, 2 mA)

(d) (4 V, 1 mA)

 

Exp. (a)

The DC equivalent circuit is shown below:

First case:

$$V_{CC} - I_{C1} R_2 - V_{CE1} = 0$$

$$6 - 1.5 \text{ mA } R_2 - 3 = 0$$

$$R_2 = 2 \text{ k}\Omega$$


$$I_{B1} = \frac{I_{C1}}{\beta_1} = \frac{1.5 \text{ mA}}{150} = 0.01 \text{ mA}$$

Second case: I_{B2} will be equal to I_{B1} as there is no change in R_1

$$I_{C2} = \beta_2 I_{B2} = 200 \times 0.01 \text{ mA} = 2 \text{ mA}$$

$$V_{CE2} = V_{CC} - I_{C2} R_2 = 6 - 2 \text{ mA} \times 2 \text{ k}\Omega$$

$$= 2 \text{ V}$$

 

Exp. (d)

For the transistor to be in saturation

$$I_B > \frac{I_C}{\beta}$$

Q.31 If for a silicon n-p-n transistor, the base-to-emitter voltage (V_{BE}) is 0.7 V and the collector to base voltage (V_{CB}) is 0.2 V, then the transistor is operating in the

- | | |
|-------------------------|---------------------|
| (a) normal active mode | (b) saturation mode |
| (c) inverse active mode | (d) cutoff mode |

Exp. (a)

$$\begin{aligned} V_{CE} &= V_{BE} + V_{CB} \\ &= 0.7 + 0.2 \\ &= 0.9 \text{ V} \end{aligned}$$

$$(V_{CE})_{\text{sat}} = 0.2 \text{ V}$$

Therefore $V_{CE} > (V_{CE})_{\text{sat}}$

It is in normal active mode

REVIEW QUESTIONS

1. What is the purpose of biasing a transistor? Indicate the methods of biasing and compare them.
2. Define the three different stability factors and give an expression that determine the variation of collector current in terms of stability factor.
3. Explain the effect of temperature on various parameters of a transistor amplifier circuit and discuss the methods of stabilization of the operating point.
4. Draw a fixed bias circuit and explain its drawbacks in detail.
5. Derive expressions for stability factors of a self bias circuit.
6. Explain how stability is improved in a self bias circuit.
7. Give a transistor circuit that employs a thermistor to compensate the variation of parameters with temperature and explain the circuit operation.
8. What is a sensistor? Explain how it can be employed in a transistor circuit to compensate the variation of operating point with temperature.
9. Distinguish between stabilization and compensation techniques. Discuss about compensation techniques in detail.
10. What do you understand by thermal run away? Derive the condition for avoiding thermal run-away in a transistor. Explain the term thermal resistance and derive the condition for thermal stability of BJT.

