

24 *Years*

Previous Years Solved Papers

Civil Services Main Examination

(2001-2024)

Electrical Engineering Paper-I

Topicwise Presentation

Also useful for
Engineering Services Main Exam



**MADE EASY Publications Pvt. Ltd.**

Corporate Office: 44-A/4, Kalu Sarai (Near Hauz Khas Metro Station), New Delhi-110016

E-mail: infomep@madeeasy.in

Contact: 9021300500

Visit us at: www.madeeasypublications.org

Civil Services Main Examination Previous Solved Papers : Electrical Engineering Paper-I

© Copyright, by MADE EASY Publications Pvt. Ltd.

All rights are reserved. No part of this publication may be reproduced, stored in or introduced into a retrieval system, or transmitted in any form or by any means (electronic, mechanical, photo-copying, recording or otherwise), without the prior written permission of the above mentioned publisher of this book.

First Edition: 2017

Second Edition: 2018

Third Edition: 2019

Fourth Edition : 2021

Fifth Edition : 2022

Sixth Edition : 2023

Seventh Edition : 2024

Eighth Edition: 2025

Preface

Civil Service is considered as the most prestigious job in India and it has become a preferred destination by all engineers. In order to reach this estimable position every aspirant has to take arduous journey of Civil Services Examination (CSE). Focused approach and strong determination are the pre-requisites for this journey. Besides this, a good book also comes in the list of essential commodity of this odyssey.



I feel extremely glad to launch the revised edition of such a book which will not only make CSE plain sailing, but also with 100% clarity in concepts.

MADE EASY team has prepared this book with utmost care and thorough study of all previous years papers of CSE. The book aims to provide complete solution to all previous years questions with accuracy.

On doing a detailed analysis of previous years CSE question papers, it came to light that a good percentage of questions have been asked in Engineering Services, Indian Forest Services and State Services exams. Hence, this book is a one stop shop for all CSE, ESE and other competitive exam aspirants.

I would like to acknowledge efforts of entire MADE EASY team who worked day and night to solve previous years papers in a limited time frame and I hope this book will prove to be an essential tool to succeed in competitive exams and my desire to serve student fraternity by providing best study material and quality guidance will get accomplished.

With Best Wishes

B. Singh (Ex. IES)

CMD, MADE EASY Group

Previous Years Solved Papers of

Civil Services Main Examination

Electrical Engineering : Paper-I

C O N T E N T S

Sl.	TOPIC	PAGE No.
Unit-1	Circuit Theory	1-104
	1. Circuit Element, Nodal and Mesh Analysis	1
	2. Network Theorems	14
	3. Transient Response of DC & AC Networks, Sinusoidal Steady State Analysis.....	36
	4. Second Order RLC Circuit, Resonance	57
	5. Two Port Networks	67
	6. Magnetically Coupled Circuits	80
	7. Network Graph, Functions and Synthesis	89
	8. Three Phase Circuits + Filters	98
Unit-2	Signals and Systems	105-172
	1. Basics and LTI Systems	105
	2. Fourier Series and Fourier Transform	122
	3. Laplace Transform.....	133
	4. Z-transform	155
Unit-3	Electromagnetic Theory	173-239
	1. Static Fields and Maxwell's Equation	173
	2. Electromagnetic Wave	192
	3. Transmission Lines.....	219
	4. Microwaves and Antenna	236


Unit-4	Analog Electronics	240-348
1.	Diode Circuits	240
2.	BJT Circuits	251
3.	MOSFET Circuits	275
4.	Feedback Amplifiers and Oscillators.....	280
5.	Operational Amplifiers and Timers.....	289
6.	IC Fabrication.....	337
7.	Miscellaneous.....	347
Unit-5	Digital Electronics.....	349-402
1.	Number System and Logic Gates.....	349
2.	Combinational Circuit	362
3.	Sequential Circuit.....	377
4.	Logic Families	396
5.	A/D and D/A Converters.....	398
Unit-6	Energy Conversion	403-512
1.	Electro Mechanical Energy Conversion	403
2.	DC Machines.....	409
3.	Transformers.....	435
4.	Induction Machines	460
5.	Synchronous Machines.....	496
Unit-7	Power Electronics and Electric Drives	513-586
1.	Power Semiconductor Devices	513
2.	Controlled and Uncontrolled Rectifiers	524
3.	Choppers.....	544
4.	Inverters	567
5.	Electric Drives.....	577
Unit-8	Analog Communication	587-670
1.	Signals, Random Variable and Noise Basics.....	587
2.	Amplitude Modulation	609
3.	Angle Modulation.....	633
4.	Transmitter, Receiver and Noise Performance of AM System.....	660

1

Circuit Theory


1. Circuit Element, Nodal and Mesh Analysis

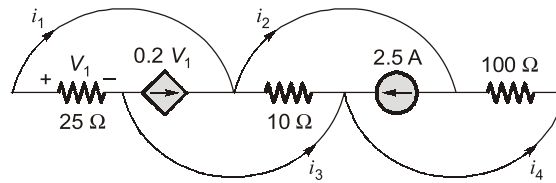1.1 For the circuit shown below, find i_1 , i_2 , i_3 and i_4 .



[CSE-2005 : 5 marks]

Solution:

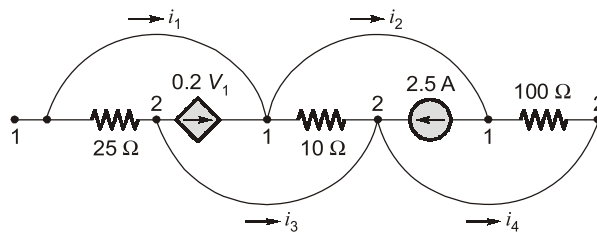

Circuit is redrawn as:

By Nodal equation,

$$-\frac{V_1}{100} - 2.5 - \frac{V_1}{10} + 0.2V_1 - \frac{V_1}{25} = 0$$

$$\Rightarrow V_1 = \frac{250}{5} = 50 \text{ V}$$


$$i_4 = -\frac{V_1}{100} = -0.5 \text{ A}$$

$$i_1 = -\frac{V_1}{25} = \frac{-50}{25} = -2 \text{ A}$$


$$i_2 = i_1 + 0.2 V_1 + i = -2 + 10 - 5 = 3 \text{ A}$$

$$i_3 = i - 2.5 + i_4 = -5 - 2.5 - 0.5 = -8 \text{ A}$$
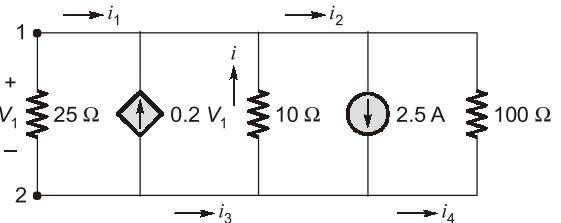
$$i_1 = -2 \text{ A} ; i_2 = 3 \text{ A} ; i_3 = -8 \text{ A} ; i_4 = -0.5 \text{ A}$$




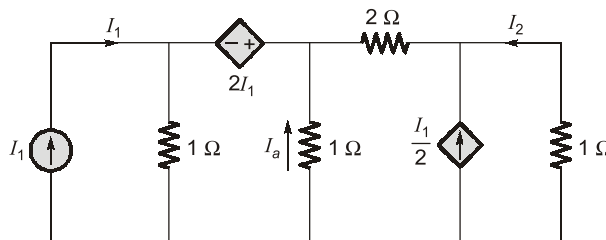1.2 For the network shown below, find the current ratio transfer function given by $\alpha = I_2/I_1$.



[CSE-2005 : 10 marks]

Solution:

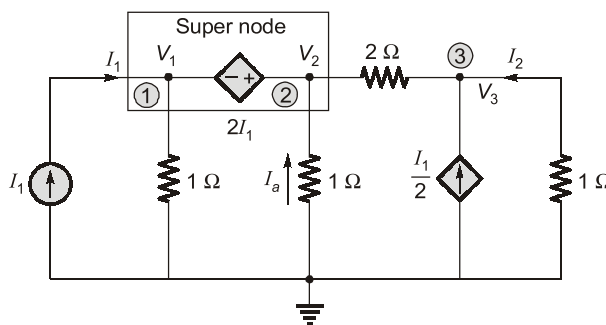

Consider nodes (1) and (2). These two nodes constitutes a super node.

$$V_2 - V_1 = 2I_1 \quad \dots(1)$$

Super node equation

$$\frac{V_1}{1} - I_1 + \frac{V_2}{1} + \frac{V_2 - V_3}{2} = 0 \quad \dots(2)$$

$$V_1 + V_2 + 0.5V_2 - 0.5V_3 = I_1$$

$$V_1 + 1.5V_2 - 0.5V_3 = I_1$$

Node (3):

$$\frac{V_3 - V_2}{2} - I_2 - \frac{I_1}{2} = 0 \quad \dots(3)$$

Put

$$\frac{V_3 - V_2}{2} = 0.5I_1 + I_2$$

$$V_1 - I_1 + V_2 - 0.5I_1 - I_2 = 0$$

$$V_1 + V_2 = 1.5I_1 + I_2 \quad \dots(4)$$

From (1) and (4)

$$V_2 = 1.75I_1 + 0.5I_2$$

Also

$$V_3 - V_2 = I_1 + 2I_2$$

$$V_3 = V_2 + I_1 + 2I_2$$

$$V_3 = 2.75I_1 + 2.5I_2$$

... (5)

Also

$$I_2 = -V_3$$

From (5),


$$-I_2 = 2.75I_1 + 2.5I_2$$

$$-3.5I_2 = 2.75I_1$$

$$\alpha = \frac{I_2}{I_1} = \frac{-2.75}{3.5} = -0.786$$

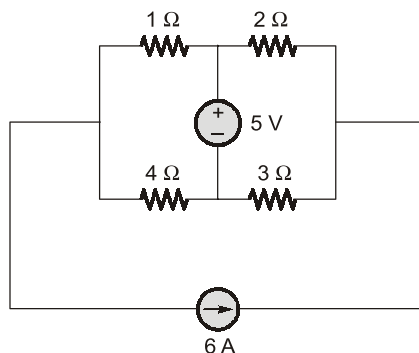1.3

Determine the power delivered by 6 A source.



[CSE-2007 : 10 marks]

Solution:

Consider node a and b

$$\text{Node } a: \quad \frac{V_a - 5}{1} + \frac{V_a}{4} + 6 = 0$$

$$V_a \left(1 + \frac{1}{4} \right) = -1$$

$$\Rightarrow \quad V_a = -0.8 \text{ V}$$



$$\text{Node } b: \quad \frac{V_b - 5}{2} + \frac{V_b}{3} - 6 = 0$$

$$V_b \left(\frac{1}{2} + \frac{1}{3} \right) = 8.5$$

$$\Rightarrow \quad V_b = 10.2 \text{ V}$$


$$\text{Power supplied} = (V_{ba}) (6) = (10.2 + 0.8) 6$$

$$P = 66 \text{ W}$$

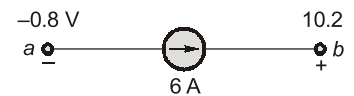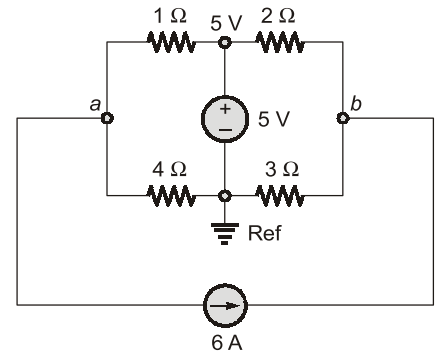

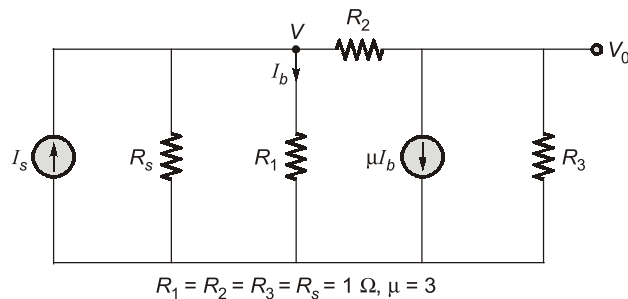1.4

For the circuit shown in the figure determine V_0/I_s using nodal analysis.



[CSE-2007 : 10 marks]

Solution:

$$V = I_b \quad \dots(1)$$

Node (1),

$$\frac{V}{1} + \frac{V}{1} + \frac{V - V_0}{1} - I_s = 0$$

$$3V - V_0 = I_s \quad \dots(2)$$

Node (2),

$$\frac{V_0}{1} + \frac{V_0 - V}{1} + 3I_b = 0$$

$$2V_0 - V = -3I_b \quad \dots(3)$$

From equation (1), $I_b = V$ put in equation (3)

$$2V_0 - V = -3V$$

$$2V_0 = -2V$$

\Rightarrow

$$V = -V_0$$


Putting,

$$V = -V_0 \text{ in equation (2)}$$


$$3(-V_0) - V_0 = I_s$$

$$-4V_0 = I_s$$
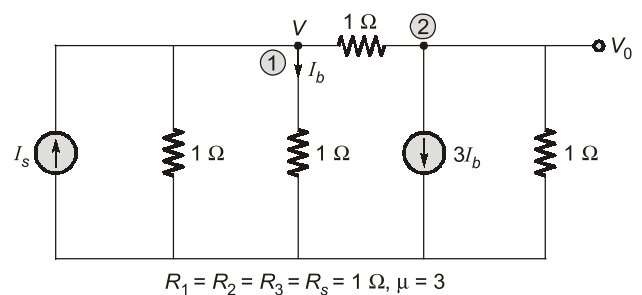
$$\frac{V_0}{I_s} = -\frac{1}{4} = -0.25$$



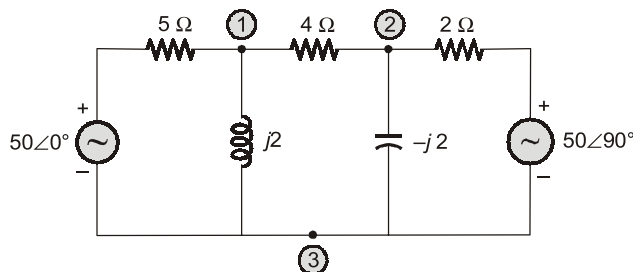1.5 Write the node equations for the network shown in figure. Assume node (2) as a reference node.



[CSE-2010 : 10 marks]

Solution:

Node 1:

$$\frac{V_1 - V_3 - 50}{5} + \frac{V_1 - V_3}{j2} + \frac{V_1}{4} = 0$$

$$V_1(0.2 + 0.25 - j0.5) - V_3(0.2 - j0.5) = 10 \quad \dots(1)$$

Node 3:


$$\frac{V_3 - V_1 + 50}{5} + \frac{V_3 - V_1}{j2} + \frac{V_3}{-j2} + \frac{V_3 + j50}{2} = 0$$

$$V_3 \left(\frac{1}{5} + \frac{1}{j2} - \frac{1}{j2} + \frac{1}{2} \right) - \frac{V_1}{5} - \frac{V_1}{j2} + 10 + j25 = 0$$

$$V_3(0.7) - V_1(-j0.5 + 0.2) = -10 - j25$$

$$V_1(0.2 - j0.5) - 0.7V_3 = 10 + j25 \quad \dots(2)$$

Nodal equation given by (1) and (2).

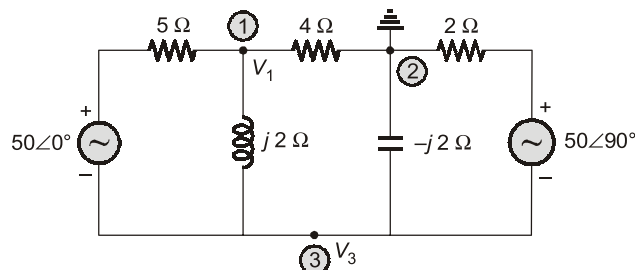

1.6 A storage battery has a no-load terminal voltage of 6 V. When the current through the battery is 100 A, the terminal voltage drops to 5 V. Show a pictorial representation of the battery as a constant current source.

[CSE-2011 : 15 marks]



Solution:

E = Open voltage of battery = 6 V
with a current of 100 A

$$V_t = E - (100) R_i$$


$$V_t = 5 \text{ V} = 6 - 100 R_i$$

$$R_i = 10 \text{ m}\Omega$$

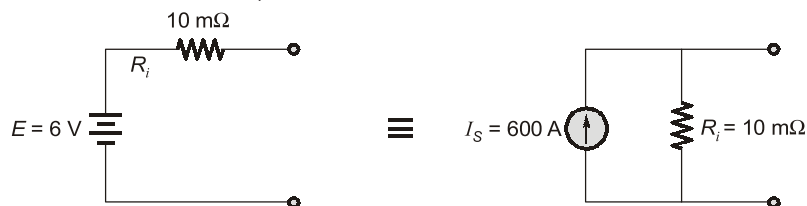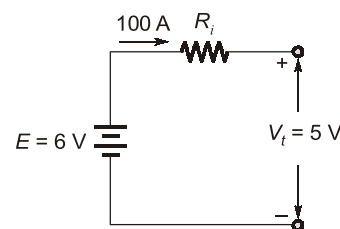


$$I_s = \frac{E}{R_i} = \frac{6}{10 \times 10^{-3}} = 600 \text{ A}$$

Constant current source,

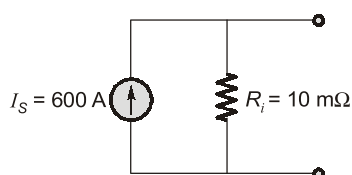

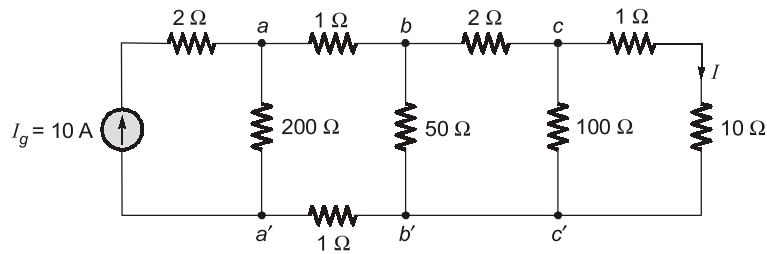
1.7 Determine the current- I in figure using the ladder reduction method.




[CSE-2013 : 20 marks]

Solution:


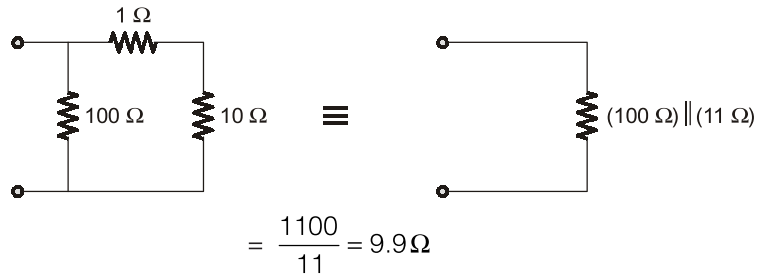
First we will determine equivalent resistance across cc'




Equivalent resistance across bb'

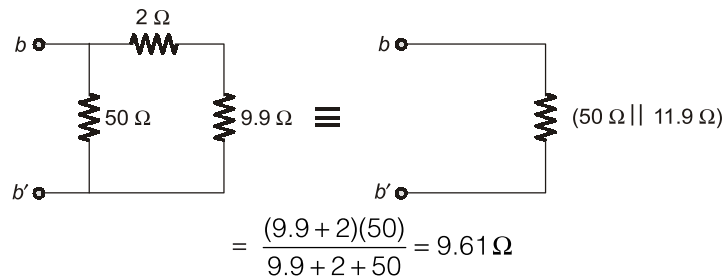


Equivalent resistance across aa'

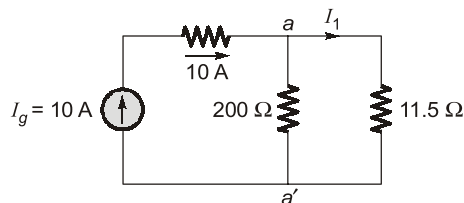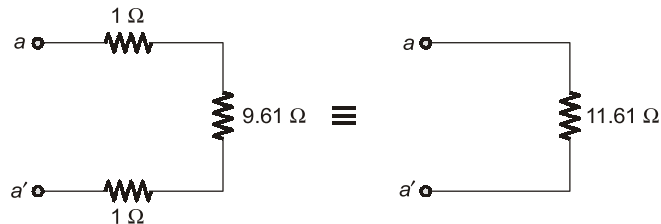
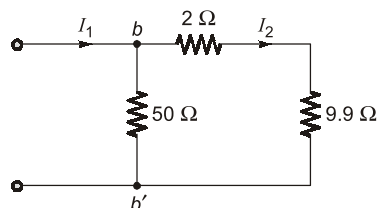
$$I_1 = \frac{(10)(200)}{200 + 11.5} = 9.46 \text{ A}$$



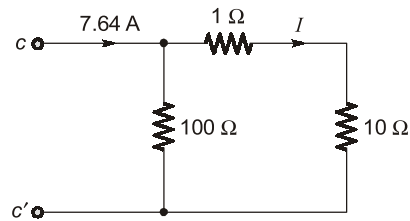
$$I_2 = \frac{(I_1)(50)}{50 + 2 + 9.9} = \frac{9.46 \times 50}{61.9} = 7.64 \text{ A}$$




$$I = \frac{(7.64)(100)}{100 + 10 + 1} = 6.88 \text{ A}$$

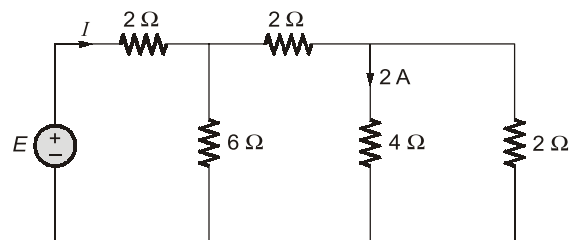1.8 Find the values of E and I in the circuit shown in figure.



[CSE-2014 : 10 marks]

Solution:

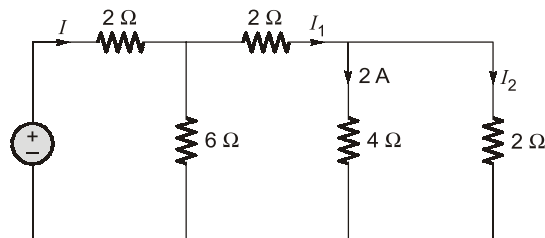


By the rule of division of current in parallel circuit

$$2 = \frac{(2)(I_1)}{2 + 4}$$

⇒

$$I_1 = 6 \text{ A}$$


$$I_2 = I_1 - 2 = 4 \text{ A}$$

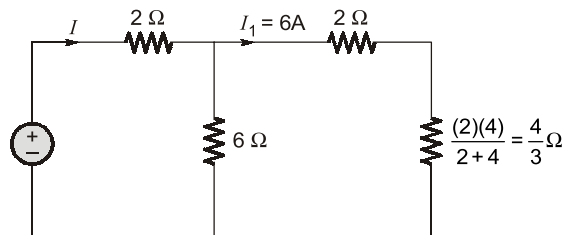


$$\frac{(2)(4)}{2 + 4} = \frac{4}{3} \Omega$$

$$I_1 = \frac{I(6)}{6 + \left(2 + \frac{4}{3}\right)} = \frac{I(18)}{18 + 6 + 4} = \frac{I(18)}{28}$$
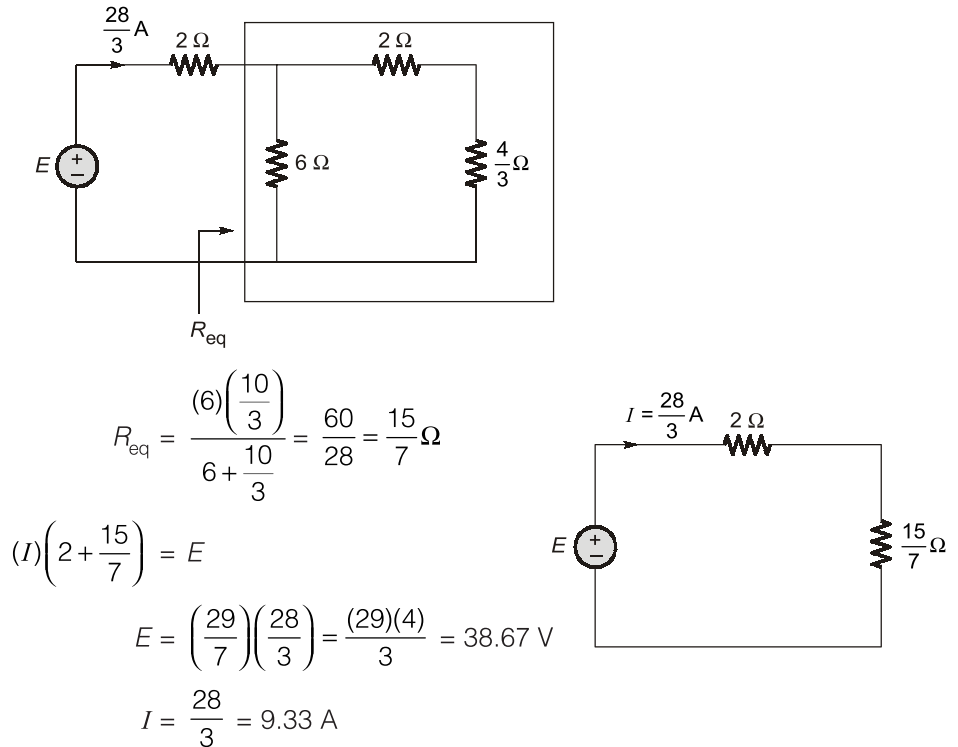
$$I_1 = 6 \text{ A} = I \frac{(18)}{28} \Rightarrow I = \frac{28}{3} \text{ A}$$



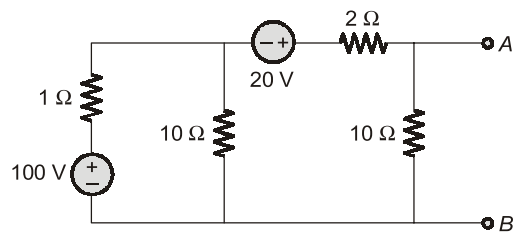
1.9 Obtain the Norton's equivalent circuit at the terminals A and B for the network shown in figure.



[CSE-2014 : 20 marks]

Solution:

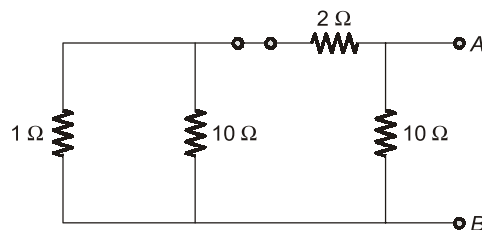R_N : Calculate same way as R_{th} . Short all independent voltage source




$$(1\Omega \parallel 10\Omega) = \frac{10}{11} \Omega$$

$$2 \Omega \text{ in series with } \frac{10}{11} \Omega = \frac{32}{11} \Omega$$

$$R_N = R_{AB} = (10\Omega) \parallel \left(\frac{32}{11} \Omega\right) = \frac{(10)\left(\frac{32}{11}\right)}{10 + \frac{32}{11}} = \frac{320}{142}$$

$$R_N = 2.25 \Omega$$

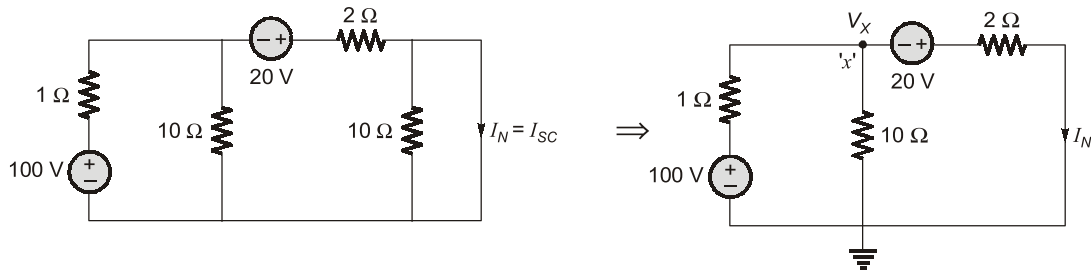I_N : Short terminal AB to get $I_{SC} = I_N$



Consider node (x) equation,


$$\frac{V_x - 100}{1} + \frac{V_x}{10} + \frac{V_x + 20}{2} = 0$$

$$V_x \left(1 + \frac{1}{10} + \frac{1}{2} \right) - 100 + 10 = 0$$


$$V_x (1 + 0.1 + 0.5) = 90$$

$$V_x = 56.25 \text{ V}$$
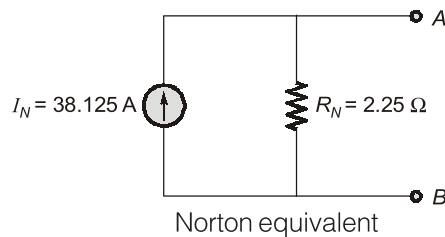
$$I_N = \frac{V_x + 20}{2} = \frac{56.25 + 20}{2} = 38.125 \text{ A}$$



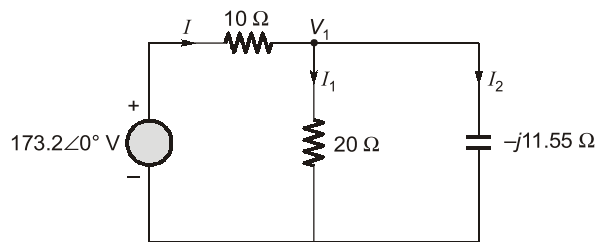1.10 For the circuit shown in figure, evaluate the current through and the voltage across each element.



[CSE-2015 : 10 marks]

Solution:

Nodal equation of node (1):

$$\frac{V_1 - 173.2}{10} + \frac{V_1}{20} + \frac{V_1}{-j11.55} = 0$$

$$V_1 \left(\frac{1}{10} + \frac{1}{20} - \frac{1}{j11.55} \right) = 17.32$$


$$V_1 (0.1 + 0.05 + j0.0866) = 17.32$$

$$V_1 (0.15 + j0.0866) = 17.32$$

$$V_1 (0.1732 \angle 30^\circ) = 17.32$$

$$V_1 = 100 \angle -30^\circ \text{ V}$$
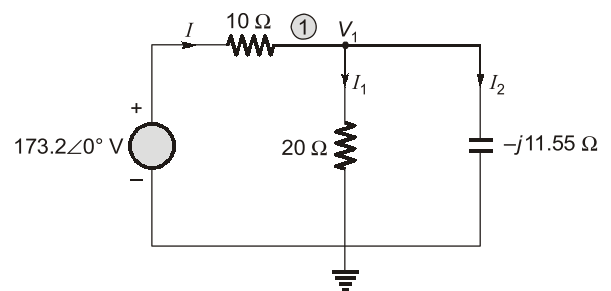
$$I_1 = \frac{V_1}{20} = \frac{100}{20} \angle -30^\circ = 5 \angle -30^\circ \text{ A}$$



$$I_2 = \frac{V_1}{-j11.55} = \frac{100\angle -30^\circ}{11.55\angle -90^\circ} = 8.66\angle 60^\circ \text{ A}$$

$$I = \frac{173.2 - 100\angle -30^\circ}{10} = \frac{173.2 - 86.6 + j50}{10} = \frac{100\angle 30^\circ}{10} = 10\angle 30^\circ \text{ A}$$

$$V_{10\Omega} = 173.2\angle 0^\circ - 100\angle -30^\circ = 100\angle 30^\circ$$

$$I_1 = 5\angle -30^\circ \text{ A}$$


$$I_2 = 8.66\angle 60^\circ \text{ A}$$

$$I = 10\angle 30^\circ \text{ A}$$

$$V_1 = 100\angle -30^\circ \text{ V}$$

$$V_{10\Omega} = 100\angle 30^\circ \text{ V}$$

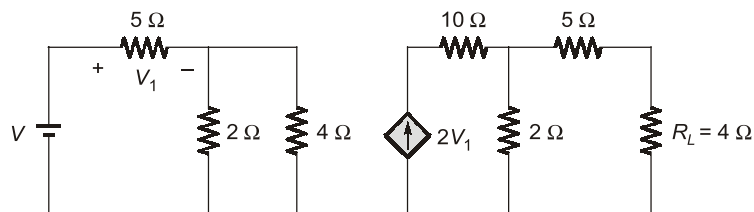
1.11 For the circuit shown in figure. Find the value of V if the power dissipated in the load resistance R_L is 36 Watts.



[CSE-2016 : 20 marks]

Solution:

The circuit can be drawn as,

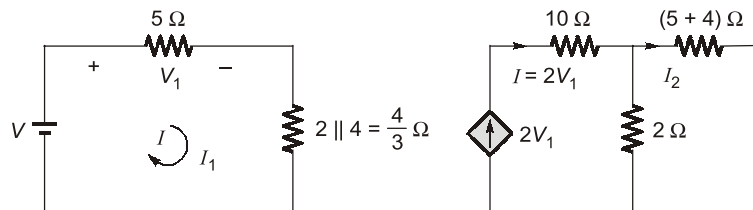

Applying KVL in loop (1),

$$-V + 5I_1 + \frac{4}{3}I_1 = 0$$

$$V = \frac{19}{3}I_1 \Rightarrow I_1 = \frac{3V}{19}$$

$$V_1 = 5I_1 = 5 \times \frac{3V}{19} = \frac{15}{19}V \quad \dots(1)$$

Now, using current division rule in I_2 loop,

$$I_2 = I \times \frac{2}{2+9} = 2V_1 \times \frac{2}{11} = \frac{4}{11}V_1 \quad \dots(2)$$

This current will flow in load resistance R_L' .

$$\therefore \text{Power dissipation in load } R_L, \quad P = I_2^2 \cdot R_L$$

$$\therefore \quad P = \left(\frac{4}{11}V_1 \right)^2 \cdot 4 \quad \text{From equation (2)}$$

$$\therefore \quad P = \left(\frac{4}{11} \times \frac{15}{19}V \right)^2 \cdot 4 \quad \text{From equation (1)}$$

$$\therefore \quad P = 0.08241 \times 4V^2 = 0.33 \text{ V}^2$$

Given,

$$P = 36 \text{ W}$$


∴

$$0.33 V^2 = 36 \text{ W}$$

∴

$$V = \sqrt{\frac{36}{0.33}} = 10.45 \text{ V}$$

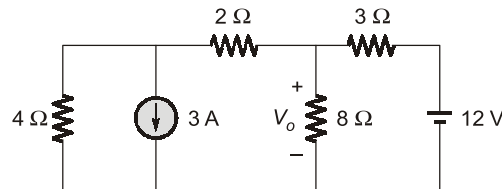
1.12 In the circuit shown in figure, find the voltage V_o across the 8Ω resistor.




[CSE-2018 : 10 marks]

Solution:

The given circuit is

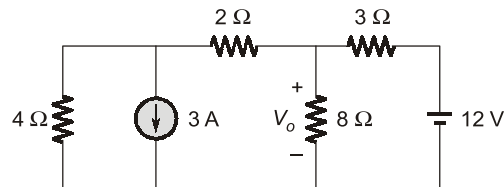

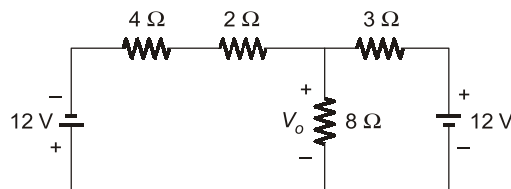The above circuit can be transformed into the circuit as (current source to voltage source transformation)



The equivalent circuit is as

Applying the KVL at node (1)


$$\frac{V_o + 12}{6} + \frac{V_o}{8} + \frac{V_o - 12}{3} = 0$$

$$4V_o + 48 + 3V_o + 8V_o - 96 = 0$$


$$15V_o = 48$$

$$V_o = \frac{48}{15} = 3.2 \text{ V}$$

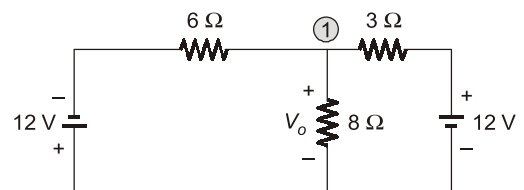Hence, the voltage V_o across the 8Ω resistor is 3.2 V.



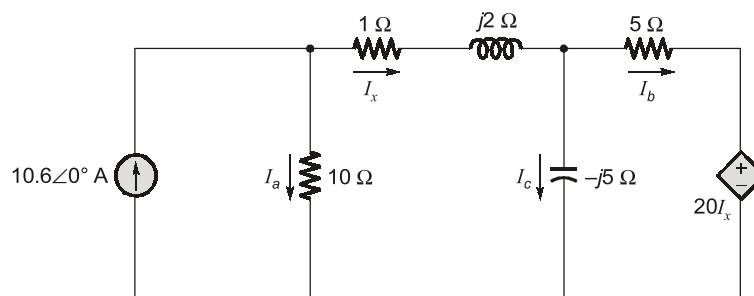
1.13 Find the values of branch currents I_a , I_b and I_c as indicated in the circuit shown below.



[CSE-2020 : 10 marks]

Solution:

Given circuit :

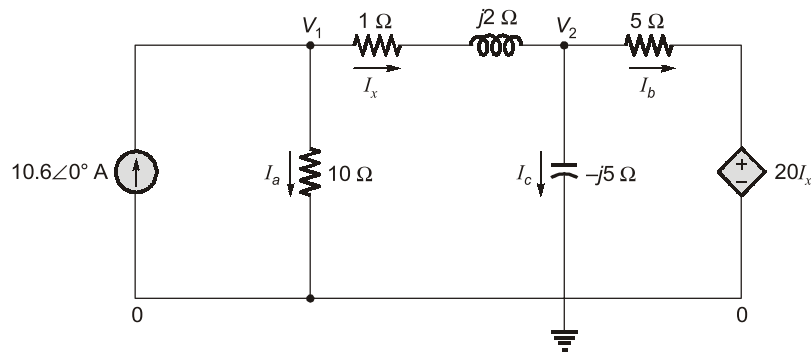

Applying KCL at node V_1 , we get

$$10.6\angle 0^\circ = \frac{V_1}{10} + \frac{V_1 - V_2}{1 + j2}$$

$$\Rightarrow V_1 \left[\frac{1}{10} + \frac{1}{1 + j2} \right] - \frac{V_2}{1 + j2} = 10.6\angle 0^\circ$$

$$(0.3 - 0.4j)V_1 - (0.2 - 0.4j)V_2 = 10.6\angle 0^\circ \quad \dots(1)$$

$$\frac{V_1 - V_2}{1 + j2} = I_x \quad \dots(2)$$

Applying KCL at node V_2 , we get

$$\frac{-V_2}{j5} + \frac{V_2 - V_1}{1 + j2} + \frac{V_2 - 20I_x}{5} = 0$$

$$\frac{-V_2}{j} + \frac{5(V_2 - V_1)}{1 + j2} + V_2 - 20 \left[\frac{V_1 - V_2}{1 + j2} \right] = 0$$

$$V_2 \left[\frac{-1}{j} + \frac{5}{1 + j2} + 1 + \frac{20}{1 + j2} \right] - V_1 \left[\frac{5}{1 + j2} + \frac{20}{1 + j2} \right] = 0$$

$$-V_1(5 - 10j) + (6 - 9j)V_2 = 0$$

$$V_1 = \frac{(6 - 9j)}{(5 - 10j)} V_2 \Rightarrow (0.96 + 0.12j)V_2 \quad \dots(2)$$

From (1) and (2)

$$(0.3 - 0.4j)(0.96 + 0.12j)V_2 - (0.2 - 0.4j)V_2 = 10.6\angle 0^\circ$$

$$V_2 = 72.80\angle -20.92^\circ \text{ V}$$

$$V_1 = 70.43\angle -13.80^\circ \text{ V}$$


$$I_a = \frac{V_1}{10} = 7.043\angle -13.80^\circ \text{ A}$$

$$I_c = \frac{V_2}{-j5} = \frac{72.80\angle -20.92^\circ}{-5j} = 14.56\angle 69.08^\circ \text{ A}$$

$$I_x = \frac{V_1 - V_2}{1 + j2} = 4.11\angle 24^\circ \text{ A}$$


$$I_b = I_x - I_c = 12.01\angle -96.90^\circ \text{ A}$$

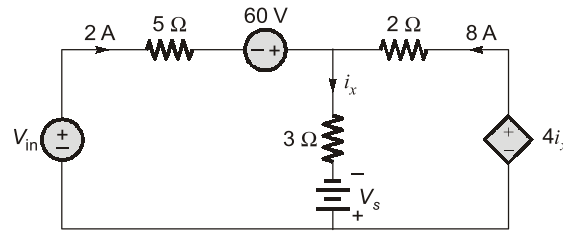1.14 For the circuit shown in figure, find the V_{in} , V_s and power supplied by the dependent source



[CSE-2022 : 10 marks]

Solution:

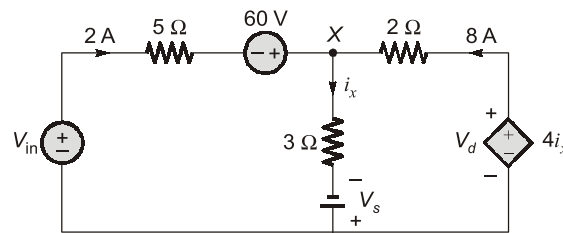

By KCL at Node X;

$$-2 - 8 + i_X = 0$$

$$i_X = 10 \text{ A}$$

$$V_d = 4i_X = 40 \text{ V}$$

...(i)

Power supplied by dependent source = $40 \times 10 = 400 \text{ W}$

By Ohm's law,

$$V_X = 3i_X - V_s$$

...(ii)

$$V_X = 4i_X - 8$$

...(iii)

$$V_X = 60 + V_{in} - 5$$

...(iv)

By (iii),

$$V_X = 40 - 16 = 24 \text{ V}$$


Using (i) and (iii) in (ii),

$$V_s = 3i_X - V_X = 6 \text{ V}$$

Using (i) and (iii) in (iv),

$$V_{in} = -26 \text{ V}$$

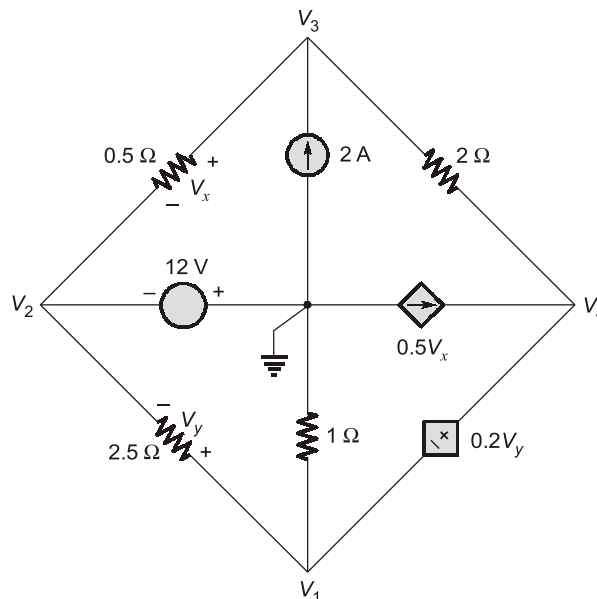1.15 For the circuit shown in figure, obtain the value of voltage across 0.5Ω and 2.5Ω resistors using nodal current analysis.



[CSE-2023 : 20 marks]

Solution:

By KVL,

$$V_x = V_3 - V_2 \quad \dots(i)$$

$$V_y = V_1 - V_2 \quad \dots(ii)$$

$$V_2 = -12V \quad \dots(iii)$$

KCL at Node 3 :

$$\frac{V_3 - (-12)}{0.5} - 2 + \frac{V_3 - V_4}{2} = 0$$

$$4V_3 + 48 - 4 + V_3 - V_4 = 0$$

$$5V_3 - V_4 = -44 \quad \dots(iv)$$

KCL at super node 1-4 :

$$\frac{V_1}{1} + \frac{V_1 - (-12)}{2.5} - 0.5V_x + \frac{V_4 - V_3}{2} = 0 \quad \dots(v)$$

(i) in (v) :

$$5V_1 + 2V_1 + 24 - 2.5(V_3 - V_2) + 2.5V_4 - 2.5V_3 = 0$$

$$7V_1 - 5V_3 + 2.5V_4 = 6 \quad \dots(vi)$$

By KVL :

$$V_4 - V_1 = 0.2V_y = 0.2(V_1 - V_2)$$

$$V_4 - V_1 = 0.2V_1 + 2.4$$

$$-1.2V_1 + V_4 = 2.4 \quad \dots(vii)$$

Solving (iv), (vi) and (vii)

$$V_1 = -4.73 \text{ V}$$

$$V_2 = -12 \text{ V}$$

$$V_3 = -9.45 \text{ V}$$

$$V_4 = -3.27 \text{ V}$$

Voltage across 0.5Ω resistor,

$$V_x = V_3 - V_2$$


$$V_x = 2.55 \text{ V}$$

Voltage across 2.5Ω resistor,

$$V_y = V_1 - V_2$$


$$V_y = 7.27 \text{ V}$$

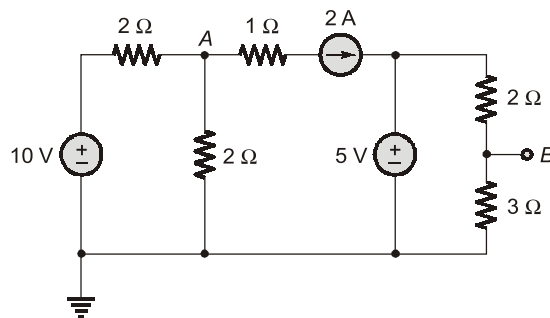1.16 Find the voltage on points *A* and *B* of the given circuit :



[CSE-2024 : 10 marks]

Solution:

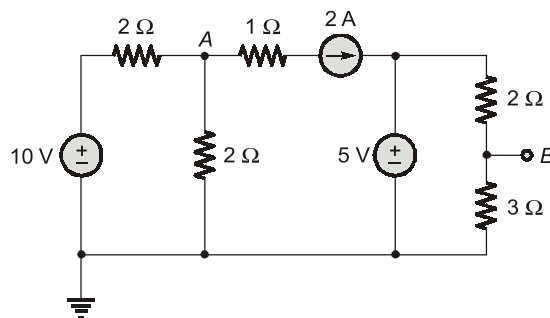

By voltage division,

$$V_B = \frac{3}{3+2} \times 5 = 3 \text{ V}$$

By KCL at point A,

$$\frac{V_A - 10}{2} + \frac{V_A}{2} + 2 = 0$$


$$V_A - 10 + V_A + 4 = 0$$

$$2V_A = 6$$

$$V_A = 3 \text{ V}$$


$$V_B = 3 \text{ V}$$

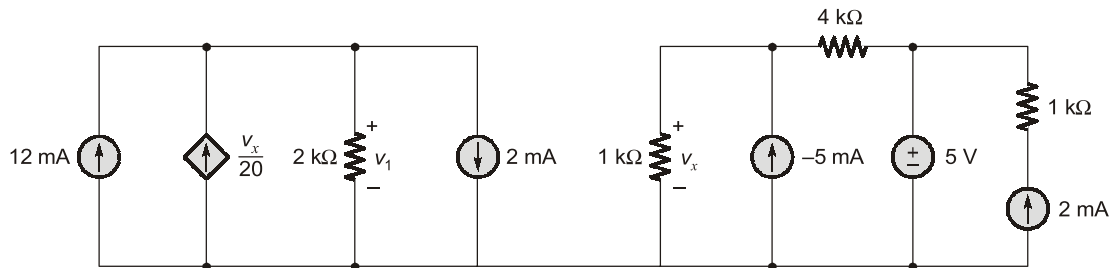1.17 In the circuit given here, find the value of voltage v_1 :



[CSE-2024 : 10 marks]

Solution:

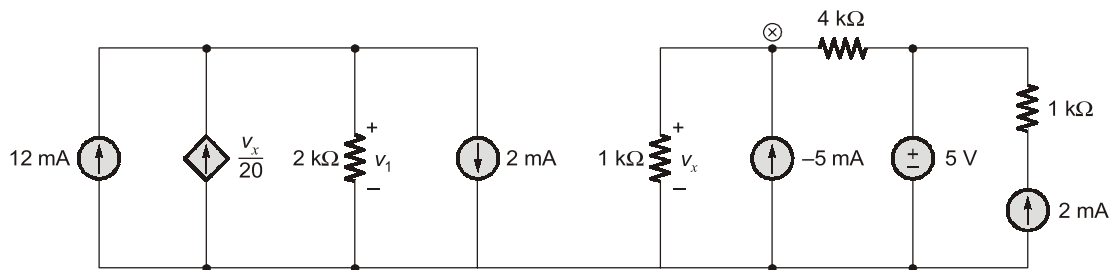

By KCL at point X :

$$\frac{V_X}{1 \text{ k}\Omega} - (-5 \times 10^{-3}) + \frac{V_X - 5}{4 \text{ k}\Omega} = 0$$

$$4V_X + 5 + V_X - 5 = 0$$

$$V_X = 0$$

By KCL :

$$I_1 = 12 \text{ mA} + \frac{V_X}{20} - 2 \text{ mA}$$

$$I_1 = 10 \text{ mA}$$

$$v_1 = I_1 \times 2 \text{ k}\Omega$$

$$v_1 = 20 \text{ V}$$

(By Ohm's law)

2. Network Theorems

2.1 If an impedance Z_L is connected across a voltage source V_s with source impedance Z_s , then for maximum power transfer, what will be the load impedance?

[CSE-2004 : 4 marks]