

Electrical Engineering

PRACTICE BOOK

for

Junior Engineer

2900 MCQs

Fully solved multiple choice questions
with detailed explanations

Useful for

All examinations of Junior Engineer Level





MADE EASY Publications

Corporate Office: 44-A/4, Kalu Sarai (Near Hauz Khas Metro Station), New Delhi-110016

E-mail: infomep@madeeasy.in

Contact: 011-45124660, 0-8860378007

Visit us at: www.madeeasypublications.org

2900 MCQs for Junior Engineer : Electrical Engineering Practice Book

© Copyright, by MADE EASY Publications.

All rights are reserved. No part of this publication may be reproduced, stored in or introduced into a retrieval system, or transmitted in any form or by any means (electronic, mechanical, photo-copying, recording or otherwise), without the prior written permission of the above mentioned publisher of this book.

First Edition: 2024

MADE EASY PUBLICATIONS PVT. LTD. has taken due care in collecting the data and providing the solutions, before publishing this book. In spite of this, if any inaccuracy or printing error occurs then MADE EASY PUBLICATIONS PVT. LTD owes no responsibility. MADE EASY PUBLICATIONS PVT. LTD will be grateful if you could point out any such error. Your suggestions will be appreciated.

© All rights reserved by MADE EASY PUBLICATIONS PVT. LTD. No part of this book may be reproduced or utilized in any form without the written permission from the publisher.

Contents


Sl.	Subject	Page No.
1.	Circuit Theory.....	1-78
2.	AC Fundamentals and Magnetic Circuit.....	79-167
3.	Measurement & Measuring Instruments	168-261
4.	Electrical Machines	262-374
5.	Generation, Transmission and Distribution	375-458
6.	Estimation & Costing and Utilization of Electrical Energy	459-476
7.	Basic Electronics.....	477-546



UNIT 1


Circuit Theory

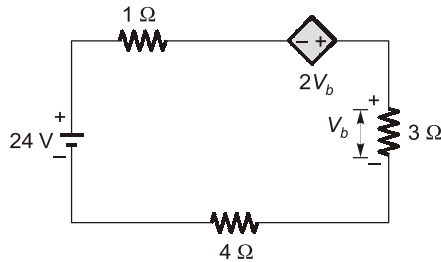Q.1 The current in the given circuit with a dependent voltage source is




- (a) 10 A (b) 12 A
(c) 14 A (d) 16 A

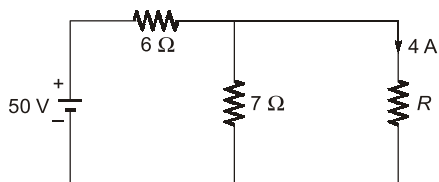Q.2 The value of resistance ' R ' shown in the given figure is




- (a) 3.5 Ω (b) 2.5 Ω
(c) 1 Ω (d) 4.5 Ω

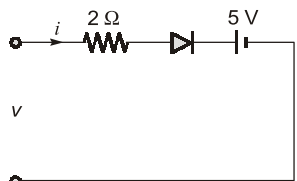
Q.3 The figure shows a network in which the diode is an ideal one.



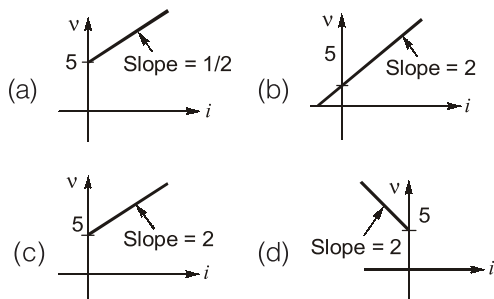The terminal v-i characteristics of the network is given by




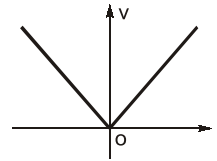Q.4 The v-i characteristic of an element is shown in the figure given below. The element is




- (a) non-linear, active, non-bilateral
(b) linear, active, non-bilateral
(c) non-linear, passive, non-bilateral
(d) non-linear, active, bilateral

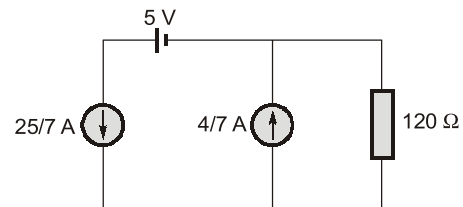Q.5 The current through 120 ohm resistor in the circuit shown in the figure below is




- (a) 1 A (b) 2 A
(c) 3 A (d) 4 A

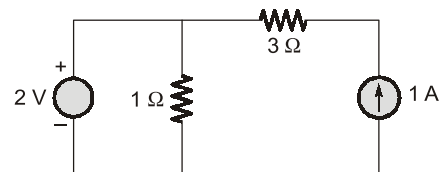Q.6 For the circuit given in figure below the power delivered by the 2 volt source is given by



- (a) 4 W (b) 2 W
(c) -2 W (d) -4 W

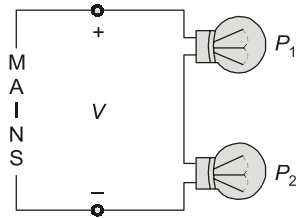Q.7 The incandescent bulbs rated respectively as P_1 and P_2 for operation at a specified mains voltage are connected in series across the mains as shown in the above figure. Then the total power supplied by the mains to the two bulbs are




- (a) $\frac{P_1 P_2}{P_1 + P_2}$
- (b) $\sqrt{P_1^2 + P_2^2}$
- (c) $(P_1 + P_2)$
- (d) $\sqrt{P_1 \times P_2}$

Q.8 A certain network consists of a large number of ideal linear resistances, one of which is designated as R and two constant ideal sources. The power consumed by R is P_1 when only the first source is active, and P_2 when only the second source is active. If both sources are active simultaneously, then the power consumed by R is


- (a) $P_1 \pm P_2$
- (b) $\sqrt{P_1} \pm \sqrt{P_2}$
- (c) $(\sqrt{P_1} \pm \sqrt{P_2})^2$
- (d) $(P_1 \pm P_2)^2$

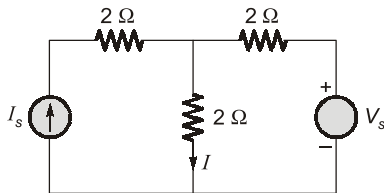Q.9 For the circuit shown below, the value of V_s is 0 when $I = 4$ A. The value of I when $V_s = 16$ V, is



- (a) 6 A
- (b) 8 A
- (c) 10 A
- (d) 12 A

Q.10 Consider the following circuit:

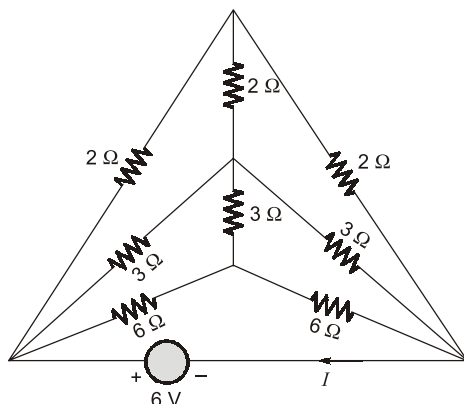


What is the value of the current- I in the above circuit ?

- (a) 1 A
- (b) 2 A
- (c) 3 A
- (d) 4 A

Q.11 In a network made up of linear resistors and ideal voltage sources, values of all resistors are doubled. Then the voltage across each resistor is

- (a) Doubled
- (b) Halved
- (c) Decreases four times
- (d) Not changed

Q.12 Consider the following circuit:

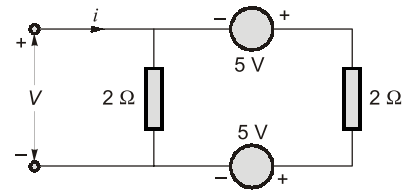

Which one of the following statements is correct?


The circuit shown above is

- (a) passive and linear
- (b) active and linear
- (c) passive and non-linear
- (d) active and non-linear

Q.13 Three parallel resistive branches are connected across a d.c. supply. What will be the ratio of the branch currents $I_1 : I_2 : I_3$ if the branch resistances are in the ratio $R_1 : R_2 : R_3 :: 2 : 4 : 6$?


- (a) 3 : 2 : 6
- (b) 2 : 4 : 6
- (c) 6 : 3 : 2
- (d) 6 : 2 : 4

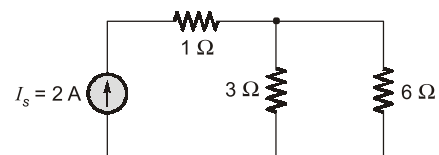Q.14 For the circuit shown below, what is the voltage across the current source I_s ?




- (a) 0
- (b) 2 V
- (c) 3 V
- (d) 6 V

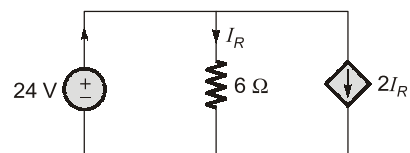Q.15 Consider the circuit in the below figure. What is the power delivered by the 24 V source?




- (a) 96 W (b) 144 W
- (c) 192 W (d) 288 W

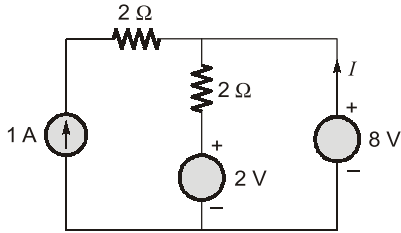Q.16 In the circuit shown below, what is the value of the current- I ?




- (a) 1 A (b) 2 A
- (c) 3 A (d) 4 A

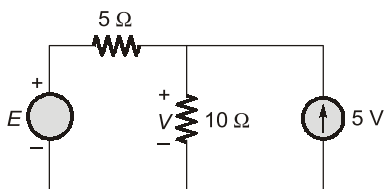Q.17 If the voltage V across 10 W resistance is 10 V , what is the voltage E of the voltage source in the circuit shown below?




- (a) -50 V (b) -10 V
- (c) +10 V (d) +50 V

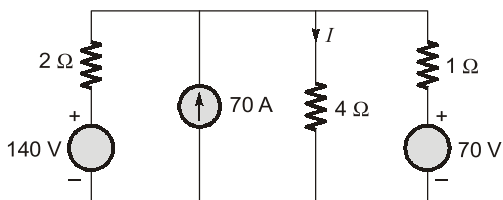Q.18 What is the value of the current I in the circuit shown below?




- (a) 20 A (b) 25 A
- (c) 30 A (d) 36 A

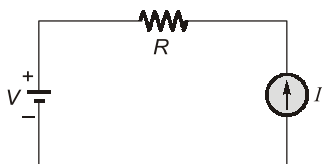Q.19 For the network shown in the figure below, what is the voltage across the current source?




- (a) $V - RI$ (b) $V + RI$
- (c) Zero (d) $RI - V$

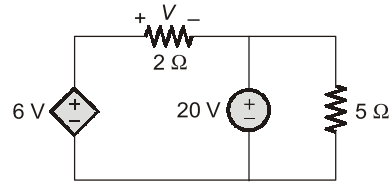Q.20 What is the current through the $2\ \Omega$ resistance for the circuit as shown below?




- (a) 5 A (b) 4 A
- (c) 3 A (d) 2 A

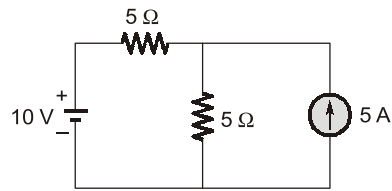Q.21 What is the voltage across the current source for the below shown circuit?




- (a) 5.0 V (b) 7.5 V
- (c) 12.5 V (d) 17.5 V

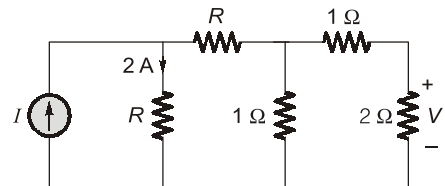Q.22 What is the value of I for the below shown circuit, if $V = 2\text{ volts}$?




- (a) 2 A (b) 4 A
- (c) 6 A (d) 8 A

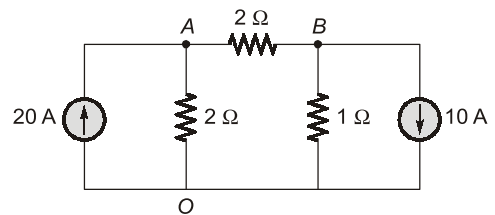Q.23 Find the voltage of the node A with respect to 'O' for the circuit as shown in below.




- (a) 40 V (b) 20 V
- (c) 50 V (d) 60 V

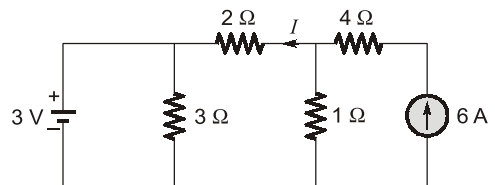Q.24 For the circuit as shown below, what is the value of I ?




- (a) 4 A
- (b) 3 A
- (c) 2 A
- (d) 1 A

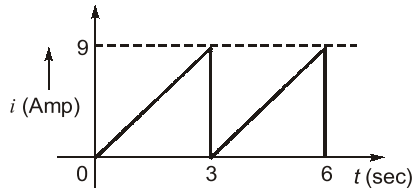Q.25 The current waveform as shown below, is applied in a pure resistor of 10Ω . What is the power dissipated in the resistor?




- (a) 270 W
- (b) 135 W
- (c) 52 W
- (d) 7 W

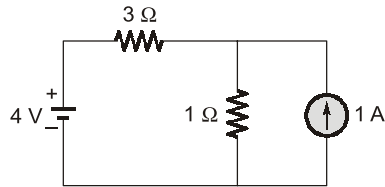Q.26 For the circuit shown in the figure below, the voltage across the 1 ohm resistor is given by




- (a) $7 \text{ V}/4$
- (b) $5 \text{ V}/4$
- (c) $7 \text{ V}/3$
- (d) $2 \text{ V}/3$

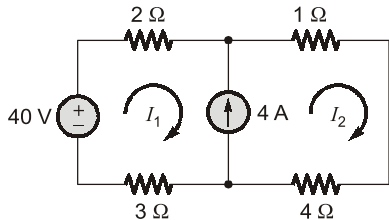Q.27 The currents I_1 and I_2 in the below circuit are respectively




- (a) 4 A; 4 A
- (b) 3 A; 5 A
- (c) 2 A; 6 A
- (d) 6 A; 2 A

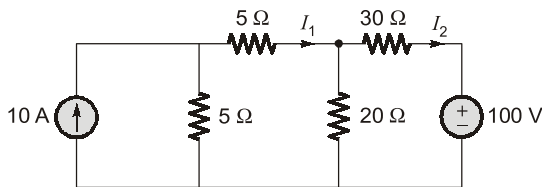Q.28 The currents I_1 and I_2 in the below circuit are respectively




- (a) 1.818 A; -0.4545 A
- (b) 2.451 A; -1.568 A
- (c) 0.4545 A; -1.818 A
- (d) 1.56 A; -2.45 A

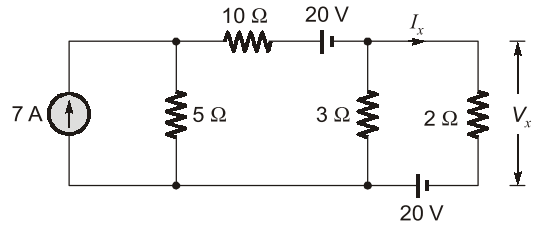Q.29 The currents I_x and V_x in the below circuit are respectively




- (a) 5 A; 10 V
- (b) 10 A; 20 V
- (c) 6 A; 12 V
- (d) 4 A; 8 V

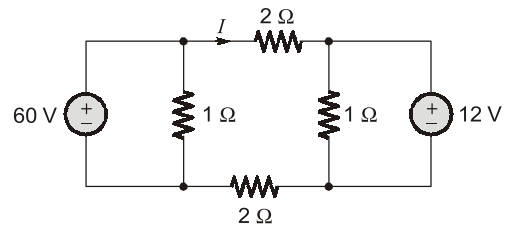Q.30 For the circuit shown in figure below, the value of current, I is




- (a) 2 A
- (b) 3 A
- (c) 6 A
- (d) 12 A

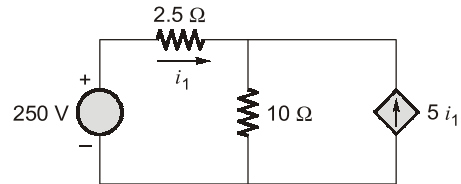Q.31 In the circuit shown, the current i_1 is




- (a) 4 A
- (b) 2 A
- (c) 4.76 A
- (d) 20 A

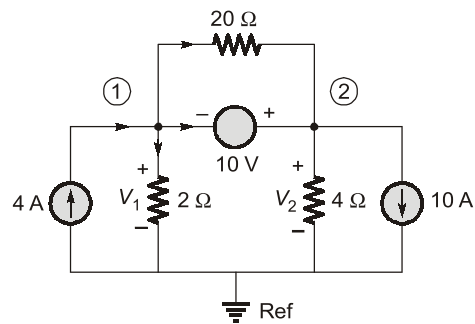Q.32 When KCL is applied at the super node in the below circuit, the current equation in terms of node voltages V_1 and V_2 is




- (a) $-6 = \frac{V_1}{2} + \frac{V_2}{4}$
- (b) $4 = \frac{V_1 - V_2}{2} + \frac{V_1 - V_2}{20}$
- (c) $4 = \frac{V_1}{2} + \frac{V_1 - V_2}{20}$
- (d) $4 = \frac{V_1}{2} + \frac{V_2}{4}$

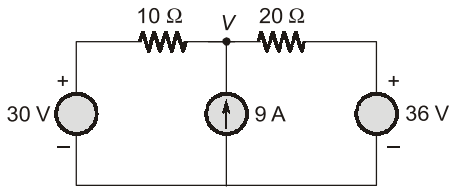Q.33 The node voltage V in the circuit is




- (a) 6 V
- (b) 30 V
- (c) 36 V
- (d) 92 V

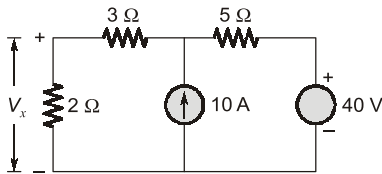Q.34 The voltage V_x across the $2\ \Omega$ resistance in the circuit is



- (a) 16 V
- (b) 60 V
- (c) 18 V
- (d) 10 V

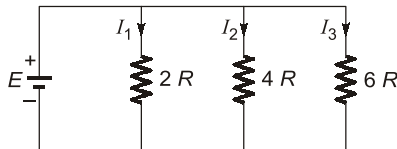Q.35 Three parallel branches of resistors are connected across a d.c. source as shown in the figure. What is $I_1 : I_2 : I_3$?




- (a) 3 : 2 : 6
- (b) 2 : 4 : 6
- (c) 6 : 3 : 2
- (d) 6 : 2 : 4

Q.36 The number of independent KVL and KCL equations for a network with n -nodes and l links are respectively


- (a) l and n
- (b) l and $n - 1$
- (c) $n - 1$ and l
- (d) $n - 1$ and $l - 1$

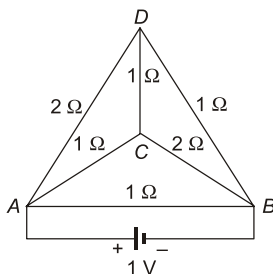Q.37 A triangular pyramid, built up of six wires whose resistances are shown in the figure, is fed from a 1 V battery at the terminals A and B . The current through the branch DB is



- (a) $\frac{1}{7}$ A
- (b) $\frac{2}{7}$ A
- (c) $\frac{3}{7}$ A
- (d) $\frac{4}{7}$ A

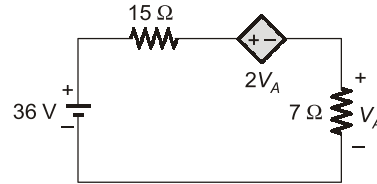Q.38 The power dissipated in the controlled source of the network shown below is



- (a) 36 W
- (b) 15 W
- (c) 07 W
- (d) 14 W

Q.39 A conductor of diameter d , length l consumes a power of W when a current I flows through it. What will be the power consumed if d is doubled, l is halved and current is tripled?

- (a) 18 W
- (b) 36 W
- (c) 48 W
- (d) $9/8$ W

Q.40 Consider the following two types of non-identical sources:

1. Voltage source $e_1(t)$ and $e_2(t)$
2. Current sources i_1 and $i_2(t)$

Regarding the mode of their connection in a circuit.

- (a) 1 cannot be connected in parallel, and 2 cannot be connected in series.
- (b) 1 cannot be connected in series, and 2 cannot be connected in parallel.
- (c) Both 1 and 2 cannot be connected in parallel.
- (d) Both 1 and 2 cannot be connected in parallel


Q.41 n resistors each of resistance R when connected in series offer an equivalent resistance of $50\ \Omega$ and when reconnected in parallel the effective resistance is $2\ \Omega$. The value of R is

- (a) $2.5\ \Omega$
- (b) $5\ \Omega$
- (c) $7.5\ \Omega$
- (d) $10\ \Omega$

Q.42 Two bulbs of $100\text{ W}/250\text{ V}$ and $150\text{ W}/250\text{ V}$ are connected in series across a supply of 250 V . The power consumed by the circuit is

- (a) 30 W
- (b) 60 W
- (c) 100 W
- (d) 250 W

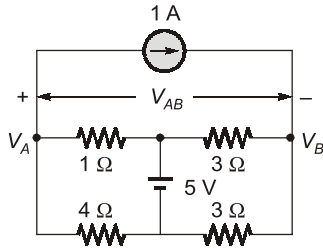Q.43 The potential difference V_{AB} in the circuit is



- (a) 0.8 V
- (b) -0.8 V
- (c) 1.8 V
- (d) -1.8 V

Q.44 Three 30 Ω resistors are connected in parallel across an ideal 40 V source. What would be the equivalent resistance seen by the load connected across this circuit?

- (a) 0 Ω
- (b) 10 Ω
- (c) 20 Ω
- (d) 30 Ω

Q.45 Two networks are said to be dual when

- (a) their node equations are the same
- (b) the loop equations of one network are analogous to the node equations of the other
- (c) their loop equations are the same
- (d) the voltage sources of one networks are the current sources of the other


Q.46 The mesh-current method

1. works with both planar and non-planar circuits.
2. uses Kirchhoffs voltage law.

Which of the above is/are correct?

- (a) 1 only
- (b) 2 only
- (c) Both 1 and 2
- (d) Neither 1 nor 2

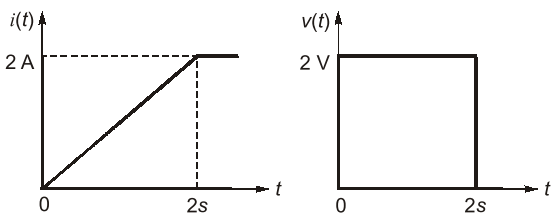
Q.47 The voltage and current waveforms for an element are shown in the figure.



The circuit element and its value are


- (a) Capacitor, 2 F
- (b) Inductor, 2 H
- (c) Capacitor, 0.5 F
- (d) Inductor, 0.5 H

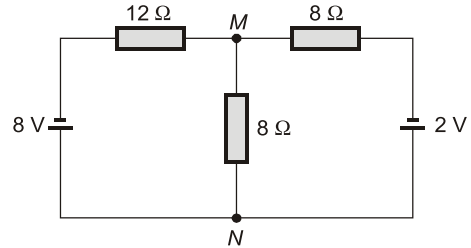Q.48 What is the current through the 8 Ω resistance connected across terminals, M and N in the circuit?




- (a) 0.34 A from M to N
- (b) 0.29 A from M to N
- (c) 0.29 A from N to M
- (d) 0.34 A from N to M

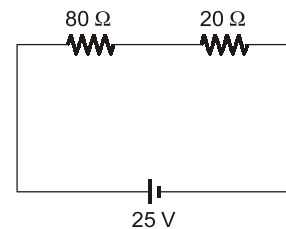Q.49 What is the potential drop across the 80 Ω resistor in the figure?




- (a) 20 V
- (b) 15 V
- (c) 10 V
- (d) 5 V

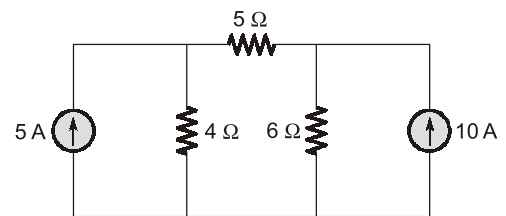Q.50 What is the current through the 5 Ω resistance in the circuit shown?




- (a) 5.33 A
- (b) 4.66 A
- (c) 2.66 A
- (d) 1.33 A

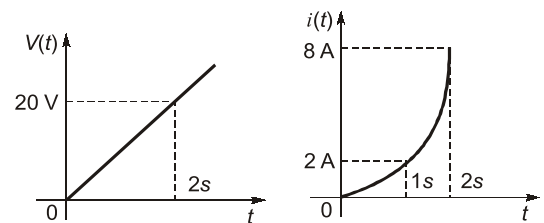Q.51 The voltage and current characteristic of an element is as shown in figure. The nature and value of the element are




- (a) Capacitor of 3.3 μF
- (b) Inductor of 2.5 H
- (c) Capacitor of 6.7 μF
- (d) Inductor of 5.0 H

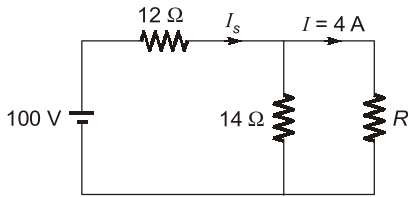Q.52 In the circuit shown, what value of R will result in $I = 4\text{ A}$?




- (a) $9\ \Omega$
- (b) $7\ \Omega$
- (c) $5.5\ \Omega$
- (d) $3.5\ \Omega$

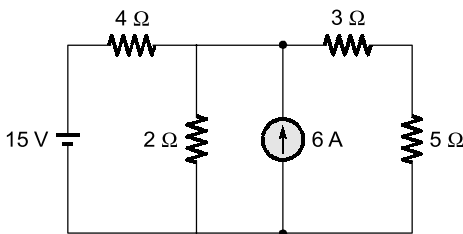Q.53 For the network shown in the figure, the current flowing through the $5\ \Omega$ resistance will be




- (a) $\frac{37}{25}\text{ A}$
- (b) $\frac{40}{28}\text{ A}$
- (c) $\frac{39}{28}\text{ A}$
- (d) $\frac{41}{28}\text{ A}$

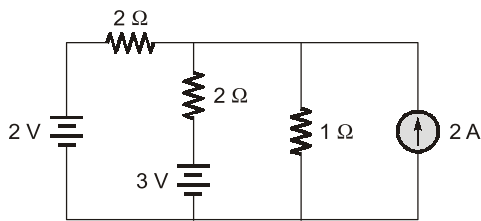Q.54 The current in the $1\ \Omega$ resistor in the network as shown is




- (a) 2.00 A
- (b) 2.25 A
- (c) 2.50 A
- (d) 2.75 A

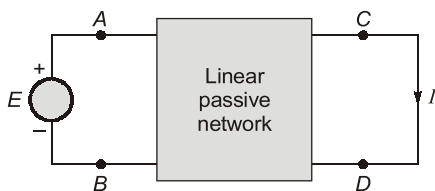Q.55 For the circuit shown in the given figure, when the voltage E is 10 V , the current I is 1 A . If the applied voltage across terminal C-D is 100 V , the short circuit current flowing through the terminal A-B will be




- (a) 0.1 A
- (b) 1 A
- (c) 10 A
- (d) 100 A

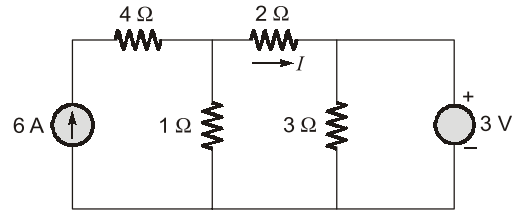Q.56 For the circuit shown in the given figure the current I is given by




- (a) 3 A
- (b) 2 A
- (c) 1 A
- (d) zero

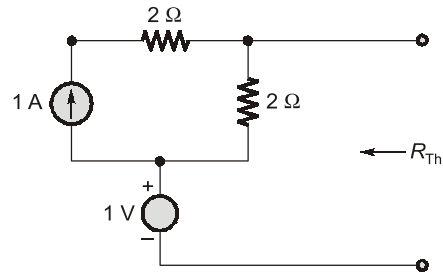Q.57 The Thevenin's equivalent resistance R_{Th} for the given network is



- (a) $1\ \Omega$
- (b) $2\ \Omega$
- (c) $4\ \Omega$
- (d) infinity

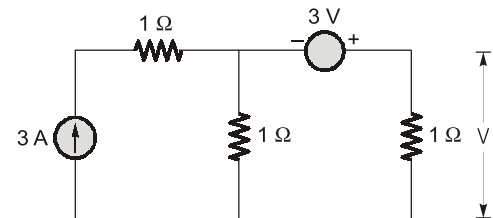Q.58 The value of V in the circuit shown in the given figure is



- (a) 1 V
- (b) 2 V
- (c) 3 V
- (d) 4 V

Q.59 The Norton's equivalent of circuit shown in Figure-I is drawn in the circuit shown in Figure-II. The value of I_{SC} and R_{eq} in Figure-II are respectively

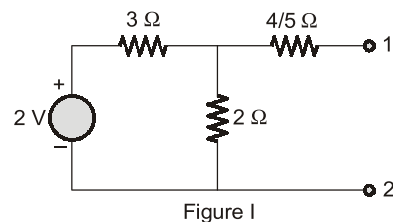
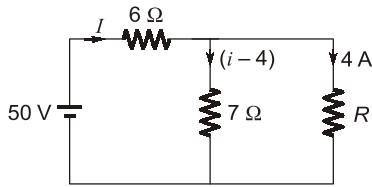


Figure I

Explanations

1. (b)


Applying KVL in the loop
 $24 - 1I + 2V_b - V_b - 4I = 0$
 where, $V_b = 3I$
 $\Rightarrow 24 - 5I + V_b = 0$
 $\Rightarrow 24 - 5I + 3I = 0$
 $I = 12 \text{ A}$

2. (a)

By applying KVL in 1st loop
 $50 = 6i + 7(i - 4)$
 $\Rightarrow 13i = 78$
 $\Rightarrow i = 6 \text{ A}$
 Now, by applying KVL in 2nd loop
 $7 \times 2 = 4 \times R$
 $R = 3.5 \Omega$

3. (c)


By applying KVL
 The terminal v-i characteristic is $v = 2i + 5$

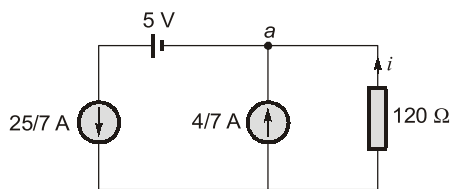5. (c)

By applying KCL at node a

$$i = \frac{25}{7} - \frac{4}{7} = 3 \text{ A}$$

Voltage source in series with constant current source will behave like short circuit.

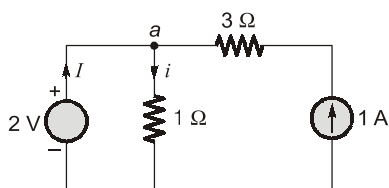6. (b)

From figure, $i = \frac{2}{1} = 2 \text{ Amp}$

By applying KCL at node a

$$I = i - 1 = 2 - 1 = 1 \text{ Amp}$$

i.e. the current delivered by voltage source = 1 amp.

\therefore power delivered by voltage source
 $= 2 \times 1 = 2 \text{ W}$

7. (a)

$$R_1 = \frac{V^2}{P_1} \text{ and } R_2 = \frac{V^2}{P_2}$$

Bulbs are connected in series

$$R_{\text{eq}} = R_1 + R_2$$

$$= V^2 \left[\frac{1}{P_1} + \frac{1}{P_2} \right] = V^2 \left[\frac{P_1 + P_2}{P_1 P_2} \right]$$

$$\text{Total power} = \frac{V^2}{R_{\text{eq}}} = \frac{P_1 P_2}{P_1 + P_2}$$

8. (c)

$$i_1 = \sqrt{\frac{P_1}{R}} \text{ and } i_2 = \sqrt{\frac{P_2}{R}}$$

when both source are active

$$i = i_1 \pm i_2 = \sqrt{\frac{P_1}{R}} \pm \sqrt{\frac{P_2}{R}}$$

Total power = $i^2 R$


$$= \left(\sqrt{\frac{P_1}{R}} \pm \sqrt{\frac{P_2}{R}} \right)^2 R$$

$$= (\sqrt{P_1} \pm \sqrt{P_2})^2$$

9. (b)


When,

$$V_s = 0$$

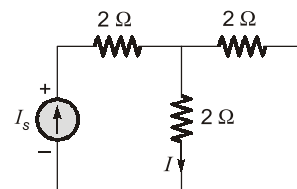

$$I = \frac{I_s}{2}$$
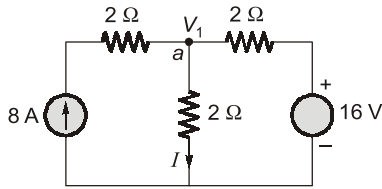
$$\Rightarrow I_s = 2I = 2 \times 4 = 8 \text{ A}$$



When $V_s = 16\text{ V}$

Applying KCL node a,

$$-8 + \frac{V_1}{2} + \frac{V_1 - 16}{2} = 0$$

$$V_1 = 16\text{ V}$$


$$I = \frac{V_1}{2} = \frac{16}{2} = 8\text{ A}$$

10. (c)

Circuit is symmetrical, so voltage at nodes V_A , V_B and V_C are equal and no current flows between these nodes.

or

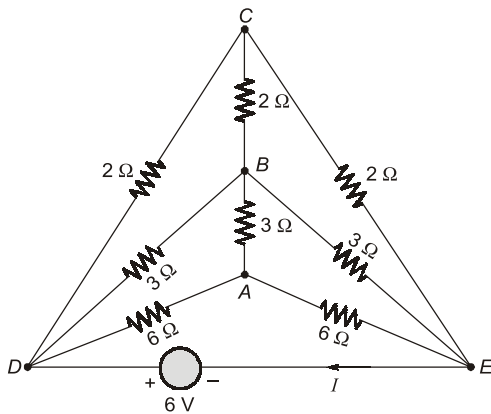$DCEB$ and $DBEA$ are two balanced Wheatstone's bridges hence there will not be any current in branch CB and BA .



$$I = \frac{6}{2+2} + \frac{6}{3+3} + \frac{6}{6+6} = 3\text{ A}$$

11. (d)

Ideal voltage source keeps the terminal voltage constant so accordingly current will change and the voltage across each resistor is unchanged following superposition principle.

12. (a)

In the given circuit there are only resistor/inductor or capacitor and a voltage source, of $V = 5 - 5 = 0\text{ V}$. As these are passive elements and follow the superposition theorem. The circuit is passive and linear.


13. (c)

As all the resistive branches are in parallel. \therefore voltage across each branch will be constant and will be equal to the dc supply voltage $\therefore V = IR = \text{constant}$

$$\Rightarrow I \propto \frac{1}{R}$$

$$\begin{aligned} I_1 : I_2 : I_3 &= \frac{1}{R_1} : \frac{1}{R_2} : \frac{1}{R_3} \\ &= R_2 R_3 : R_1 R_3 : R_1 R_2 \\ &= 24 : 12 : 8 \\ &= 6 : 3 : 2 \end{aligned}$$

14. (d)

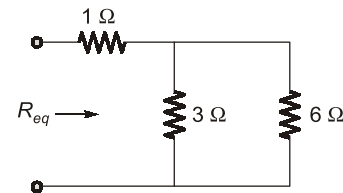

$$\begin{aligned} R_{eq} &= 1 + (3 \parallel 6) = 3\ \Omega \\ \text{Voltage across current source} \\ I_s R_{eq} &= 2 \times 3 = 6\text{ V} \end{aligned}$$

15. (d)

$$I_R = \frac{24}{6} = 4\text{ A}$$

Current delivered by the voltage source.
 $I = I_R + 2I_R = 3I_R = 3 \times 4 = 12\text{ A}$
 Power delivered by the voltage source
 $= 24 \times 12 = 288\text{ W}$

16. (b)

Applying KCL,

$$-1 + \frac{8-2}{2} - I = 0 \Rightarrow I = 2\text{ A}$$

17. (b)

Applying KCL,

$$\begin{aligned} -5 + \frac{V}{10} + \frac{V-E}{5} &= 0 \\ \Rightarrow -5 + \frac{10}{10} + \frac{10-E}{5} &= 0 \\ \Rightarrow E &= -10\text{ V} \end{aligned}$$

18. (c)

Assuming voltage of the node V


Applying KCL,

$$\frac{V - 140}{2} - 70 + \frac{V}{4} + \frac{V - 70}{1} = 0$$

$$\Rightarrow V = 120 \text{ V}$$

$$I = \frac{V}{4} = \frac{120}{4} = 30 \text{ A}$$

19. (b)

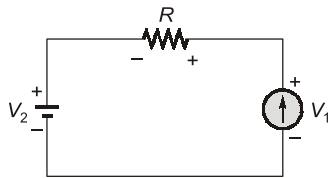


Assuming voltage across current source is V_1

Applying KVL,

$$V + IR - V_1 = 0$$

$$\Rightarrow V_1 = V + IR$$

20. (d)

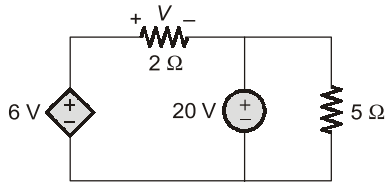


$$6 \text{ V} - V - 20 = 0$$

$$V = 4 \text{ V}$$

$$\text{Current through } 2 \Omega \text{ resistor} = \frac{V}{2} = \frac{4}{2} = 2 \text{ A}$$

21. (d)

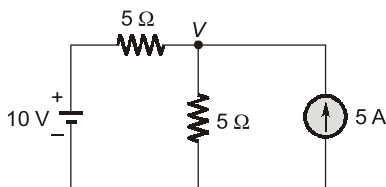


Applying Nodal Analysis

$$\frac{10 - V}{5} + 5 = \frac{V}{5}$$

$$\therefore 10 - V + 25 = V$$

$$\therefore V = 17.5 \text{ V}$$

22. (c)

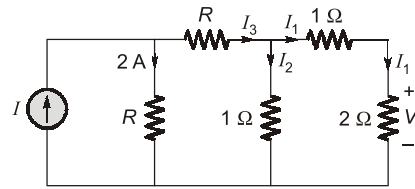

$$V = 2 \text{ V}$$

$$\therefore I_1 = \frac{V}{2} = 1 \text{ A}$$

$$\text{and } I_1 = \left(\frac{1}{1+3} \right) I_3$$

$$I = \frac{1}{4} I_3$$

$$\therefore I_3 = 4 \text{ A}$$

$$\text{and } I = 4 + 2 = 6 \text{ A}$$

23. (b)

Applying Nodal Analysis

$$20 = \frac{V_A}{2} + \frac{V_A - V_B}{2}$$

$$40 = 2V_A - V_B \quad \dots(i)$$

$$\text{and } \frac{V_A + V_B}{2} = \frac{V_B}{1} + 10$$


$$V_A - V_B = 2V_B + 20$$

$$\therefore V_A - 3V_B = 20 \quad \dots(ii)$$

Solving (i) and (ii),

$$V_A = 20 \text{ V}$$

24. (d)

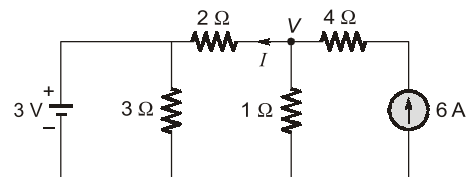

Applying Nodal Analysis,

$$6 = \frac{V - 3}{2} + \frac{V}{1}$$

$$12 = V - 3 + 2V$$

$$\therefore \boxed{V = 5 \text{ V}}$$

$$I = \frac{5 - 3}{2} = 1 \text{ A}$$

25. (a)

$$i_{\text{rms}}^2 = \frac{1}{T} \int_0^T (i_{\text{avg}})^2 \cdot dt$$

$$\therefore i_{\text{avg}} = \left(\frac{9-0}{3-0} \right) \times t = 3t$$


$$\therefore i_{\text{rms}}^2 = \frac{1}{3} \int_0^3 (3t)^2 \times dt$$

$$= \frac{1}{3} \times 9 \times \left[\frac{t^3}{3} \right]_0^3 = 27$$


and $P = i_{\text{rms}}^2 \times R$

$$= 27 \times 10 = 270 \text{ W}$$

26. (a)

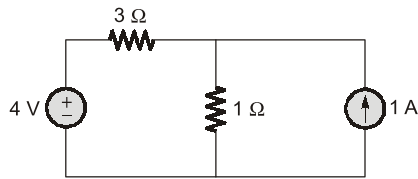


1. By O.C. the 1 A current source.

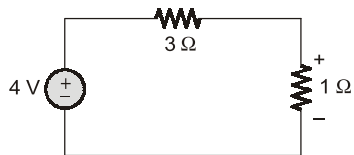

$$V'_{1\Omega} = \frac{4 \times 1}{4} = 1 \text{ V}$$

2. By S.C. the voltage source.

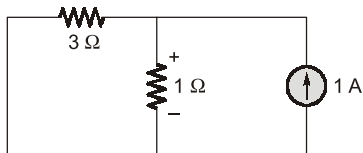


$$V''_{1\Omega} = \frac{3 \times 1}{4} = \frac{3}{4} \text{ V}$$

By superposition theorem,

$$V_{1\Omega}^{\text{total}} = V'_{1\Omega} + V''_{1\Omega} = 1 + \frac{3}{4} = \frac{7}{4} \text{ V}$$

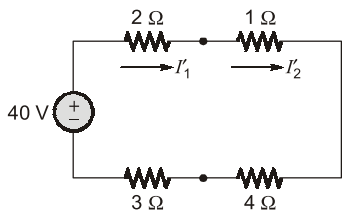
27. (c)

By open circuiting the 4 A current source.



$$I'_1 = I'_2 = 4 \text{ A}$$

By short-circuiting 40 V voltage source.

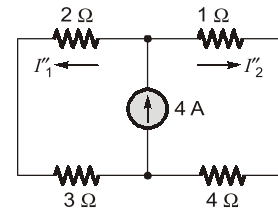


$$I''_1 = I''_2 = 2 \text{ A}$$

By superposition theorem


$$I_1 = I'_1 - I''_1 = 2 \text{ A}$$

$$I_2 = I'_2 - I''_2 = 6 \text{ A}$$

28. (c)

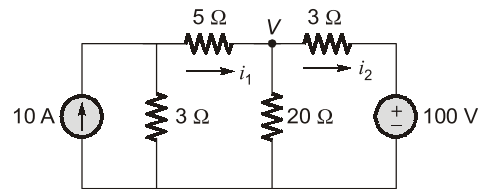

By applying source transformation

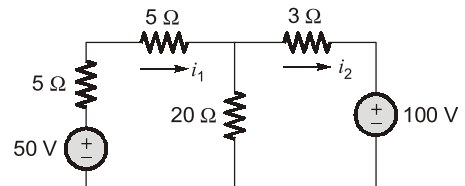

By applying KCL

$$\frac{V - 50}{10} + \frac{V}{20} + \frac{V - 100}{30} = 0$$


$$\frac{11}{60} V = 8.33$$

$$V = 45.45 \text{ V}$$


$$i_1 = \frac{50 - 45.45}{10} = 0.4545 \text{ A}$$

$$i_2 = \frac{45.45 - 100}{10} = -1.818 \text{ A}$$

29. (a)

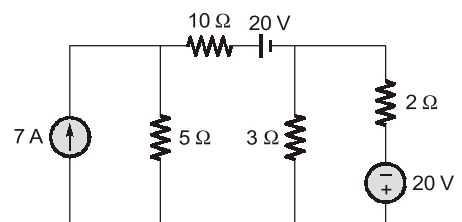

By applying source transformation

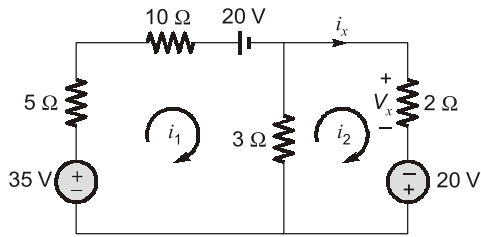

$$35 - 20 = 18i_1 - 3i_2 \quad \dots(i)$$

$$15 = 18i_1 - 3i_2$$

$$20 = 5i_2 - 3i_1 \quad \dots(ii)$$

By equation (i) and (ii),

$$i_1 = 1.66 \text{ A}$$


$$i_2 = 5 \text{ A}$$

so,

$$i_x = 5 \text{ A}$$

$$V_x = 10 \text{ V}$$

30. (d)

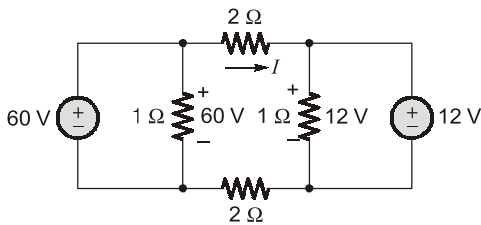


$$-60 + 2I + 12 + 2I = 0$$

$$48 = 4I$$

$$I = 12 \text{ A}$$

31. (a)

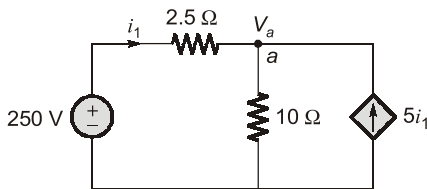

Applying KCL at node a.

$$-i_1 - 5i_1 + \frac{V_a}{10} = 0$$


$$\Rightarrow V_a = 60 i_1$$

$$i_1 = \frac{250 - V_a}{2.5} = \frac{250 - 60 i_1}{2.5}$$

$$\Rightarrow i_1 = \frac{250}{62.5} = 4 \text{ A}$$

Hence, option (a) is correct.

32. (a)

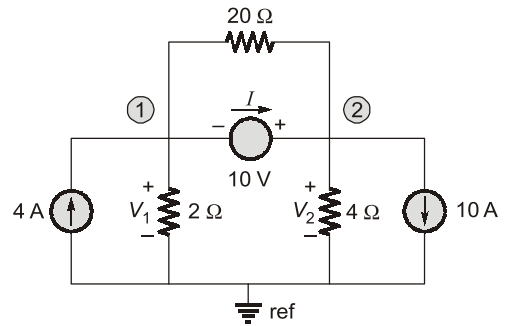

Let current through 10 V source is I .

Applying KCL at node 1,

$$-4 + \frac{V_1}{2} + \frac{V_2 - V_1}{20} + I = 0 \quad \dots(i)$$

Applying KCL at node 2,

$$-I + \frac{V_2}{4} + \frac{V_2 - V_1}{20} + 10 = 0 \quad \dots(ii)$$

Adding equation (i) and (ii) we get,

$$-6 = \frac{V_1}{2} + \frac{V_2}{4}$$

Hence, option (a) is correct.

33. (d)


Applying KCL,

$$\frac{V - 30}{10} - 9 + \frac{V - 36}{20} = 0$$

$$V = 92 \text{ V}$$

Hence, option (d) is correct.

34. (c)

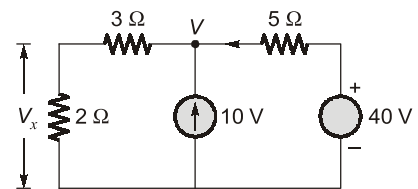

Applying KCL,

$$\frac{V}{5} + \frac{V - 40}{5} - 10 = 0$$

$$V = 45 \text{ V}$$

$$V_x = \frac{V}{5} \times 2 = \frac{45}{5} \times 2 = 18 \text{ V}$$

Hence, option (c) is correct.

35. (c)

$$I_1 = \frac{E}{2R}; I_2 = \frac{E}{4R}; I_3 = \frac{E}{6R}$$


$$I_1 : I_2 : I_3 = \frac{E}{2R} : \frac{E}{4R} : \frac{E}{6R} = 6 : 3 : 2$$

Hence, option (c) is correct.

36. (b)

In any linear, planer network number of independent KVL equations are equal to number of links and KCL equations are $(n - 1)$.

37. (c)

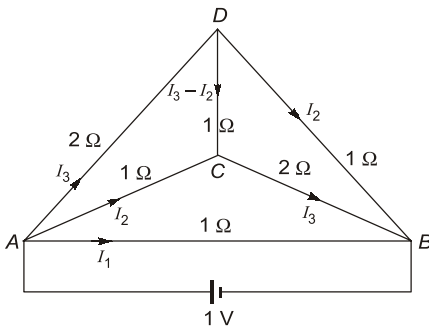

$$1 = 2I_3 + I_2 \quad \dots(i)$$

$$2I_3 + I_3 - I_2 - I_2 = 0 \quad \dots(ii)$$

$$\Rightarrow I_3 = \frac{2}{3} I_2$$

From equation (i),

$$1 = 2 \times \frac{2}{3} I_2 + I_2$$

$$1 = \frac{7}{3} I_2 \Rightarrow I_2 = \frac{3}{7} \text{ A}$$

38. (d)

Let current flowing through the circuit = I

So that, $V_A = 7I$

∴ Using KVL,

$$36 - 15I - 2V_A - V_A = 0$$

$$36 - 15I - 3 \times (7I) = 0 \Rightarrow I = 1 \text{ A}$$

and $V_A = 7V$

∴ Power dissipated in the controlled source

$$= 2 V_A I = 14 \text{ W}$$

39. (d)

$$P = I^2 R = I^2 \times P \frac{l}{A}$$

$$P \propto I^2 \times \frac{l}{d^2}$$

$$\frac{w}{x} = \frac{P_1}{P_2} = \frac{I^2 \times \frac{l}{d^2}}{(3I)^2 \times \frac{l/2}{(2d)^2}}$$

$$= \frac{I^2 \times \frac{l}{d^2}}{9I^2 \times \frac{l}{2} \times \frac{1}{4d^2}} = \frac{8}{9}$$


$$x = \frac{9}{8} \text{ W}$$

40. (a)

Voltage sources of different values cannot be connected in parallel, because voltage across a parallel paths will be equal.

The current sources of different values cannot be connected in series, because current through a series circuit path is same.

41. (d)

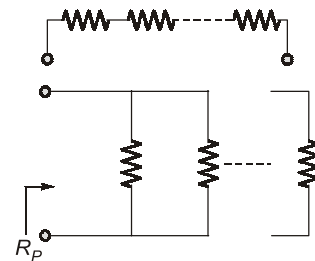

$$R_S = nR$$

$$R_P = \frac{R}{n}$$

$$\Rightarrow n \cdot R = 50$$

$$2 = \frac{R}{n}$$

$$R = \frac{50}{n} \quad \dots(1)$$


$$\Rightarrow R = 2n \quad \dots(2)$$

Multiplying equation (1) and (2),

$$R^2 = \frac{50}{n} \times 2n = 100$$

$$\Rightarrow R = \sqrt{100} = 10 \text{ } \Omega$$

42. (b)

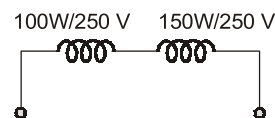


$$R_1 = \frac{V^2}{P_1} = \frac{250 \times 250}{100} = 625 \Omega$$

$$R_2 = \frac{V^2}{P_2} = \frac{250 \times 250}{150} = 416.67 \Omega$$

$$R_{eq} = R_1 + R_2 = 1041.67 \Omega$$

$$P = \frac{V^2}{R_{eq}} = \frac{250 \times 250}{1041.66} \approx 60 \text{ W}$$

43. (b)

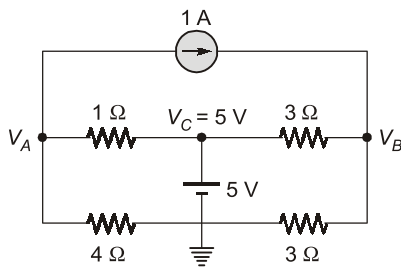

$$V_C - 0 = 5 \Rightarrow V_C = 5 \text{ V}$$

At node A:

$$1 + \frac{V_A - 5}{1} + \frac{V_A}{4} = 0$$

$$5V_A = 16 \Rightarrow V_A = \frac{16}{5} \text{ V}$$


At node B:

$$-1 + \frac{V_B - 5}{3} + \frac{V_B}{3} = 0 \Rightarrow 2V_B = 8$$


$$\therefore V_B = 4 \text{ V}$$

$$\therefore V_{AB} = V_A - V_B = \frac{16}{5} - 4 = -0.8 \text{ V}$$

44. (a)

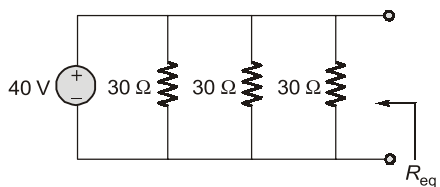

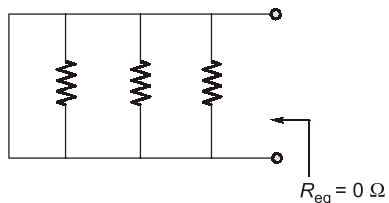Replacing voltage source by a short circuit



45. (b)

Duality means mathematical representation of both the networks should be identical (KVL and KCL).

∴ Loop equations of one network are analogous to the node equations of the other.

46. (b)

Mesh analysis is valid only for planar networks and for its application we apply KVL.

47. (b)

From the given waveforms,

$$\text{slope} = \frac{di}{dt} = \frac{2}{2} = 1 \text{ A/sec}$$


$$v = L \frac{di}{dt}$$

$$2 = L(1)$$

$$L = 2 \text{ H}$$

48. (d)

From the given network,

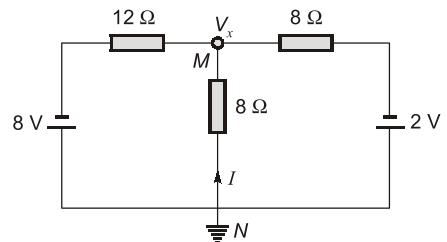

Applying KCL at M,

$$\frac{V_x + 8}{12} + \frac{V_x}{8} + \frac{V_x + 2}{8} = 0$$

$$2V_x + 16 + 3V_x + 3V_x + 6 = 0$$

$$8V_x = -22$$

$$\Rightarrow V_x = -\frac{22}{8} \text{ V}$$

$$I = \frac{0 - V_x}{8} = \frac{0 - \left(-\frac{22}{8}\right)}{8} = \frac{22}{64} \text{ A}$$

$$= 0.343 \text{ A from } N \text{ to } M$$


49. (a)

$$V_{80\Omega} = \frac{25}{80 + 20} \times 80 = \frac{25}{100} \times 80$$

$$= \frac{1}{4} \times 80 = 20 \text{ V}$$

50. (c)

Applying source transformations,

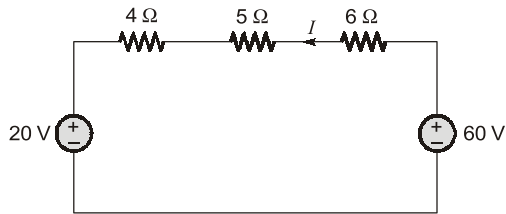

$$I = \frac{60 - 20}{15} = \frac{40}{15} = 2.66 \text{ A}$$

51. (b)

$$V(t) = 10t$$

$$i = \frac{1}{L} \int idt$$

$$i = \frac{1}{L} \int 10t dt$$


$$i = \frac{10t^2}{2L}$$

From plot at $t = 1$ sec $i = 2$ A

$$2 = \frac{(10)}{2L} \Rightarrow L = \frac{10}{4} = 2.54$$

\therefore Inductor of 2.5 H

52. (b)

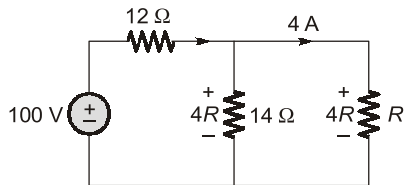

$$I_S = 4 + \frac{4R}{14} \quad \dots(1)$$


KVL: $100 = 12I_S + 4R$

Using (1) equation,

$$100 = 12 \left[4 + \frac{4R}{14} \right] + 4R$$

Solving, $R = 7.008$
 $R \approx 7 \Omega$

53. (c)

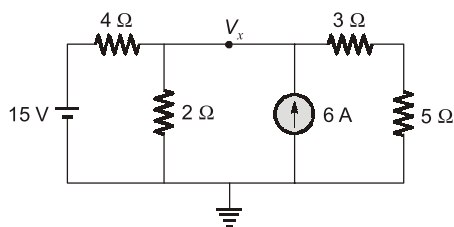


$$\frac{V_x - 15}{4} + \frac{V_x}{2} + \frac{V_x}{8} = 6$$

$$\frac{7}{8} V_x = \frac{39}{4}$$

$$\Rightarrow V_x = \frac{39 \times 2}{7}$$

$$\therefore I = \frac{V_x}{8} = \frac{39 \times 2}{7 \times 8} = \frac{39}{28} \text{ A}$$

54. (b)

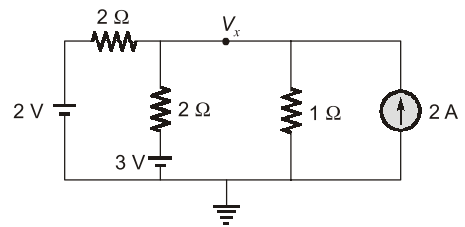

$$\frac{V_x - 2}{2} + \frac{V_x - 3}{2} + \frac{V_x}{1} = 2$$

$$4V_x = 9$$

$$\Rightarrow V_x = \frac{9}{4}$$

$$I = \frac{V_x}{1} = \frac{9}{4} = 2.25 \text{ A}$$

55. (c)

According to reciprocity theorem, the ratio of excitation to response is constant when the position of excitation and response are interchanged.

$$\frac{E_{AB}}{I_{CD}} = \frac{E_{CD}}{I_{AB}}$$

$$\Rightarrow I_{AB} = \frac{E_{CD} \times I_{CD}}{E_{AB}}$$

$$= \frac{100 \times 1}{10} = 10 \text{ A}$$

56. (c)

