

**22** *Years*  
Previous Solved Papers

# ESE 2023

UPSC ENGINEERING SERVICES EXAMINATION

## Preliminary Examination

### ELECTRICAL ENGINEERING

*Objective Solved Papers*

**Volume-II**

- ✓ Topicwise presentation
- ✓ Thoroughly revised & updated

*Also useful for*

State Engineering Services Examinations, Public Sector Examinations  
& Other Competitive Examinations





## **MADE EASY Publications Pvt. Ltd.**

**Corporate Office:** 44-A/4, Kalu Sarai (Near Hauz Khas Metro Station), New Delhi-110016

**Contact:** 9021300500, 8860378007

**E-mail:** infomep@madeeasy.in

**Visit us at:** [www.madeeasypublications.org](http://www.madeeasypublications.org)

### **ESE-2023 : Preliminary Examination Electrical Engineering : Volume-2 Topicwise Objective Solved Questions : (2001-2022)**

© Copyright, by MADE EASY Publications Pvt. Ltd.

All rights are reserved. No part of this publication may be reproduced, stored in or introduced into a retrieval system, or transmitted in any form or by any means (electronic, mechanical, photo-copying, recording or otherwise), without the prior written permission of the above mentioned publisher of this book.

1st Edition : 2008  
2nd Edition : 2009  
3rd Edition : 2010  
4th Edition : 2011  
5th Edition : 2012  
6th Edition : 2013  
7th Edition : 2014  
8th Edition : 2015  
9th Edition : 2016  
10th Edition : 2017  
11th Edition : 2018  
12th Edition : 2019  
13th Edition: 2020  
14th Edition : 2021

**15th Edition: 2022**

MADE EASY PUBLICATIONS PVT. LTD. has taken due care in collecting the data and providing the solutions, before publishing this book. In spite of this, if any inaccuracy or printing error occurs then MADE EASY PUBLICATIONS PVT. LTD owes no responsibility. MADE EASY PUBLICATIONS PVT. LTD will be grateful if you could point out any such error. Your suggestions will be appreciated.

---

© All rights reserved by MADE EASY PUBLICATIONS PVT. LTD. No part of this book may be reproduced or utilized in any form without the written permission from the publisher.

## Director's Message



**B. Singh** (Ex. IES)

Engineering is one of the most chosen graduating field. Taking engineering is usually a matter of interest but this eventually develops into “purpose of being an engineer” when you choose engineering services as a carrier option.

Train goes in tunnel we don't panic but sit still and trust the engineer, even we don't doubt on signalling system, we don't think twice crossing over a bridge reducing our travel time; every engineer has a purpose in his department which when coupled with his unique talent provides service to mankind.

I believe *“the educator must realize in the potential power of his pupil and he must employ all his art, in seeking to bring his pupil to experience this power”*. To support dreams of every engineer and to make efficient use of capabilities of aspirant, MADE EASY team has put sincere efforts in compiling all the previous years' ESE-Pre questions with accurate and detailed explanation. The objective of this book is to facilitate every aspirant in ESE preparation and so, questions are segregated chapterwise and topicwise to enable the student to do topicwise preparation and strengthen the concept as and when they are read.

I would like to acknowledge efforts of entire MADE EASY team who worked hard to solve previous years' papers with accuracy and I hope this book will stand up to the expectations of aspirants and my desire to serve student fraternity by providing best study material and quality guidance will get accomplished.

**B. Singh** (Ex. IES)  
CMD, MADE EASY Group

## Contents

| Sl. | Topic                               | Pages     |
|-----|-------------------------------------|-----------|
| 1.  | Analog Electronics .....            | 1 - 20    |
| 2.  | Digital Electronics .....           | 21 - 47   |
| 3.  | Microprocessors .....               | 48 - 95   |
| 4.  | Communication Systems .....         | 96 - 146  |
| 5.  | Control Systems.....                | 147 - 263 |
| 6.  | Electrical Machines .....           | 264 - 365 |
| 7.  | Power Systems .....                 | 366 - 450 |
| 8.  | Power Electronics & Drives .....    | 451 - 511 |
| 9.  | Systems and Signal Processing ..... | 512 - 532 |
| 10. | Engineering Mathematics.....        | 533 - 557 |



## UNIT

# I

# Analog Electronics

## Syllabus

Operational amplifiers – characteristics and applications, multi-vibrators, sample and hold circuits, basics of filter circuits and applications, simple active filters; basics of linear integrated circuits.

## Contents

| Sl. | Topic   | Page No. |
|-----|---|----------|
| 1.  | Operational Amplifier Characteristics and Application .....               | 2        |
| 2.  | Basics of Filter Circuits, Multivibrators and Simple Active Filters ..... | 13       |

○○○○

# 1

## Operational Amplifier Characteristics and Application

- 1.1 Active load is used in the collector of the differential amplifier of an op-amp to
- increase the output resistance
  - increase the differential gain  $A_d$
  - increase maximum peak to peak output voltage
  - eliminate load resistance from the circuit


[ESE-2001]

- 1.2 The slew rate of an op-amp is  $0.5 \text{ V}/\mu\text{sec}$ . The maximum frequency of a sinusoidal input of  $2 V_{\text{rms}}$  with unity gain that can be handled without excessive distortion is

- 3 kHz
- 30 kHz
- 200 kHz
- 2 MHz

[ESE-2001]

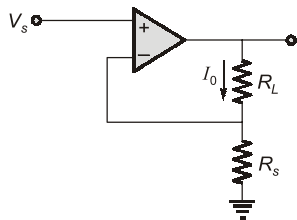
- 1.3 An op-amp is used in the circuit as shown in the below figure. Current  $I_0$  is



- $V_s \times \frac{R_L}{R_s(R_L + R_s)}$
- $\frac{V_s}{R_s}$
- $\frac{V_s}{R_L}$
- $V_s \left( \frac{1}{R_s} + \frac{1}{R_L} \right)$

[ESE-2001]

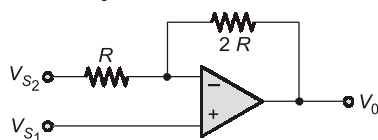
- 1.4 A circuit with op-amp is shown in the below figure. The voltage  $V_0$  is



- $3 V_{s1} - 6 V_{s2}$
- $2 V_{s1} - 3 V_{s2}$
- $2 V_{s1} - 2 V_{s2}$
- $3 V_{s1} - 2 V_{s2}$

[ESE-2001]

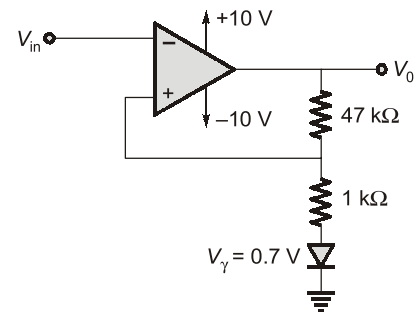
- 1.5 The Schmitt trigger circuit is shown in the below figure. If  $V_{\text{sat}} = \pm 10 \text{ V}$ , the tripping point for the increasing input voltage will be



- 1 V
- 0.893 V
- 0.477 V
- 0.416 V

[ESE-2001]

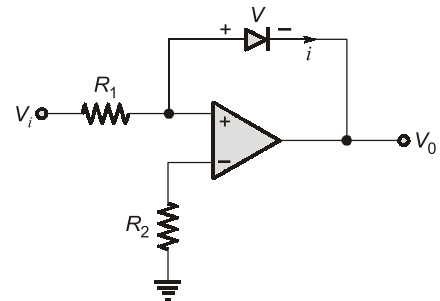
- 1.6 In the op-amp circuit shown below,  $V_i > 0$  and  $i = I_0 e^{V/V_T}$ . The output  $V_0$  will be proportional to



- $\sqrt{V_i}$
- $V_i$
- $e^{kV_i}$
- $\ln(kV_i)$

[ESE-2002]

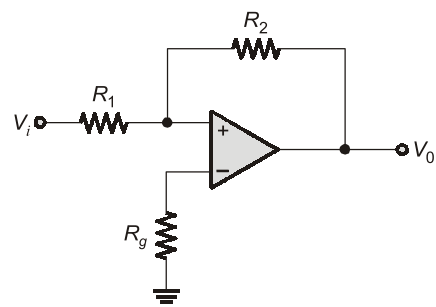- 1.7 In the inverting op-amp circuit shown below, the resistance  $R_g$  is chosen as  $R_1 \parallel R_2$  in order to




- (a) increase gain
- (b) reduce offset voltage
- (c) reduce offset current
- (d) increase CMRR

[ESE-2002]

- 1.8 An op-amp has a differential gain of  $10^3$  and a CMRR of 100. The output voltage of the op-amp with inputs of  $120 \mu\text{V}$  and  $80 \mu\text{V}$  will be
- (a) 26 mV
  - (b) 41 mV
  - (c) 100 mV
  - (d) 200 mV

[ESE-2003]

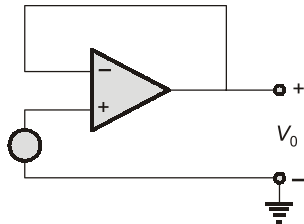- 1.9 Consider the following statements with reference to an ideal voltage follower circuit as shown below:




1. Unity gain and no phase shift
2. Infinite gain and  $180^\circ$  phase shift
3. Very high input impedance and very low output impedance
4. It is a buffer amplifier

Which of these statements are correct?

- (a) 1 and 3
- (b) 2 and 4
- (c) 1, 3 and 4
- (d) 1, 2, 3 and 4

[ESE-2003]

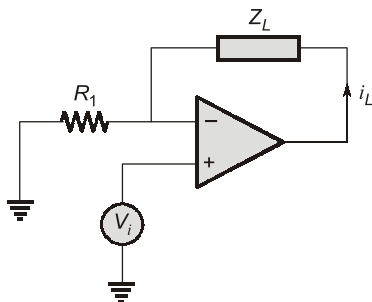
- 1.10 In the op-amp circuit as shown below, the current  $i_L$  is



- (a)  $\frac{V_i}{Z_L}$
- (b)  $\frac{V_i}{Z_L \parallel R_1}$
- (c)  $\frac{V_i}{R_1}$
- (d)  $V_i(R_1 + Z_L)$

[ESE-2003]

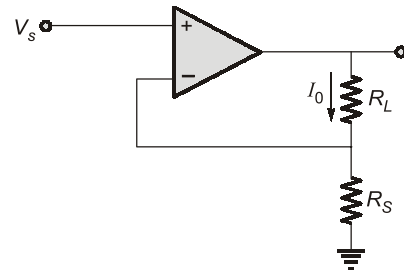
- 1.11 Which one of the following is the correct expression for the current  $I_0$ ?



- (a)  $\frac{V_S \cdot R_L}{R_S(R_L + R_S)}$
- (b)  $\frac{V_S}{R_S}$
- (c)  $\frac{V_S}{R_L}$
- (d)  $V_S \left( \frac{1}{R_L} + \frac{1}{R_S} \right)$

[ESE-2004]


- 1.12 Consider the following circuit:

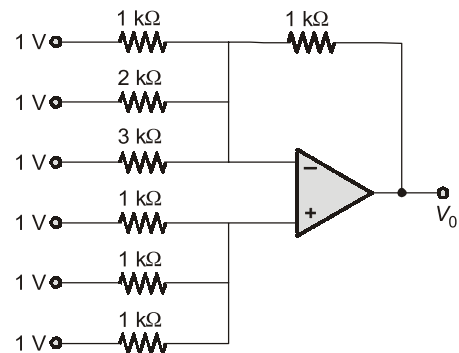What is the output voltage  $V_o$  in the above circuit?

- (a) 9.5 V
- (b) 3 V
- (c) 32.2 V
- (d) 1 V

[ESE-2004]

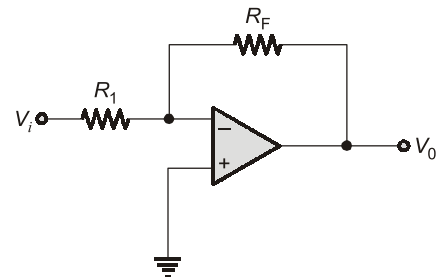
- 1.13 For the operational amplifier circuit shown in the figure below, what is the maximum possible value of  $R_1$ , if the voltage gain required is between  $-10$  and  $-25$ ? (The upper limit on  $R_F$  is  $1 \text{ M}\Omega$ )



- (a) Infinity
- (b)  $1 \text{ M}\Omega$
- (c)  $100 \text{ k}\Omega$
- (d)  $40 \text{ k}\Omega$

[ESE-2007]

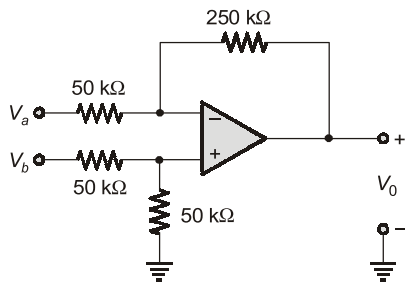1.14 What is the output voltage  $V_o$  of the given circuit?



- (a)  $-5 V_a + 2.5 V_b$  (b)  $-5 V_a + 3 V_b$   
(c)  $-2.5 V_a + 2.5 V_b$  (d)  $-2.5 V_a + 3 V_b$

[ESE-2008]


1.15 **Assertion (A):** It is not possible to design a current source using operational amplifier.




**Reason (R):** Operational amplifier is a voltage-controlled voltage source.


- (a) Both A and R are true and R is the correct explanation of A  
(b) Both A and R are true but R is not the correct explanation of A  
(c) A is true but R is false  
(d) A is false but R is true

[ESE-2008]

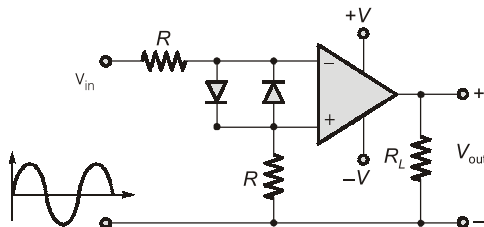1.16 For the below circuit what will be the output for the sinusoidal input shown at the input terminal?





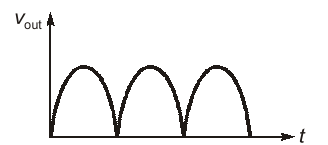
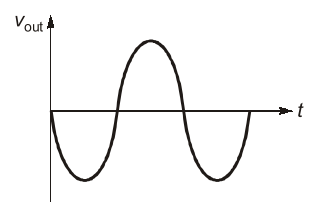
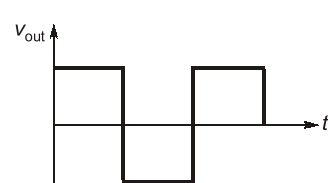
- (a)   
(b)   
(c) 

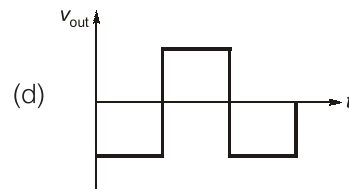

[ESE-2009]

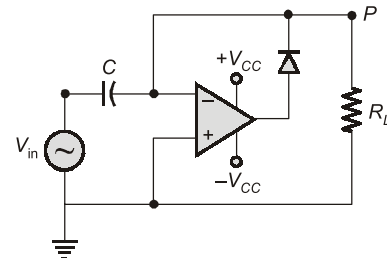1.17 For the given sinusoidal input to the circuit as shown in the figure below, the voltage waveform at point P of the clamper circuit is



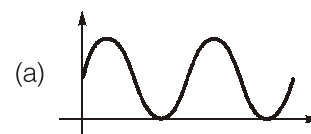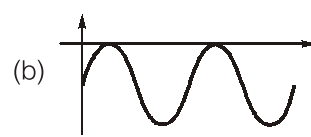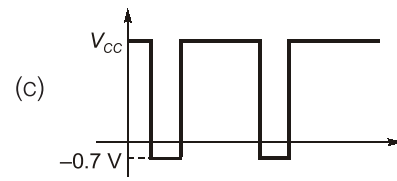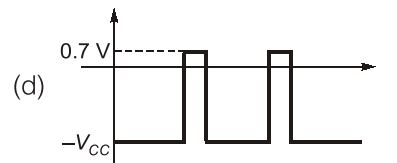- (a)   
(b)   
(c)   
(d) 


[ESE-2010]

1.18 **Assertion (A) :** In normal operation, the non-inverting and inverting input terminals of an operational amplifier are at almost same potential.  
**Reason (R) :** The two terminals are connected together.

- (a) Both A and R are true and R is the correct explanation of A  
(b) Both A and R are true but R is NOT the correct explanation of A  
(c) A is true but R is false  
(d) A is false but R is true

[ESE-2010]


1.19 The circuit shown is

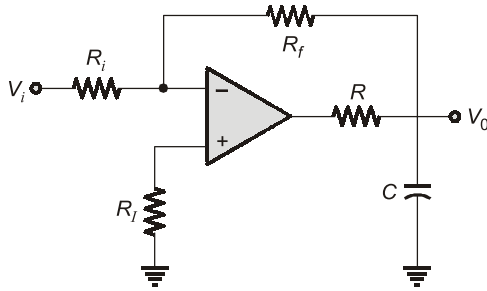

- (a) A low pass filter
- (b) A clamper
- (c) A lag compensated inverting amplifier
- (d) A narrow band video amplifier

[ESE-2011]


1.20 The circuit shown is

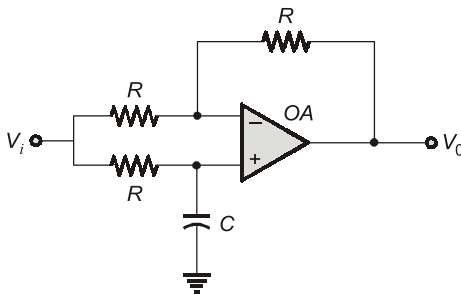

- (a) A low-pass filter
- (b) A high-pass filter
- (c) A comparator
- (d) An all-pass filter

[ESE-2011]

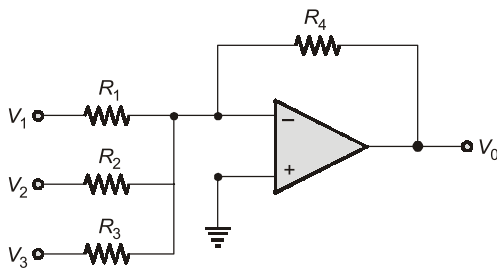1.21 In the given circuit, the magnitude of the output voltage.



If  $|V_o| = 3V_1 + 2V_2 + 7V_3$ , then the values of  $R_1$ ,  $R_2$ ,  $R_3$  and  $R_4$  are:

- (a) 3 k $\Omega$ , 2 k $\Omega$ , 7 k $\Omega$  and 1 k $\Omega$
- (b)  $\frac{1}{4}$  k $\Omega$ ,  $\frac{1}{6}$  k $\Omega$ ,  $\frac{7}{12}$  k $\Omega$  and 12 k $\Omega$
- (c) 4 k $\Omega$ , 6 k $\Omega$ ,  $\frac{12}{7}$  k $\Omega$  and 12 k $\Omega$
- (d)  $\frac{1}{3}$  k $\Omega$ ,  $\frac{1}{2}$  k $\Omega$ ,  $\frac{1}{7}$  k $\Omega$  and 12 k $\Omega$

[ESE-2011]

1.22 Virtual ground property of operational amplifier indicates that

- (a) inverting and non-inverting terminals are connected to ground.
- (b) inverting and non-inverting terminals are at the same potential.
- (c) system is at rest.
- (d) any one terminal is connected to ground.

[ESE-2012]

1.23 A comparator circuit is used to

- (a) mark the instant when an arbitrary waveform attains some reference level.
- (b) switch off a circuit when output becomes zero.
- (c) switch on and off a circuit alternately at a particular rate.
- (d) mark the instant when the input voltage becomes constant.

[ESE-2012]

1.24 A signal may have frequency components which lie in the range of 0.001 Hz to 10 Hz. Which one of the following types of couplings should be chosen in a multistage amplifier designed to amplify the signal?

- (a) RC coupling
- (b) Direct coupling
- (c) Transformer coupling
- (d) Double tuned transformer

[ESE-2013]

1.25 An operational amplifier is connected in voltage follower configuration. Input given to this is  $3 \sin 10^3 \pi t$ . Compute the slew rate of operational amplifier.

- (a)  $6\pi \times 10^{-3}$  V/ $\mu$ sec
- (b)  $3\pi \times 10^{-3}$  V/ $\mu$ sec
- (c)  $1.5\pi \times 10^{-3}$  V/ $\mu$ sec
- (d)  $\pi \times 10^{-3}$  V/ $\mu$ sec

[ESE-2013]

1.26 An OP-AMP has a common mode gain of 0.01 and a differential mode gain of  $10^5$ . Its common mode rejection ratio would be

- (a)  $10^{-7}$
- (b)  $10^{-3}$
- (c)  $10^3$
- (d)  $10^7$

[ESE-2013]

1.27 An OP-AMP has a slew rate of 5 V/ $\mu$ s. The largest sine wave output voltage possible at a frequency of 1 MHz is

- (a)  $10\pi V$  (b)  $5 V$   
 (c)  $\frac{5}{\pi} V$  (d)  $\frac{5}{2\pi} V$  [ESE-2013]

1.28 The gain and distortion of an amplifier are respectively 150 and 5%. When used with a 10% negative feedback the % distortion would be

- (a)  $\frac{5}{16}$  (b)  $\frac{9}{16}$   
 (c) 6 (d) 8 [ESE-2014]

1.29 A two stage amplifier with negative feedback  
 (a) can become unstable for larger values of  $\beta$ .  
 (b) becomes unstable at high and very low frequencies if  $A$  is very large.  
 (c) becomes unstable when the pole frequencies become complex.  
 (d) is always stable. [ESE-2014]


1.30 **Statement (I)** : An ideal op-amp should have infinite bandwidth.

**Statement (II)** : An ideal op amp should have infinite input resistance and zero output resistance.

- (a) Both Statement (I) and Statement (II) are individually true and Statement (II) is the correct explanation of Statement (I).  
 (b) Both Statement (I) and Statement (II) are individually true but Statement (II) is not the correct explanation of Statement (I).  
 (c) Statement (I) is true but Statement (II) is false.  
 (d) Statement (I) is false but Statement (II) is true. [ESE-2015]

1.31 Three identical amplifiers each having a voltage gain of 50 are cascaded. The open loop voltage gain of the combined amplifier is  
 (a) 71 dB (b) 82 dB  
 (c) 91 dB (d) 102 dB [ESE-2016]

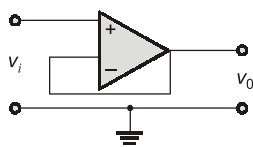1.32 The operational amplifier circuit shown in figure having a voltage gain of unity has



- (a) high input impedance and high output impedance.  
 (b) high input impedance and low output impedance.

- (c) low input impedance and low output impedance.  
 (d) low input impedance and high output impedance.

[ESE-2016]

1.33 An operational amplifier has a slew rate of  $2 V/\mu \text{ sec}$ . If the peak output is 12 V, what will be the power bandwidth?

- (a) 36.5 kHz (b) 26.5 kHz  
 (c) 22.5 kHz (d) 12.5 kHz

[ESE-2016]

1.34 A voltage follower is used as

1. An isolation amplifier
2. A buffer amplifier

Which of the above statements is/are correct?

- (a) 1 only (b) 2 only  
 (c) Both 1 and 2 (d) Neither 1 nor 2


[ESE-2016]

1.35 How fast can the output of an Op-amp change by 10 V, if its slew rate is  $1 V/\mu \text{s}$ ?

- (a)  $5 \mu \text{s}$  (b)  $10 \mu \text{s}$   
 (c)  $15 \mu \text{s}$  (d)  $20 \mu \text{s}$

[ESE-2017]

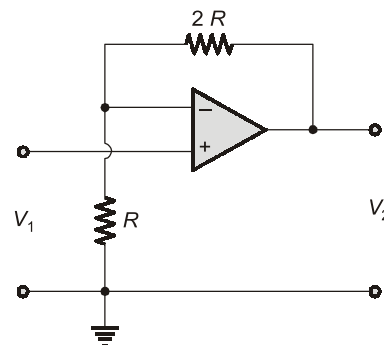1.36 An ideal operational amplifier is connected as shown in figure. What is the output voltage  $V_2$ ?



- (a)  $3V_1$  (b)  $2V_1$   
 (c)  $1V_1$  (d)  $\frac{V_1}{3}$

[ESE-2018]

1.37 For an op-amp having a slew rate of  $2 V/\mu \text{s}$ , if the input signal varies by 0.5 V in  $10 \mu \text{s}$ , the maximum closed-loop voltage gain will be

- (a) 50 (b) 40  
 (c) 22 (d) 20

[ESE-2019]

- 1.38** In order to balance the offset voltage of an operational amplifier, a small DC voltage is applied to input terminals where the connection is  
 (a) Series with both inverting as well as non-inverting input  
 (b) Series with non-inverting input  
 (c) Shunt with inverting input  
 (d) Shunt with non-inverting input  
**[ESE-2020]**
- 1.39** Multi-vibrator circuit that remains in stable state until a triggering signal causes transition to quasistable state and returns to stable state after certain time is called  
 (a) Astable multivibrator  
 (b) Monostable multivibrator  
 (c) Bistable multivibrator  
 (d) Unstable multivibrator  
**[ESE-2020]**
- 1.40** What is the output voltage for an integrator when input is a step voltage for  $0 \leq t \leq 2$ ,  $R_1 C_F = 3$  sec and  $V_{in} = 6$  V?  
 (a)  $-4$  V (b)  $-6$  V  
 (c)  $-8$  V (d)  $-10$  V  
**[ESE-2021]**
- 1.41** Which one of the following statements is correct for the active filter using op-amps?  
 (a) High frequency response is limited by the gain bandwidth product and slew-rate of the op-amp.  
 (b) Op-amps are not providing any gain.  
 (c) Due to the low input impedance of the op-amp, large value resistors can be used.  
 (d) High frequency active filters are not more expensive than passive filters.  
**[ESE-2021]**
- 1.42** Which one of the following consists of op-amp in inverting mode and network of R-C components, and the op-amp being in inverting mode it serves two purpose of amplifying and at its output  $180^\circ$  shifted phase is obtained?  
 (a) Wien's bridge oscillator  
 (b) R-C phase-shift oscillator  
 (c) Triangular wave generator  
 (d) Charging capacitor  
**[ESE-2022]**

■■■■

### Answers Operational Amplifier Characteristics and Application

- 1.1 (b) 1.2 (b) 1.3 (b) 1.4 (d) 1.5 (b) 1.6 (d) 1.7 (c) 1.8 (b) 1.9 (c)  
 1.10 (c) 1.11 (b) 1.12 (d) 1.13 (c) 1.14 (b) 1.15 (d) 1.16 (d) 1.17 (a) 1.18 (c)  
 1.19 (a) 1.20 (d) 1.21 (c) 1.22 (b) 1.23 (a) 1.24 (b) 1.25 (b) 1.26 (d) 1.27 (d)  
 1.28 (a) 1.29 (d) 1.30 (b) 1.31 (d) 1.32 (b) 1.33 (b) 1.34 (c) 1.35 (b) 1.36 (a)  
 1.37 (b) 1.38 (b) 1.39 (b) 1.40 (a) 1.41 (a) 1.42 (b)

### Explanations Operational Amplifier Characteristics and Application

- 1.1 (b)**  
 Active load is used to increase differential gain  $A_{d'}$

- 1.2 (b)**  
 For a sinusoidal signal of general form  $v_o = k \sin(2\pi ft)$  the maximum voltage rate of change can be shown to be

$$\Rightarrow \left( \frac{dv_o}{dt} \right)_{\text{maximum}} = 2\pi f k (\text{V/s})$$

To prevent distortion at the output the rate of change must also be less than the slew rate, that is,

$$2\pi f k \leq SR$$


$$\therefore f \leq \frac{SR}{2\pi k} \text{ Hz}$$

voltage gain = 1

For  $k = 2\sqrt{2}$  V and  $SR = 0.5$  V/ $\mu$ s

$$\therefore \text{Input } f_{\text{max}} = \frac{0.5}{10^{-6} \times 2 \times \pi \times 2 \times \sqrt{2}} = 28.13 \text{ kHz} \approx 30 \text{ kHz}$$

1.3 (b)

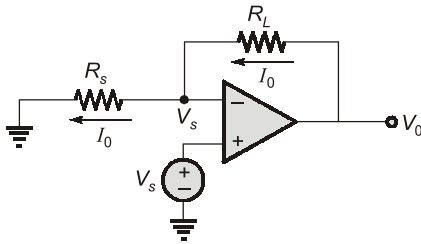

According to virtual short theory,

$$V^+ = V^-$$

$$I_0 = \frac{V_s}{R_s} \quad [\text{Non-inverting amplifier}]$$

1.4 (d)

Using superposition

$$\text{For } V_{S1}, V_{01} = \left(1 + \frac{2R}{R}\right) V_{S1}$$

$$\text{For } V_{S2}, V_{02} = -\frac{2R}{R} V_{S2}$$

$$\therefore V_0, V_{01} + V_{02} = 3V_{S1} - 2V_{S2}$$

1.5 (b)

For the increasing input voltage; ( $V_0 = +10$  V) $\therefore$  Triggering voltage using superposition theorem

$$= \frac{47}{48} \times 0.7 + \frac{1}{48} \times 10 = 0.893 \text{ V}$$

1.6 (d)

We know that,

$$V_1 = V_2$$

$$\therefore V_2 = 0$$

$$\therefore V_1 = 0$$

So, net voltage across diode  $D$ 

$$V = V_1 - V_0 \\ = 0 - V_0 = -V_0$$

So, current  $i$  through diode  $D$  (when  $V_i > 0$ )

$$i = I_0 [e^{V/\eta V_T} - 1] \quad \dots(i)$$

Where  $I_0$  = reverse saturation current. $V_T$  = Voltage equivalent of temperature

Now current,

$$i_1 = \frac{V_i - V_1}{R} = \frac{V_i}{R}$$

 $\therefore$  Current inside the op-amp is zero

$$(\because R_i \rightarrow \infty)$$

$$\therefore i = i_1$$

$$\text{i.e. } I_0 [e^{V/\eta V_T} - 1] = \frac{V_i}{R}$$

$$e^{V/\eta V_T} - 1 = \frac{V_i}{I_0 R}$$

$$e^{V/\eta V_T} = 1 + \frac{V_i}{I_0 R}$$

$$V = \eta V_T \ln \left( 1 + \frac{V_i}{I_0 R} \right)$$

$$\therefore I_0 \ll 0$$

$$\text{So, } \frac{V_i}{I_0 R} \gg 1$$

So, we can write,

$$V = \eta V_T \ln \left( \frac{V_i}{I_0 R} \right)$$

$$-V_0 = \eta V_T \ln \frac{V_i}{I_0 R}$$

$$V_0 = -\eta V_T \ln \frac{V_i}{I_0 R}$$

$$V_0 = -\eta V_T \ln k V_i \quad \text{where } k = (I_0 R)^{-1}$$

$$V_0 \propto \ln k V_i$$

1.7 (c)

$R_g$  is chosen such that it is equal to impedance seen from the  $-ve$  terminal by replacing all the sources by their internal impedances and this is done for reducing the effect of offset current.

1.8 (b)

$$V_o = A_d V_d + A_c V_c \quad \text{and} \quad \text{CMRR} = \frac{A_d}{A_c}$$

$$V_o = A_d V_d \left( 1 + \frac{1}{\text{CMRR}} \frac{V_c}{V_d} \right)$$


$$V_c = \frac{1}{2} (120 + 80) = 100 \times 10^{-6} \text{ V}$$

$$V_d = 120 - 80 = 40 \times 10^{-6} \text{ V}$$

$$\therefore V_o = 10^3 \times 40 \times 10^{-6} \times \left( 1 + \frac{1}{100} \times \frac{10^{-4}}{40 \times 10^{-6}} \right)$$

$$\therefore V_o = 41 \text{ mV}$$

1.9 (c)

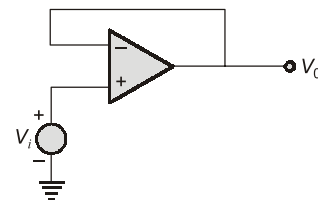

This is non-inverting amplifier with  $R_f = R_2 = 0$ ,  $R_1 \rightarrow \infty$ .

We know that gain,

$$A_V = (1 + R_2/R_1)$$

$$A_V = 1$$


$\therefore R_2 = 0, R_1 \rightarrow \infty$ .

Now this is a voltage series feedback configuration so, input impedance further increases as compare to open loop configuration and output impedance decreases (due to shunt connection at output) compare to open loop configuration.

$\therefore$  In open loop configuration input impedance is high and output impedance is low so in this configuration it becomes very high and very low respectively.

$\therefore$  It passes the input as it is ( $\because A_V = 1$ ) and with some delay so it act as buffer.

1.10 (c)

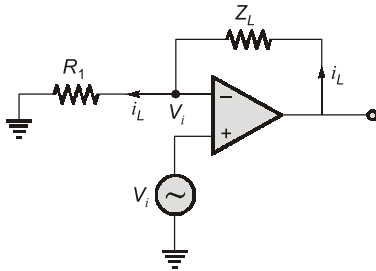

According to virtual short theory,

$$V^+ = V^-$$

$$i_L = \frac{V_i}{R_1}$$

1.11 (b)

$$I_0 = \frac{V_S}{R_S}$$

1.12 (d)

$V_{01} \rightarrow$  output voltage due to voltages at inverting terminal assuming voltages at non-inverting terminals = 0.


$$\frac{1}{3k} + \frac{1}{2k} + \frac{1}{1k} = \frac{0 - V_{01}}{1k}$$

$$V_{01} = -\frac{1}{6}[2+3+6]$$


$$V_{01} = -\frac{11}{6}V$$

$V_{02} \rightarrow$  output voltage due to voltages at non-inverting terminals keeping voltages at inverting terminals zero.

So,

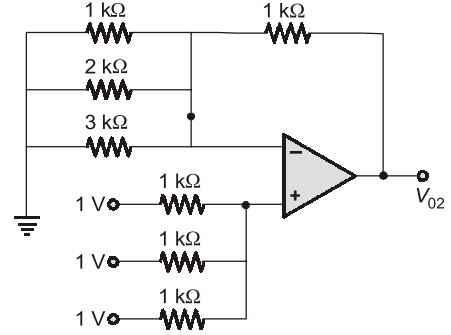

Equivalent circuit will be

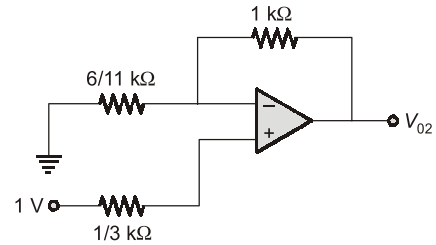

So output,

$$V_{02} = 1V \times \left[ 1 + \frac{R_2}{R_1} \right] = 1V \times \left[ 1 + \frac{1}{6/11} \right] = \frac{17}{6}V$$

$\therefore$  Net output according to superposition theorem

$$\begin{aligned} V_0 &= V_{01} + V_{02} \\ &= -\frac{11}{6} + \frac{17}{6} = \frac{6}{6} = 1V \end{aligned}$$

1.13 (c)

$$\text{Gain, } A_V = -\frac{R_f}{R_1}$$

$$\therefore R_1 = -\frac{R_f}{A_V}$$

$$\text{So, } R_1 \text{ will be } \propto \frac{1}{A_V}$$

So lesser the gain higher will be  $R_1$

So for  $A_V = -10$

$\rightarrow R_1$  will be maximum

$$\begin{aligned} \therefore R_1 &= \frac{-R_f}{-10} = \frac{R_f}{10} = \frac{1 \times 10^6}{10} = 10^5 \Omega \\ R_1 &= 100 \text{ k}\Omega \end{aligned}$$

1.14 (b)

Output due to voltage at inverting terminal keeping voltage at non-inverting terminal zero is

$$V_{01} = V_a \times \left( -\frac{R_f}{R} \right) = V_a \left( -\frac{250}{50} \right)$$

$$V_{0C} = -5 V_a$$

Output voltage due voltage at non-inverting terminal keeping voltage at inverting terminal zero,

$$\begin{aligned} V_{02} &= V_b \times \frac{50}{(50+50)} \times \left( 1 + \frac{R_f}{R} \right) \\ &= V_b \times \frac{1}{2} \left( 1 + \frac{250}{50} \right) \end{aligned}$$


$$V_{02} = 3V_b$$

So according to superposition theorem, net output voltage,

$$V_0 = V_{01} + V_{02}$$

$$V_0 = -5V_a + 3V_b$$

1.15 (d)

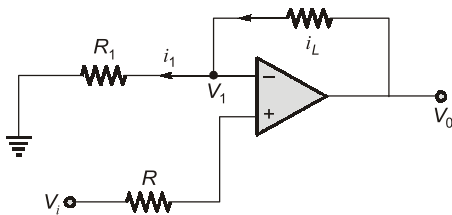

Here,  $V_1 = V_i$   
due to virtual ground concept

$$\therefore i_1 = \frac{V_1}{R_1} = \frac{V_i}{R_1}$$

$\therefore$  current inside the op-amp = 0 ( $R_i = \infty$ )

$$\therefore i_L = i_1 = \frac{V_i}{R}$$


Independent of load so work as current source.  
Statement (A) is incorrect.

1.16 (d)

Output will be at its saturated values and it is having a phase difference of  $(-180^\circ)$

1.17 (a)

It is a clamper circuit,

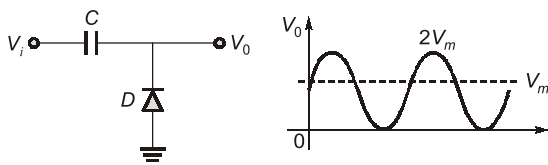

1.18 (c)

Correct reason is virtual grounding.

1.19 (a)

For low frequency  $Z_C = \frac{1}{j\omega C} \Rightarrow \infty$

$$\text{So, output } V_0 = -\frac{R_f}{R_1} V_i$$

we will get the output for high frequency

$$Z_C = \frac{1}{j\omega C} \Rightarrow 0$$

$\therefore$  Output  $V_0 \cong 0$

So cut the high frequency.

So it is a low pass filter.

1.20 (d)

It is all pass filter,

$$\text{Transfer function} = \frac{1 - j2\pi fRC}{1 + j2\pi fRC}$$

1.21 (c)

$$\begin{aligned} V_0 &= -\frac{R_4}{R_1} V_1 + \left( -\frac{R_4}{R_2} \right) V_2 + \left( -\frac{R_4}{R_3} \right) V_3 \\ &= -\left[ \frac{R_4}{R_1} V_1 + \frac{R_4}{R_2} V_2 + \frac{R_4}{R_3} V_3 \right] \end{aligned}$$

$$|V_0| = \frac{R_4}{R_1} V_1 + \frac{R_4}{R_2} V_2 + \frac{R_4}{R_3} V_3$$

Given,

$$|V_0| = 3V_1 + 2V_2 + 7V_3$$

$$\therefore \frac{R_4}{R_1} = 3, \frac{R_4}{R_2} = 2, \frac{R_4}{R_3} = 7$$

$$\therefore R_1 : R_2 : R_3 : R_4$$

$$\frac{1}{3} : \frac{1}{2} : \frac{1}{7} : 1$$

Multiplying by 12 we get,

$$\frac{12}{3} : \frac{12}{2} : \frac{12}{7} : 12$$

$$4 \text{ k}\Omega : 6 \text{ k}\Omega : \frac{12}{7} \text{ k}\Omega : 12 \text{ k}\Omega$$

1.22 (b)

In virtual ground property the potential of inverting and non-inverting end are same.