

POSTAL Book Package

2022

Electrical Engineering

Objective Practice Sets

Analog Electronics

Contents

| Sl. | Topic | Page No. |
|-----|--|----------|
| 1. | Basics of Semiconductor Diodes | 2 |
| 2. | Bipolar Junction Transistors and Characteristics | 29 |
| 3. | Junction and Field Effect Transistors | 44 |
| 4. | Transistor Amplifiers and Frequency Response | 55 |
| 5. | Feedback Amplifiers | 67 |
| 6. | Oscillators and Multivibrators | 73 |
| 7. | Operational Amplifiers | 80 |
| 8. | Miscellaneous | 95 |



MADE EASY
Publications


Note: This book contains copyright subject matter to MADE EASY Publications, New Delhi. No part of this book may be reproduced, stored in a retrieval system or transmitted in any form or by any means. Violators are liable to be legally prosecuted.

Basics of Semiconductor Diodes

MCQ and NAT Questions




- Q.1** A diode whose terminal characteristics are related as $i_D = I_s e^{V/V_T}$, where I_s is the reverse saturation current and V_T is thermal voltage ($V_T = 25$ mV), is biased at $I_D = 4$ mA. Its dynamic resistance is
- (a) 12.5Ω (b) 50Ω
(c) 6.25Ω (d) 25Ω

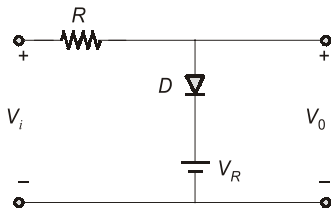- Q.2** In the circuit shown below the input V_i has positive and negative swings. V_o is the output.




- (a) $V_o = 0$ for negative V_i
(b) $V_o = V_R$ for positive V_i
(c) $V_o = V_R$ for $V_i > V_R$
(d) $V_o = V_R$ for all V_i

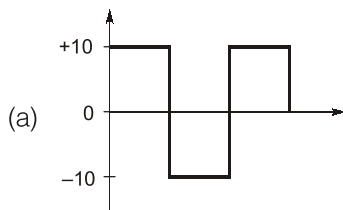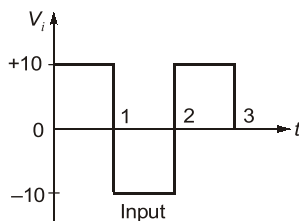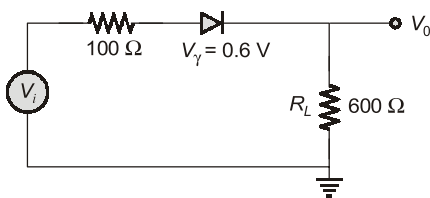
- Q.3** In the circuit shown below, if the input voltage V_i is as shown below then the corresponding output waveform will be



(a)


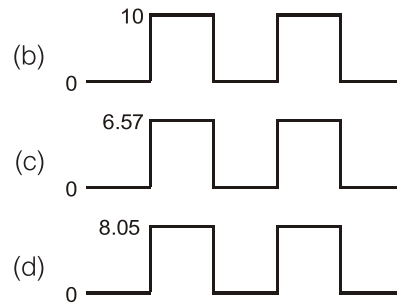


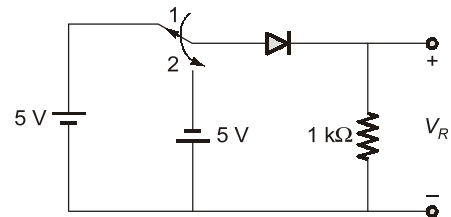- Q.4** In the circuit shown below, the switch was connected to position 1 at $t < 0$ and at $t = 0$, it is changed to position 2. Assume that the diode has zero voltage drop and a storage time t_s . For $0 < t \leq t_s$, V_R is given by (all in Volts)




- (a) $V_R = -5$ (b) $V_R = 0$
(c) $0 \leq V_R < 5$ (d) $-5 < V_R < 0$

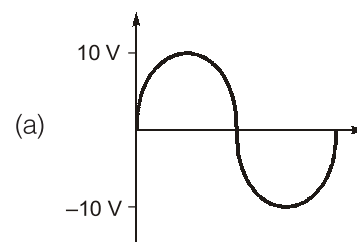
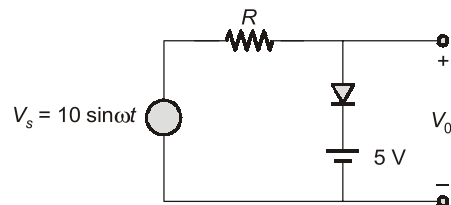
- Q.5** For the circuit shown below assuming ideal diode, the output waveform V_o is




(a)

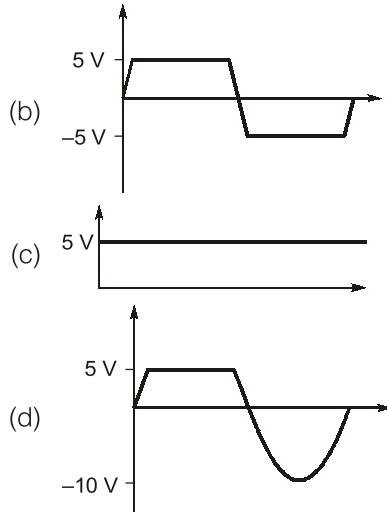

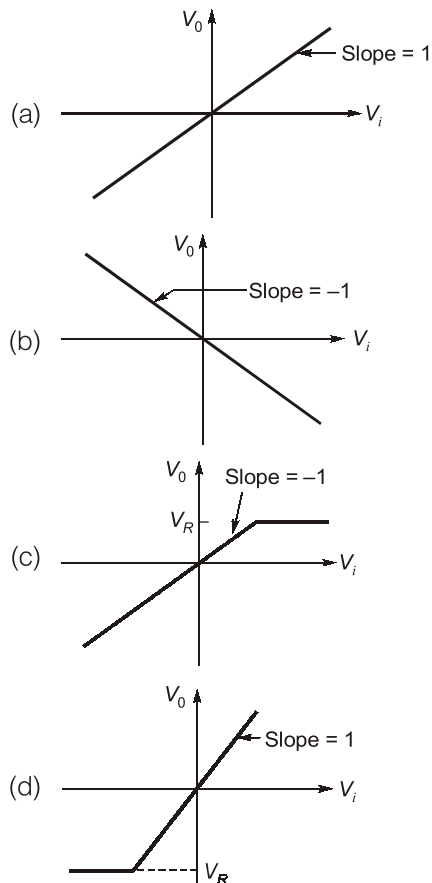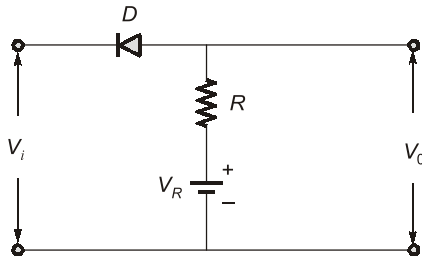Q.6 The transfer characteristic of the network shown below is represented as




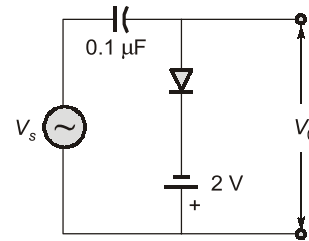Q.7 For an input of $V_s = 5 \sin \omega t$, (assuming ideal diode), circuit shown below will behave as a




- (a) clipper, sine wave clipped at -2 V
- (b) clamper, sine wave clamped at -2 V
- (c) clamper, sine wave clamped at zero volt
- (d) clipper, sine wave clipped at 2 V

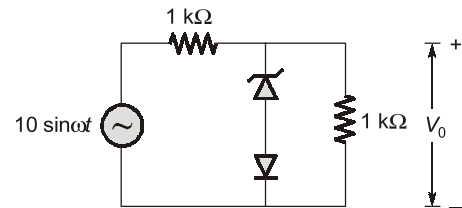Q.8 The cut-in voltage of both zener diode D_z and D shown in figure is 0.65 V , while breakdown voltage of the zener is 3 V . Diode is considered to be ideal. The value of peak output voltage V_o .




- (a) 3 V in the positive half cycle and 0.65 V in the negative half cycle.
- (b) 3.65 V in the positive half cycle and -5 V in the negative half cycle.
- (c) 3 V in positive half cycle and -5 V in the negative half cycle
- (d) -3.65 V in positive half cycle and 5 V in the negative half cycle

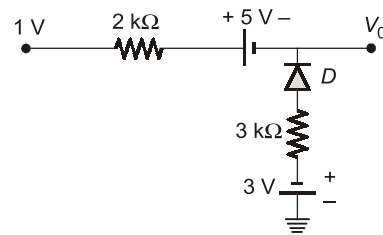Q.9 What is the output voltage V_o for the circuit shown below assuming an ideal diode?




- (a) $-\frac{18}{5} \text{ V}$
- (b) $\frac{18}{5} \text{ V}$
- (c) $-\frac{13}{5} \text{ V}$
- (d) $\frac{13}{5} \text{ V}$

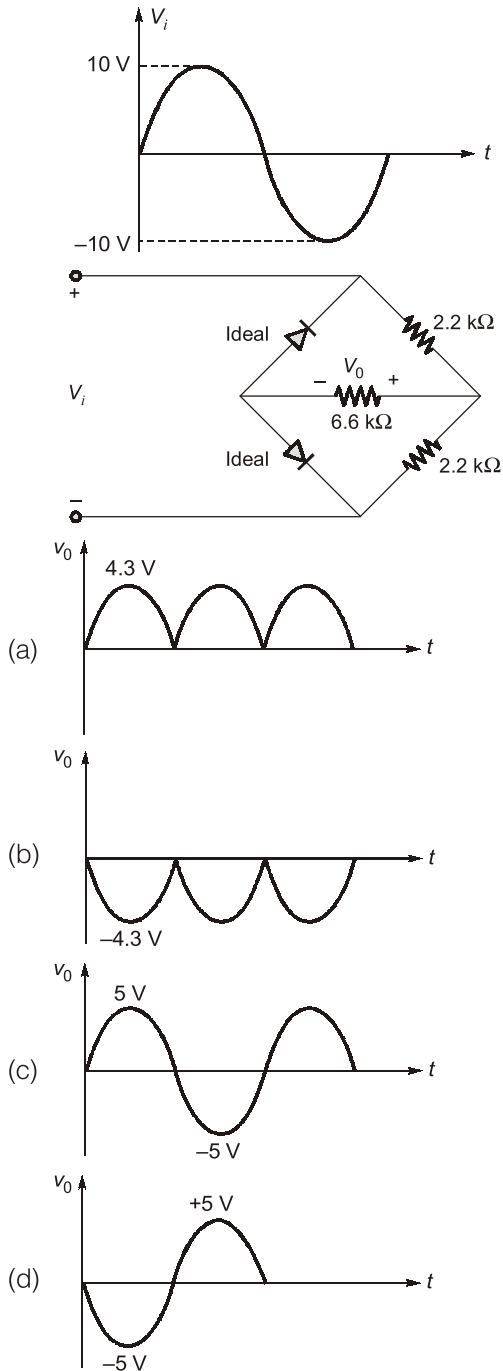
Q.10 The correct waveform for output (V_o) for below network is



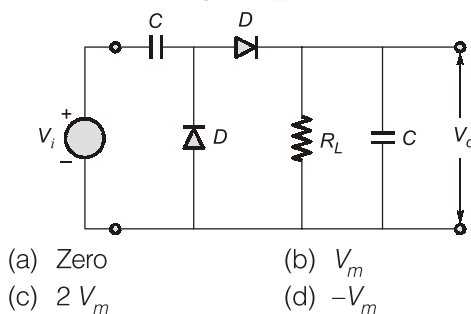Q.11 Consider the below circuit, for $V_i = V_m \sin \omega t$, the output voltage V_o for $R_L \rightarrow \infty$ will be



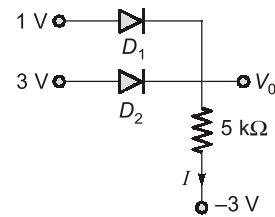
Q.12 Consider the circuit shown in the figure below:



If diode D_1 and D_2 are made up of same material with the cut-in voltage $V_\gamma = 0.7$ V, then the value of current I is equal to


- (a) 0.46 mA (b) 0.99 mA
(c) 0.59 mA (d) 1.06 mA

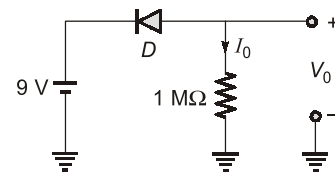Q.13 Consider the diode circuit shown in the figure below:




The diode in the circuit is a large high-current silicon device whose reverse leakage current is reasonably independent of voltage appearing on the diode. If $V_o = 1$ V at 20°C , then the value of output voltage at 40°C is equal to _____ V.

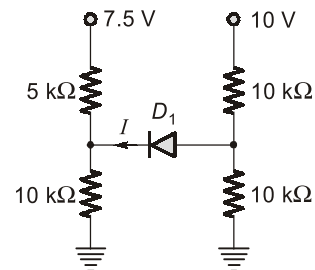Q.14 Consider the circuit shown in the figure below




If the cut-in voltage of the diode D_1 is equal to 0.7 V, then the value of current flowing through the diode is equal to _____ mA.

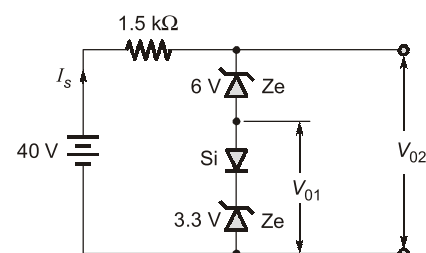Q.15 A 40 V dc supply is connected across the network comprising of Zener and Silicon diodes as shown. The regulated voltages V_{01} , V_{02} and source current I_s are



- (a) 2.4 V, 5.1 V and 21.7 mA
- (b) 3 V, 6 V and 22.7 mA
- (c) 3.3 V, 9.3 V and 20.5 mA
- (d) 4 V, 10 V and 20 mA

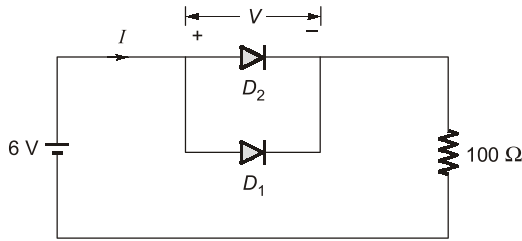Q.16 In the given circuit, D_1 is an ideal germanium diode and D_2 is a silicon diode having its cut-in voltage as 0.7 V, forward resistance as $20\ \Omega$ and reverse saturation current (I_s) as 10 nA. What are the values of I and V for this circuit, respectively?



- (a) 60 mA and 0 V
- (b) 50 mA and 0 V
- (c) 53 mA and 0.7 V
- (d) 44 mA and 1.58 V

Q.17 Consider the following statements :

A clamper circuit

1. adds/subtracts a dc voltage to/from a waveform.
2. does not change the shape of the waveform.
3. amplifies the waveform.


Of these statements

- (a) 1 and 2 are correct
- (b) 1 and 3 are correct
- (c) 2 and 3 are correct
- (d) 1, 2 and 3 are correct

Q.18 In order to rectify sinusoidal signals of millivolt range ($< 0.6\text{ V}$)


- (a) bridge rectifier using diodes can be employed
- (b) full-wave diode rectifier can be used
- (c) a diode is to be inserted in the feedback loop of an OP-AMP
- (d) a diode is to be inserted in the input of an OP-AMP

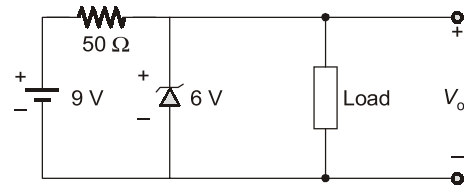Q.19 A zener diode in the circuit shown below has a knee current of 5 mA, and a maximum allowed power dissipation of 300 mW. What are the minimum and maximum load currents that can be drawn safely from the circuit, keeping the output voltage V_o constant at 6 V?



- (a) 0 mA, 180 mA
- (b) 5 mA, 110 mA
- (c) 10 mA, 55 mA
- (d) 60 mA, 180 mA

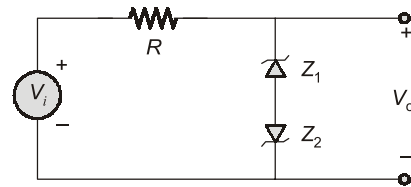Q.20 In the circuit shown below the zener voltage $V_{Z1} = V_{Z2} = 5\text{ volts}$, $V_f = 0.6\text{ V}$, V_o is the output



- (a) For $|V_i| \leq 5.6\text{ volts}$, $V_o = V_i$
- (b) For $|V_i| \leq 10\text{ volts}$, $V_o = V_i$
- (c) For $|V_i| \geq 5.6\text{ volts}$, $V_o = V_i$
- (d) $V_i \leq 5.6\text{ volts}$ for all V_i

Q.21 Following are the three statements regarding zener diode regulator. Which of them is incorrect?

1. It is a simple circuit, light weight, more reliable and provides regulation over a wide range of current
 2. As there is power dissipation in series resistor and the diode, it results in poor efficiency
 3. The stabilized output is independent of zener breakdown voltage and can be varied
- (a) only 1
 - (b) only 2
 - (c) only 3
 - (d) all are incorrect

Q.22 If the input ac is 10 V rms, the maximum voltage that will appear across the diode of a half-wave rectifier with a capacitor input filter will be


- (a) 10 V
- (b) 14 V
- (c) 20 V
- (d) 28 V

Q.23 A single-phase diode-bridge rectifier is connected to a load-resistor of $50\ \Omega$. The source voltage is $V = 200 \sin \omega t$ where $\omega = 2\pi \times 50$ radians/second. The power dissipated in the load resistor is

- (a) $\frac{400}{\pi}\text{ W}$
- (b) $\frac{3200}{\pi^2}\text{ W}$
- (c) 400 W
- (d) $\frac{800}{\pi}\text{ W}$

Multiple Select Questions (MSQ)


Q.116 For the circuit shown below :

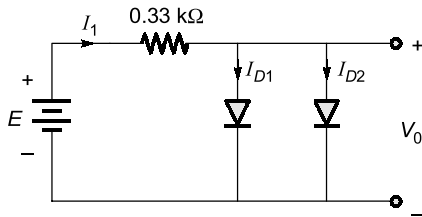

Which of the following statement is correct?


- (a) $I_1 > I_{D1} > I_{D2}$ (b) $I_{D1} < I_{D2} < I_1$
(c) $I_{D1} = I_{D2} = \frac{I_1}{2}$ (d) $I_1 = 28.18 \text{ mA}$

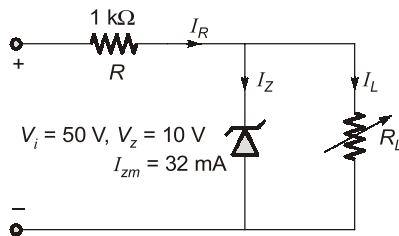Q.117 For the network shown below, which of the following option(s) is/are correct regarding the range of R_L and I_L that will result in V_{RL} being maintained at 10 V.



- (a) $R_{L \min} = 250 \Omega$ (b) $I_{L \min} = 8 \text{ mA}$
(c) $R_{L \max} = 1.25 \text{ k}\Omega$ (d) $I_{R} = 40 \text{ mA}$


Q.118 For the circuit shown below :

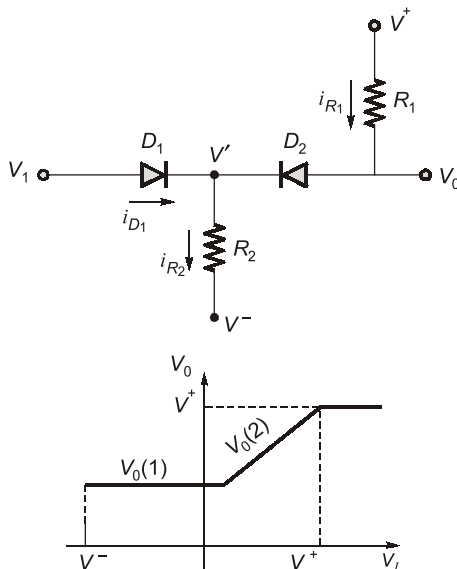

Assume the circuit parameters are $R_1 = 5 \text{ k}\Omega$, $R_2 = 10 \text{ k}\Omega$, $V_\gamma = 0.7 \text{ V}$, $V^+ = +5 \text{ V}$ and $V^- = -5 \text{ V}$

- (a) For $V_1 = 0$, $i_{R1} = 0.62 \text{ mA}$
(b) For $V_1 = 4 \text{ V}$, $i_{R1} = 0.2 \text{ mA}$
(c) For $V_1 = 4 \text{ V}$, $i_{R2} = 0.83 \text{ mA}$
(d) For $V_1 = 4 \text{ V}$, $i_{D1} = 0.63 \text{ mA}$


Q.119 For the circuit shown below :

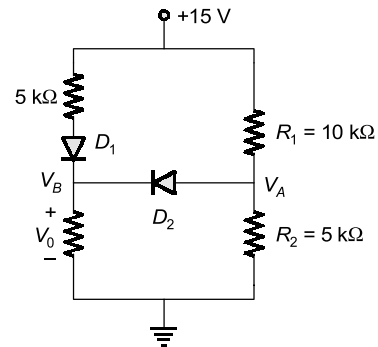

Which of the following are correct?

- (a) $V_A = 7.62 \text{ V}$ (b) $V_B = 6.92 \text{ V}$
(c) $V_A = 5 \text{ V}$ (d) $V_B = 9.53 \text{ V}$

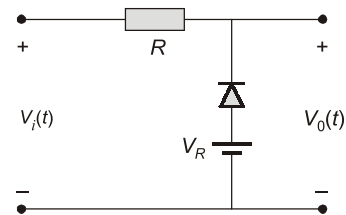Q.120 Assuming ideal diode characteristics, the input/output voltage relationship for the circuit shown in figure is



- (a) When $V_i(t) \leq V_R$: $V_0 = V_R$
(b) When $V_i(t) \leq V_R$: $V_0 = V_i(t)$
(c) When $V_i(t) > V_R$: $V_0 = V_R$
(d) When $V_i(t) > V_R$: $V_0 = V_i(t)$

Answers Basics of Semiconductor Diodes


| | | | | | | | |
|---------------|-----------|-----------|-------------|----------------|----------------|-------------|------------|
| 1. (c) | 2. (c) | 3. (d) | 4. (a) | 5. (d) | 6. (c) | 7. (b) | 8. (b) |
| 9. (a) | 10. (a) | 11. (c) | 12. (d) | 13. (4) | 14. (0) | 15. (d) | 16. (a) |
| 17. (a) | 18. (c) | 19. (c) | 20. (a) | 21. (c) | 22. (d) | 23. (c) | 24. (b) |
| 25. (b) | 26. (a) | 27. (d) | 28. (c) | 29. (a) | 30. (c) | 31. (c) | 32. (d) |
| 33. (d) | 34. (b) | 35. (c) | 36. (b) | 37. (d) | 38. (c) | 39. (a) | 40. (b) |
| 41. (a) | 42. (c) | 43. (d) | 44. (c) | 45. (b) | 46. (d) | 47. (b) | 48. (d) |
| 49. (b) | 50. (a) | 51. (d) | 52. (b) | 53. (d) | 54. (b) | 55. (c) | 56. (d) |
| 57. (b) | 58. (a) | 59. (a) | 60. (b) | 61. (d) | 62. (b) | 63. (b) | 64. (c) |
| 65. (c) | 66. (c) | 67. (500) | 68. (1.048) | 69. (b) | 70. (d) | 71. (b) | 72. (b) |
| 73. (c) | 74. (d) | 75. (b) | 76. (a) | 77. (c) | 78. (b) | 79. (b) | 80. (d) |
| 81. (d) | 82. (a) | 83. (d) | 84. (b) | 85. (b) | 86. (c) | 87. (d) | 88. (c) |
| 89. (c) | 90. (b) | 91. (a) | 92. (b) | 93. (d) | 94. (c) | 95. (d) | 96. (b) |
| 97. (c) | 98. (d) | 99. (d) | 100. (c) | 101. (b) | 102. (c) | 103. (a) | 104. (b) |
| 105. (c) | 106. (a) | 107. (b) | 108. (a) | 109. (a) | 110. (c) | 111. (0.12) | 112. (40) |
| 113. (0.5147) | 114. (10) | 115. (b) | 116. (c,d) | 117. (a,b,c,d) | 118. (a,b,c,d) | 119. (c,d) | 120. (a,d) |

Explanations Basics of Semiconductor Diodes**1. (c)**

$$\frac{1}{r_d} = \frac{\partial I_D}{\partial V} = \frac{I_D}{V_T}$$

r_d : dynamic resistance.
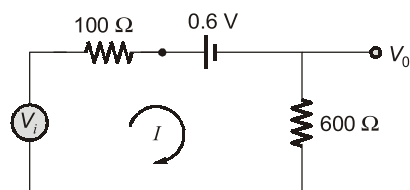
$$\therefore r_d = \frac{V_T}{I_D} = \frac{25}{4} = 6.25 \Omega$$



$$I = \frac{V_i - 0.6}{100 + 600} = \frac{10 - 0.6}{700}$$

$$= 0.01343 \text{ A}$$

$$\therefore V_0 = 600 \times 0.01343 = 8.058 \text{ V}$$

For $1 < t < 2$, diode is OFF, there will be no current in the circuit and hence

$$V_0 = 0 \text{ V}$$

Hence output waveform can be given as shown below:

**4. (a)**


For $0 < t < t_s$ diode will remain ON and hence

$$V_R + 5 = 0$$

$$\therefore V_R = -5 \text{ V}$$

3. (d)

For $0 \leq t \leq 1$, diode is ON

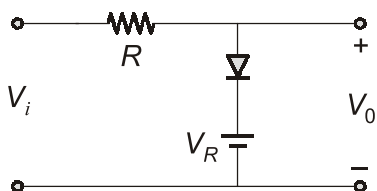2. (c)

Considering ideal diode :

for $V_i < V_R$, diode is OFF hence there is no current through R and $V_0 = V_i$.

For $V_i > V_R$, diode is ON hence

$$V_0 = V_R$$


(as diode will act as short circuit)

5. (d)

For $0 \leq V_i < V_R$ diode is OFF $\Rightarrow V_o = V_i$

For $V_R \leq V_i \Rightarrow$ diode is ON $\Rightarrow V_o = 5 \text{ V}$

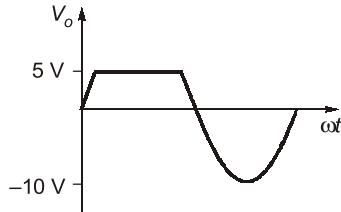Hence output waveform can be as shown below




6. (c)


For $V_i < V_R$ Diode is OFF $\Rightarrow V_o = V_i$

For $V_i > V_R$ Diode is ON $\Rightarrow V_o \simeq V_R$

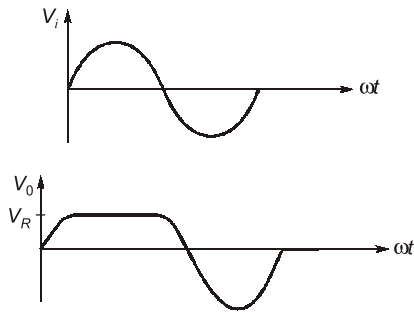
Hence for a sinusoidal input, output can be shown as below



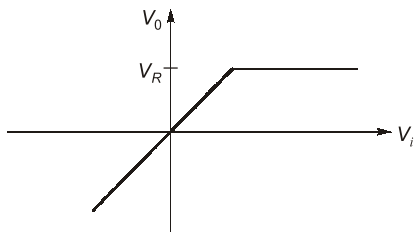Hence characteristic can be as shown below




7. (b)

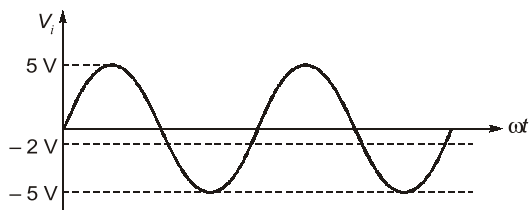

Hence given circuit acts as a clamper, sine wave clamped at -2 V .


8. (b)

For positive half cycle:

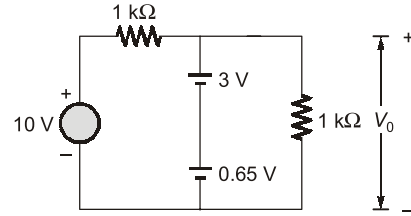

So, $V_o = 3.65 \text{ V}$


In negative half cycle:

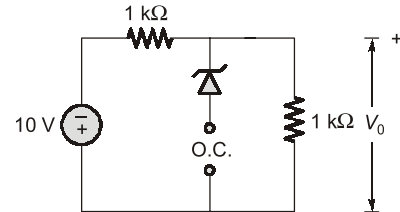

So, $V_o = -5 \text{ V}$

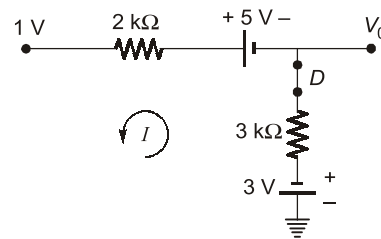9. (a)

\therefore Diode is forward bias (short circuit)




By applying KVL,

$$3 \text{ V} + 3 \text{ k}\Omega I - 5 \text{ V} + 2 \text{ k}\Omega I + 1 \text{ V} = 0$$

$$I = \frac{1 \text{ V}}{5 \text{ k}\Omega} = \frac{1}{5} \text{ mA}$$

$$\therefore V_o = -3 - 3 \times \frac{1}{5} = -\frac{18}{5} \text{ V}$$

10. (a)

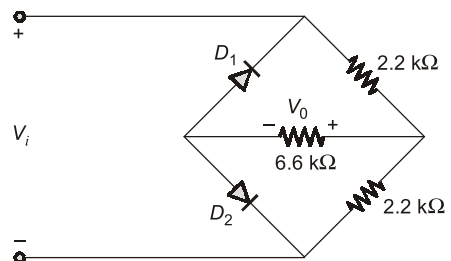

For positive half cycle of input voltage,

$D_1 \rightarrow \text{OFF}$

$D_2 \rightarrow \text{ON}$

