



POSTAL BOOK PACKAGE 2026

ELECTRONICS ENGINEERING

.....

CONVENTIONAL Practice Sets


CONTENTS

ANALOG CIRCUITS

1. Diode Circuits	2 - 18
2. BJT-Characteristics and Biasing	19 - 38
3. BJT as an Amplifier	39 - 52
4. FET Biasing and Basic FET Amplifiers	53 - 67
5. Frequency Response of Amplifiers	68 - 79
6. Differential Amplifiers	80 - 84
7. Feedback Amplifiers	85 - 95
8. Large Signal Amplifier	96 - 106
9. Operational Amplifier	107 - 137
10. Signal Generators and Waveform Shaping Circuits	138 - 157

Diode Circuits

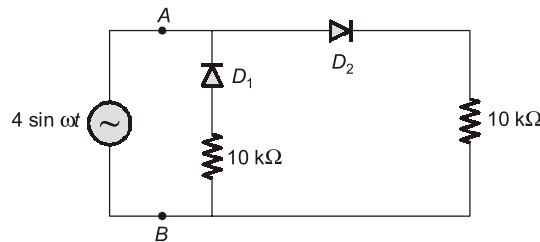Q1 A voltage source $V_{AB} = 4 \sin \omega t$, is applied across the terminals A and B of the circuit. The diodes are assumed to be ideal. Find the impedance offered by the circuit across the terminals A and B in kilo ohm.



Solution:

In +ve half cycle D_1 – off (R.B.)

D_2 – on (F.B.)

∴ Equivalent circuit will be


∴

$$V_{AB} = 4 \sin \omega t$$

$$I_{AB} = \frac{V_{AB}}{10 \text{ k}\Omega}$$

∴
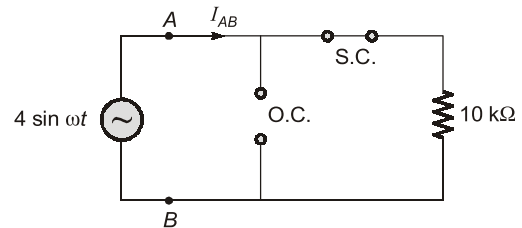
$$R_i = \frac{V_{AB}}{I_{AB}} = 10 \text{ k}\Omega$$



For –ve half cycle,

D_1 on, D_2 off


Equivalent circuit,

$$V_{AB} = 4 \sin \omega t$$


$$I_{AB} = \frac{4 \sin \omega t}{10 \text{ k}\Omega}$$

∴
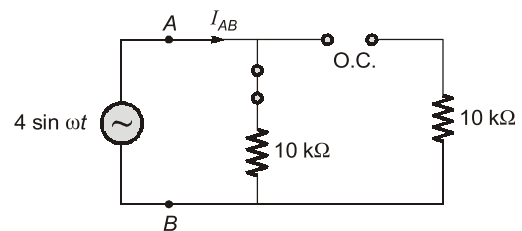
$$\frac{V_{AB}}{I_{AB}} = R_i = 10 \text{ k}\Omega$$



 Q2 A DC current of $26 \mu\text{A}$ flows through the circuit shown. The diode in the circuit is forward biased and it has an ideality factor of one. At the quiescent point, the diode has a junction capacitance of 0.5 nF . Its neutral region resistances can be neglected. Assume that the room temperature thermal equivalent voltage is 26 mV .




For $\omega = 2 \times 10^6 \text{ rad/s}$, the amplitude of the small-signal component of diode current.

Solution:

The small-signal equivalent model of the given circuit can be drawn as shown below.

Given that,
 
$$\begin{aligned}\omega &= 2 \times 10^6 \text{ rad/sec} \\ C_j &= 0.5 \text{ nF} \\ I_{DC} &= 26 \mu\text{A} \\ V_T &= 26 \text{ mV} \\ \eta &= 1\end{aligned}$$



Since, small signal incremental diode resistance, $r_d = \frac{\eta V_T}{I_{DC}} = \frac{26 \text{ mV}}{26 \mu\text{A}} = 1 \text{ k}\Omega$

and impedance due to junction capacitance, $\frac{1}{\omega C_j} = \frac{1}{2 \times 10^6 \times 0.5 \times 10^{-9}} \Omega = 1 \text{ k}\Omega$

So, total impedance of the circuit will be,

$$Z = \left(r_d \parallel \frac{1}{j\omega C_j} \right) + 100 \Omega$$

$$\left(r_d \parallel \frac{1}{j\omega C_j} \right) = \frac{(1000)(-j1000)}{1000 - j1000} \Omega = \frac{-j(1+j)}{2} \text{ k}\Omega = \frac{1}{2}(1-j) \text{ k}\Omega = (500 - j500) \Omega$$


\therefore

$$Z = 600 - j500 \Omega$$

$$|Z| = 100\sqrt{36 + 25} = 100\sqrt{61} \Omega$$

$$I_m = \frac{V_m}{|Z|} = \frac{5 \text{ mV}}{100\sqrt{61} \Omega} = \frac{50}{\sqrt{61}} \mu\text{A} = 6.40 \mu\text{A}$$

 Q3 Determine the current I_{D2} and the voltage V_o in the multidiode circuit shown in the figure below. Assume that, cut-in voltage $V_\gamma = 0.7 \text{ V}$ for each diode.



Solution:

To begin, initially assume that, both the diodes D_1 and D_2 are in their conducting state.

By applying KCL at A and B nodes, we have

$$\frac{15 - V_A}{10} = I_{D2} + \frac{V_A}{5} \quad \dots(i)$$

$$\text{and} \quad \frac{15 - (V_B + 0.7)}{5} + I_{D2} = \frac{V_B}{10} \quad \dots(ii)$$

We note that $V_B = V_A - 0.7$. Combining the two equations and eliminating I_{D2} , we find

$$V_A = 7.62 \text{ V} \quad \text{and} \quad V_B = 6.92 \text{ V}$$

From equation (i) above, we obtain

$$\frac{15 - 7.62}{10} = I_{D2} + \frac{7.62}{5} \Rightarrow I_{D2} = -0.786 \text{ mA}$$

We assumed that D_2 was ON, so a negative current is inconsistent with that initial assumption.

Now assume that diode D_2 is OFF and D_1 is ON. To find the node voltages, we can simply use voltage divider principle as


$$V_A = \left(\frac{5}{5 + 10} \right) (15) = 5 \text{ V}$$

and


$$V_B = V_o = \left(\frac{10}{10 + 5} \right) (15 - 0.7) = 9.53 \text{ V}$$

These voltages show that diode D_2 is indeed reverse biased so that $I_{D2} = 0$.

 Q4 Find the diode current I_D in the circuit shown below when the diode has cut in voltage, $V_\gamma = 0.7 \text{ V}$ and forward resistance, $R_f = 25 \Omega$.





Solution:

 

Given : Diode cut-in voltage = 0.7 V and diode forward resistance = 25 Ω

  Replacing the diode with its equivalent, we get,



Using KVL, $10 - 100I_1 - 100(I_1 - I_D) = 0$... (i)

$-0.7 - 25I_D + 100(I_1 - I_D) = 0$... (ii)

Solving equation (i) and (ii)

$10 - 200I_1 - 100I_D = 0$... (iii)

$-0.7 - 225I_D + 100I_1 = 0$... (iv)

Multiplying equation (iv) by 2 and adding, we get


$10 - 1.4 - 450I_D - 100I_D = 0$

$8.6 = 550I_D$

\therefore

$$I_D = \frac{8.6}{550} = 15.63 \text{ mA}$$

 Q5 The ideal transfer characteristic of a particular circuit is given in figure. Design the circuit. Draw the output waveform with proper explanation, if $V_i = 10 \sin \omega t$.



Solution:

Slope of the curve between A and B is

$$m = \frac{(8-5)}{(8-5)} = 1$$

The circuit diagram for the above input-output (transfer) characteristic is a two-level clipper as shown below.



Cut in voltages of diodes are zero.

For $V_i < 5 \text{ V} \rightarrow$ diode D_1 will be on and D_2 will be off

and

$$V_o = 5 \text{ V}$$

  For $V_i > 8 \text{ V} \rightarrow$ diode D_1 will be off and diode D_2 will be on



and

$$V_o = 8 \text{ V}$$

For $5 < V_i < 8 \text{ V} \rightarrow$ both the diodes will be off

and

$$V_o = V_i$$

Given that

$$V_i = 10 \sin \omega t$$

or

$$V_i = 10 \sin \theta$$

$$(\omega t = \theta)$$

For $V_i < 5$;

$$10 \sin \theta < 5 \Rightarrow 0 < \theta < 30^\circ \text{ and } 150^\circ < \theta < 360^\circ$$

$$V_o = 5 \text{ V}$$

For $V_i > 8 \text{ V}$;

$$10 \sin \theta > 8 \Rightarrow 53.13^\circ < \theta < 126.869^\circ$$

$$V_o = 8 \text{ V}$$

For $5 < V_i < 8 \text{ V}$;


$$30^\circ < \theta < 53.13^\circ \text{ and } 126.87^\circ < \theta < 150^\circ$$

$$V_o = V_i$$

The required voltage-current characteristics can be written as


$$V_o = \begin{cases} 5 \text{ V} & ; V_i < 5 \text{ V} \\ V_i & ; 5 \text{ V} < V_i < 8 \text{ V} \\ 8 \text{ V} & ; V_i > 8 \text{ V} \end{cases}$$

Now output waveform will be

 


Q.6 Draw the neat circuit of a voltage doubler. Explain its operation. Draw the waveforms for the voltages across the two capacitors.

Solution:

 

Voltage follower circuit

 The figure shows a circuit-composed of two sections in cascade, a clamp circuit formed by C_1 and D_1 and peak rectifier formed by D_2 and C_2 .



When excited by a sinusoidal of amplitude V_m the clamping section provides the waveform shown. Assuming ideal diodes, while the positive peaks are damped to 0 V, the negative peak reaches $-2V_m$. In response to this wave form, the peak-detector section provides, across capacitor C_2 a negative dc voltage of magnitude $2V_m$. Because the output voltage is double the input peak, the circuit is known as a voltage doubler.