



POSTAL BOOK PACKAGE 2025

ELECTRICAL ENGINEERING

.....

CONVENTIONAL Practice Sets


CONTENTS

POWER ELECTRONICS

| | |
|--|----|
| 1. Power Semi-conductor Diode and Transistor | 2 |
| 2. Diode Rectifiers | 5 |
| 3. Thyristors | 12 |
| 4. Thyristor Commutation Techniques | 18 |
| 5. Phase Controlled Rectifiers | 23 |
| 6. Choppers | 42 |
| 7. Inverters | 54 |
| 8. Resonant Converters | 74 |
| 9. Power Semiconductor Drives | 76 |
| 10. Switched Mode Power Supply (SMPS) | 90 |
| 11. Miscallenaous | 94 |

Power Semi-conductor Diode and Transistor

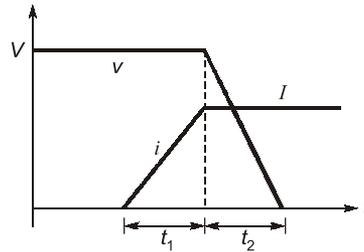Q1 The voltage across and current through a power semiconductor device switching transients are shown in the figure. Deduce the expression for the energy lost in the ON/OFF transition in terms of V , I , t and t_2 .



Solution:

During t_1 interval voltage is constant (V), while current starts increasing. Thereafter, in t_2 interval voltage starts decreasing and becomes zero and current becomes constant (I), so the transition is turn on.

During t_1 interval:

$$\text{Power loss} = vi$$

$$\text{Energy loss, } E_1 = \int vi dt [= E_1(\text{Say})]$$

$\therefore v$ is constant in this interval,

\therefore

$$\begin{aligned} E_1 &= V \cdot \int i dt \\ &= V(\text{Area under } i\text{-}t \text{ curve in } t_1) \end{aligned}$$

or

$$E_1 = V \left[\frac{1}{2} I t_1 \right] = \frac{1}{2} V I t_1$$

During t_2 interval:

$$\text{Power loss} = vi$$

$$\text{Energy loss, } E_2 = \int vi dt$$

$\therefore i$ is constant in the interval ($=I$)

\therefore

$$\begin{aligned} E_2 &= I \cdot \int v dt \\ &= I(\text{Area under } v\text{-}t \text{ curve in } t_2) \end{aligned}$$

or


$$E_2 = I \left(\frac{1}{2} V t_2 \right) = \frac{1}{2} V I t_2$$

Therefore, total energy lost during ON transition,


$$E_{\text{lost}} = E_1 + E_2 = \frac{1}{2} V I t_1 + \frac{1}{2} V I t_2$$

or,
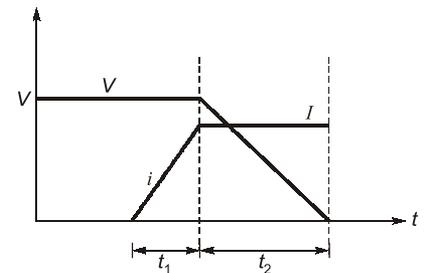
$$E_{\text{lost}} = \frac{1}{2} V I (t_1 + t_2)$$



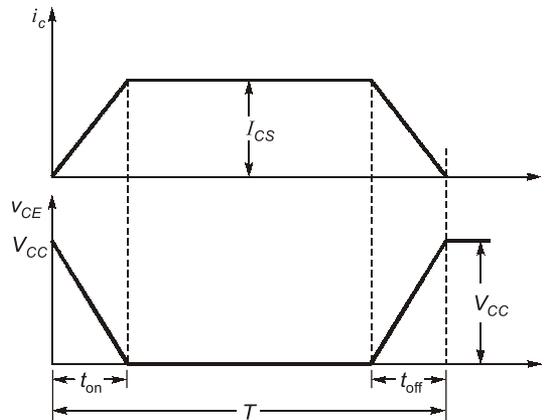Q2 Find the energy loss during switch-on and off intervals of a power transistor with switching characteristics as shown in the figure. Where $I_{CS} = 80$ A, $V_{CC} = 220$ V, $t_{on} = 1.5$ ms and $t_{off} = 4$ ms. Also determine the average power loss in the transistor if switching frequency is 2 kHz.



Solution:

From the switching characteristics given in the figure above.

$$\begin{aligned}
 \text{Energy loss during turn-on } (E_{\text{loss(on)}}) &= \int_0^{t_{on}} i_c \cdot v_{CE} dt \\
 &= \int_0^{t_{on}} \left[\frac{I_{CS}}{t_{on}} \right] t \cdot \left(V_{CC} - \frac{V_{CC}}{t_{on}} t \right) dt \\
 &= \int_0^{t_{on}} \frac{I_{CS} V_{CC}}{t_{on}} \cdot t dt - \int_0^{t_{on}} \frac{I_{CS} V_{CC}}{t_{on}^2} \cdot t^2 dt \\
 &= \frac{I_{CS} V_{CC}}{t_{on}} \cdot \frac{t_{on}^2}{2} - \frac{I_{CS} V_{CC}}{t_{on}^2} \cdot \frac{t_{on}^3}{3} = \frac{I_{CS} V_{CC}}{6} \cdot t_{on}
 \end{aligned}$$

$$\therefore E_{\text{loss(on)}} = \frac{80 \times 220}{6} \times 0.15 \times 10^{-3} \text{ Watt-sec.}$$

$$E_{\text{loss(on)}} = 0.44 \text{ Watt-sec.}$$

Similarly,

$$E_{\text{loss(off)}} = \frac{I_{CS} V_{CC}}{6} \cdot t_{off} \quad \text{or} \quad E_{\text{loss(off)}} = \frac{80 \times 220}{6} \times 0.4 \times 10^{-3} \text{ Watt-sec.}$$

$$\therefore E_{\text{loss(off)}} = 1.17 \text{ Watt-sec.}$$

Average power loss in the power transistor for switching frequency of 2 kHz

$$= (\text{Energy loss in ON and OFF switching}) \times \text{Switching frequency}$$

$$= \frac{I_{CS} V_{CC}}{6} (t_{on} + t_{off}) \times f = (0.44 + 1.17) \times 2 \times 10^3 = 3.22 \text{ kW}$$

Q3 For a power diode, the reverse recovery time is 3.9 μ s and the rate of diode-current decay is 50 A/ μ s. For a softness factor of 0.3, calculate the peak inverse current and storage charge.


Solution:

Given, Reverse recovery time (t_{rr}) = 3.9 μ s

$$\text{Softness factor } \left(\frac{t_5}{t_4} \right) = 0.3$$

Diode Rectifiers

- Q1** A diode circuit feeds an ideal inductor as shown in the figure. Given $V_s = 100 \sin(\omega t)$ volt, where $\omega = 100\pi$ rad/s and $L = 31.83$ mH. The initial value of inductor current is zero. When switch S is closed at $t = 2.5$ ms, then calculate the maximum value of inductor current i_L in the first cycle.

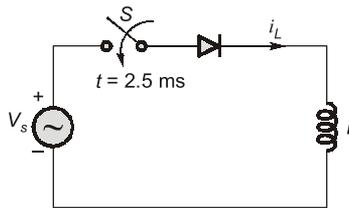**Solution:**

At $t = 2.5$ ms the circuit is as shown in figure,

$$-V_s + V_L = 0$$

$$V_L = L \frac{di_L}{dt} = V_s$$

$$di_L = \frac{V_s}{L} dt$$

Integrating on both sides,

$$\int di_L = \int \frac{V_s}{L} dt = \int \frac{V_m \sin \omega t}{\omega L} d(\omega t)$$

$$i_L(t) = \frac{V_m}{\omega L} [-\cos(\omega t)] + K$$

When $t = 0.0025$ sec, at this instant $i_L(t) = 0$

$$0 = \frac{100}{100\pi \times 31.83 \times 10^{-3}} [-\cos(100\pi \times 0.0025)] + K$$

$$= -7.07 + K$$

\therefore

$$K = 7.07$$

The peak value of the inductor current in the first half cycle will be at $(\omega t = 180^\circ)$

$$i_L(t)_{\max} = \frac{V_m}{\omega L} [-\cos(\pi)] + K$$

\therefore

$$I_{\max} = \frac{100}{100\pi \times 31.83 \times 10^{-3}} + 7.07 = 17.07 \text{ A}$$

- Q2** The IGBT used in the circuit of figure shown below, has the following data:

$t_{\text{on}} = 3 \mu\text{s}$, $t_{\text{off}} = 1.2 \mu\text{s}$, Duty cycle (D) = 0.7, $V_{CE(\text{sat})} = 2$ V and $f_s = 1$ kHz.

Determine:

- Average load current
- Conduction power loss
- Switching power loss during turn-on and turn-off.

