



**POSTAL  
BOOK PACKAGE**

**2024**

**CONTENTS**

**ELECTRICAL  
ENGINEERING**

**Objective Practice Sets**

## **Analog Electronics**

1.	Basics of Semiconductor Diodes .....	2
2.	Bipolar Junction Transistors and Characteristics .....	29
3.	Junction and Field Effect Transistors .....	44
4.	Transistor Amplifiers and Frequency Response .....	55
5.	Feedback Amplifiers .....	67
6.	Oscillators and Multivibrators .....	73
7.	Operational Amplifiers .....	80
8.	Miscellaneous .....	95


## Basics of Semiconductor Diodes

### MCQ and NAT Questions

**Q.1** A diode whose terminal characteristics are related as  $i_D = I_s e^{V/V_T}$ , where  $I_s$  is the reverse saturation current and  $V_T$  is thermal voltage ( $V_T = 25$  mV), is biased at  $I_D = 4$  mA. Its dynamic resistance is





- (a)  $12.5 \Omega$                       (b)  $50 \Omega$   
 (c)  $6.25 \Omega$                       (d)  $25 \Omega$

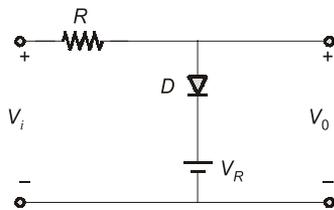**Q.2** In the circuit shown below the input  $V_i$  has positive and negative swings.  $V_o$  is the output.




- (a)  $V_o = 0$  for negative  $V_i$   
 (b)  $V_o = V_R$  for positive  $V_i$   
 (c)  $V_o = V_R$  for  $V_i > V_R$   
 (d)  $V_o = V_R$  for all  $V_i$

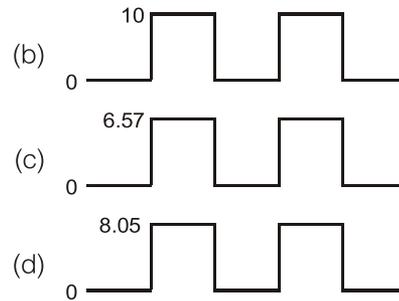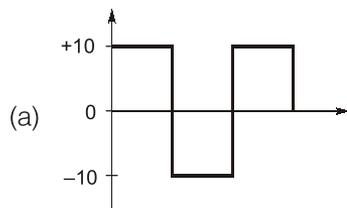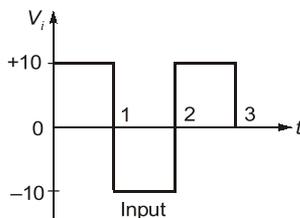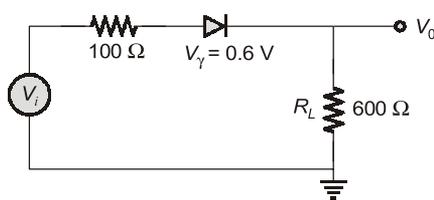**Q.3** In the circuit shown below, if the input voltage  $V_i$  is as shown below then the corresponding output waveform will be





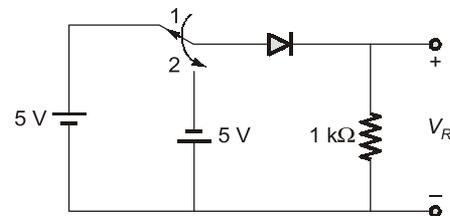
**Q.4** In the circuit shown below, the switch was connected to position 1 at  $t < 0$  and at  $t = 0$ , it is changed to position 2. Assume that the diode has zero voltage drop and a storage time  $t_s$ . For  $0 < t \leq t_s$ ,  $V_R$  is given by (all in Volts)





- (a)  $V_R = -5$                       (b)  $V_R = 0$   
 (c)  $0 \leq V_R < 5$                       (d)  $-5 < V_R < 0$

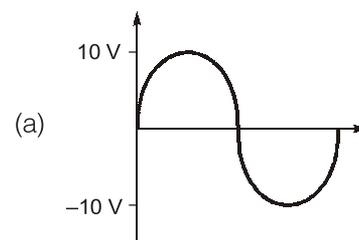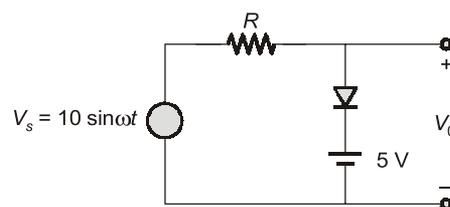**Q.5** For the circuit shown below assuming ideal diode, the output waveform  $V_o$  is




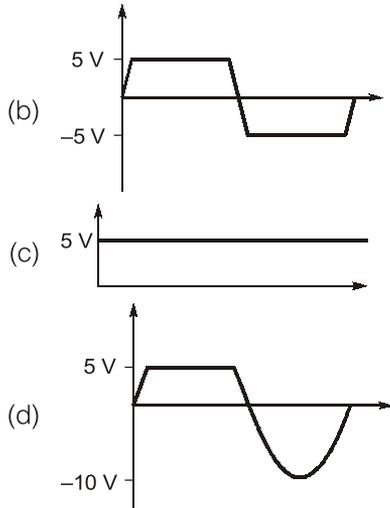

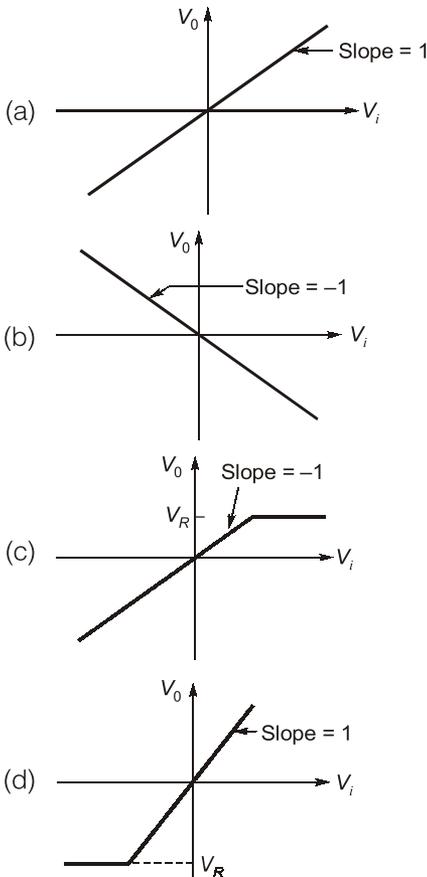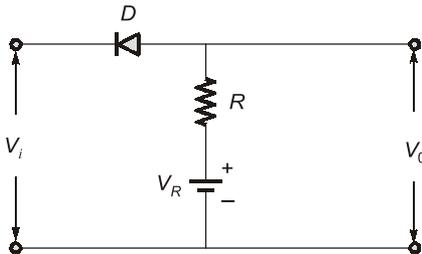**Q.6** The transfer characteristic of the network shown below is represented as




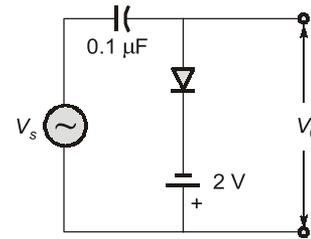**Q.7** For an input of  $V_s = 5 \sin \omega t$ , (assuming ideal diode), circuit shown below will behave as a




- (a) clipper, sine wave clipped at  $-2\text{ V}$
- (b) clamper, sine wave clamped at  $-2\text{ V}$
- (c) clamper, sine wave clamped at zero volt
- (d) clipper, sine wave clipped at  $2\text{ V}$

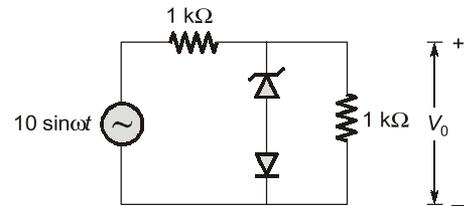**Q.8** The cut-in voltage of both zener diode  $D_z$  and  $D$  shown in figure is  $0.65\text{ V}$ , while breakdown voltage of the zener is  $3\text{ V}$ . Diode is considered to be ideal. The value of peak output voltage  $V_o$ ,





- (a)  $3\text{ V}$  in the positive half cycle and  $0.65\text{ V}$  in the negative half cycle.
- (b)  $3.65\text{ V}$  in the positive half cycle and  $-5\text{ V}$  in the negative half cycle.
- (c)  $3\text{ V}$  in positive half cycle and  $-5\text{ V}$  in the negative half cycle
- (d)  $-3.65\text{ V}$  in positive half cycle and  $5\text{ V}$  in the negative half cycle

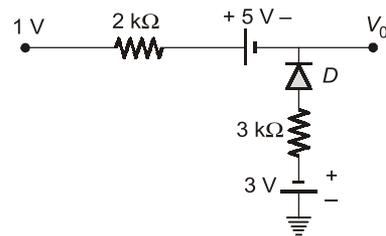**Q.9** What is the output voltage  $V_o$  for the circuit shown below assuming an ideal diode?




- (a)  $-\frac{18}{5}\text{ V}$
- (b)  $\frac{18}{5}\text{ V}$
- (c)  $-\frac{13}{5}\text{ V}$
- (d)  $\frac{13}{5}\text{ V}$

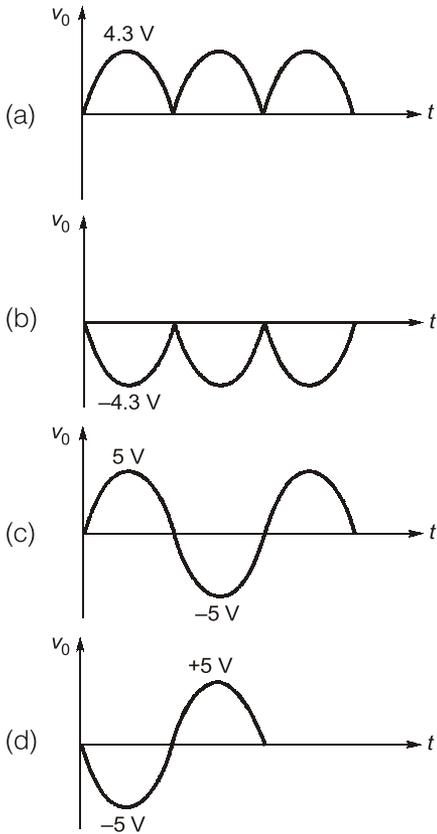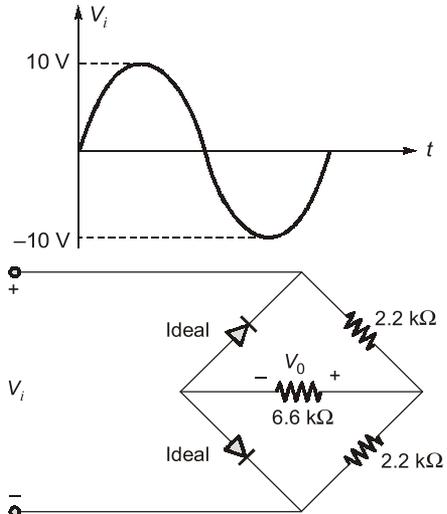**Q.10** The correct waveform for output ( $V_o$ ) for below network is




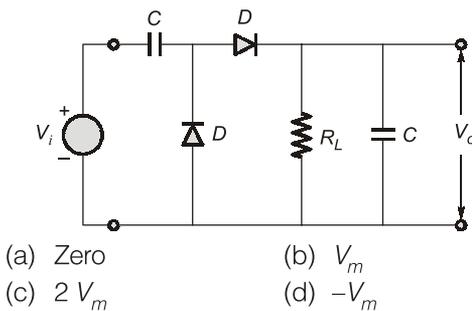Q.11 Consider the below circuit, for  $V_i = V_m \sin \omega t$ , the output voltage  $V_o$  for  $R_L \rightarrow \infty$  will be



- (a) Zero
- (b)  $V_m$
- (c)  $2 V_m$
- (d)  $-V_m$

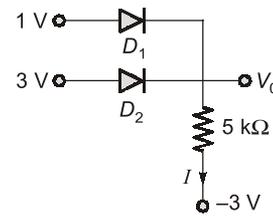
Q.12 Consider the circuit shown in the figure below:



If diode  $D_1$  and  $D_2$  are made up of same material with the cut-in voltage  $V_\gamma = 0.7 \text{ V}$ , then the value of current  $I$  is equal to


- (a) 0.46 mA
- (b) 0.99 mA
- (c) 0.59 mA
- (d) 1.06 mA

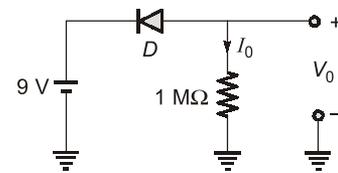Q.13 Consider the diode circuit shown in the figure below:




The diode in the circuit is a large high-current silicon device whose reverse leakage current is reasonably independent of voltage appearing on the diode. If  $V_o = 1 \text{ V}$  at  $20^\circ \text{C}$ , then the value of output voltage at  $40^\circ \text{C}$  is equal to \_\_\_\_\_ V.

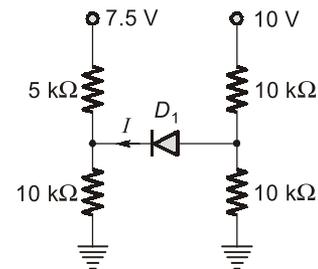Q.14 Consider the circuit shown in the figure below




If the cut-in voltage of the diode  $D_1$  is equal to  $0.7 \text{ V}$ , then the value of current flowing through the diode is equal to \_\_\_\_\_ mA.

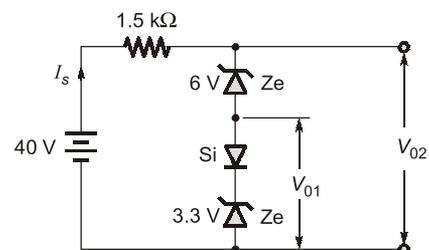Q.15 A 40 V dc supply is connected across the network comprising of Zener and Silicon diodes as shown. The regulated voltages  $V_{o1}$ ,  $V_{o2}$  and source current  $I_s$  are



- (a) 2.4 V, 5.1 V and 21.7 mA
- (b) 3 V, 6 V and 22.7 mA
- (c) 3.3 V, 9.3 V and 20.5 mA
- (d) 4 V, 10 V and 20 mA

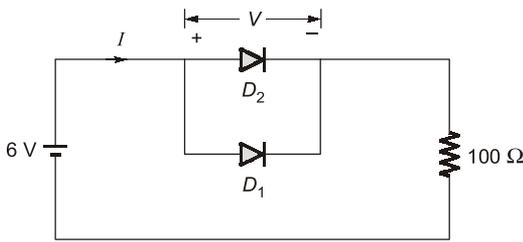**Q.16** In the given circuit,  $D_1$  is an ideal germanium diode and  $D_2$  is a silicon diode having its cut-in voltage as 0.7 V, forward resistance as  $20\ \Omega$  and reverse saturation current ( $I_s$ ) as 10 nA. What are the values of  $I$  and  $V$  for this circuit, respectively?



- (a) 60 mA and 0 V
- (b) 50 mA and 0 V
- (c) 53 mA and 0.7 V
- (d) 44 mA and 1.58 V

**Q.17** Consider the following statements :

A clamper circuit

1. adds/subtracts a dc voltage to/from a waveform.
2. does not change the shape of the waveform.
3. amplifies the waveform.


Of these statements

- (a) 1 and 2 are correct
- (b) 1 and 3 are correct
- (c) 2 and 3 are correct
- (d) 1, 2 and 3 are correct

**Q.18** In order to rectify sinusoidal signals of millivolt range ( $< 0.6\text{ V}$ )


- (a) bridge rectifier using diodes can be employed
- (b) full-wave diode rectifier can be used
- (c) a diode is to be inserted in the feedback loop of an OP-AMP
- (d) a diode is to be inserted in the input of an OP-AMP

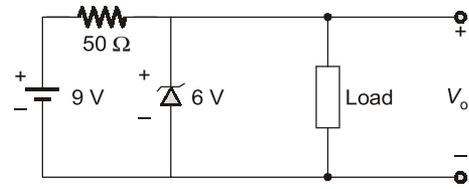**Q.19** A zener diode in the circuit shown below has a knee current of 5 mA, and a maximum allowed power dissipation of 300 mW. What are the minimum and maximum load currents that can be drawn safely from the circuit, keeping the output voltage  $V_o$  constant at 6 V?



- (a) 0 mA, 180 mA
- (b) 5 mA, 110 mA
- (c) 10 mA, 55 mA
- (d) 60 mA, 180 mA

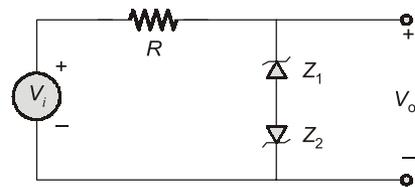**Q.20** In the circuit shown below the zener voltage  $V_{Z1} = V_{Z2} = 5\text{ volts}$ ,  $V_f = 0.6\text{ V}$ ,  $V_o$  is the output



- (a) For  $|V_i| \leq 5.6\text{ volts}$ ,  $V_o = V_i$
- (b) For  $|V_i| \leq 10\text{ volts}$ ,  $V_o = V_i$
- (c) For  $|V_i| \geq 5.6\text{ volts}$ ,  $V_o = V_i$
- (d)  $V_i \leq 5.6\text{ volts}$  for all  $V_i$

**Q.21** Following are the three statements regarding zener diode regulator. Which of them is incorrect?

1. It is a simple circuit, light weight, more reliable and provides regulation over a wide range of current
  2. As there is power dissipation in series resistor and the diode, it results in poor efficiency
  3. The stabilized output is independent of zener breakdown voltage and can be varied
- (a) only 1
  - (b) only 2
  - (c) only 3
  - (d) all are incorrect

**Q.22** If the input ac is 10 V rms, the maximum voltage that will appear across the diode of a half-wave rectifier with a capacitor input filter will be

- (a) 10 V
- (b) 14 V
- (c) 20 V
- (d) 28 V

**Q.23** A single-phase diode-bridge rectifier is connected to a load-resistor of  $50\ \Omega$ . The source voltage is  $V = 200 \sin \omega t$  where  $\omega = 2\pi \times 50$  radians/second. The power dissipated in the load resistor is

- (a)  $\frac{400}{\pi}\text{ W}$
- (b)  $\frac{3200}{\pi^2}\text{ W}$
- (c) 400 W
- (d)  $\frac{800}{\pi}\text{ W}$

**Q.24** The ripple factor of a power supply is given by (symbols have the usual meaning)

(a)  $\frac{P_{dc}}{P_{ac}}$                       (b)  $\sqrt{\left(\frac{I_{rms}}{I_{dc}}\right)^2} - 1$   
 (c)  $\sqrt{\left(\frac{I_{dc}}{I_{rms}}\right)^2} - 1$                       (d)  $\frac{I_{dc}}{I_{rms}}$

**Q.25** A voltage of  $200 \cos 100t$  is applied to a HWR with a load resistance of  $5 \text{ k}\Omega$ . The rectifier is represented by an ideal diode in series with a resistance of  $1 \text{ k}\Omega$ . The maximum value of current, d.c component of current and rms value of current will be respectively

- (a) 33.33 mA, 14.61 mA, 16.67 mA  
 (b) 33.33 mA, 10.61 mA, 16.67 mA  
 (c) 28.33 mA, 14.61 mA, 13.33 mA  
 (d) 40 mA, 20 mA, 25 mA

**Q.26** An ideal low-pass filter has a cut-off frequency of 100 Hz. If the input to the filter in volts is  $v(t) = 30\sqrt{2} \sin 1256t$ , the magnitude of the output of the filter will be

- (a) 0 V                                      (b) 20 V  
 (c) 100 V                                    (d) 200 V

**Q.27** The ratio of available power from the DC component of a full-wave rectified sinusoid to the available power of the rectified sinusoid is

- (a)  $8/\pi$                                       (b) 2  
 (c)  $4/\pi$                                       (d)  $8/\pi^2$

**Q.28** For a full-wave rectifier with shunt capacitor filter, the peak to peak ripple voltage is

(a)  $\frac{2I_{DC}}{fC}$                                       (b)  $\frac{I_{DC}}{fC}$   
 (c)  $\frac{I_{DC}}{2fC}$                                       (d)  $\frac{I_{DC}}{4fC}$

(where  $f$  = fundamental power line frequency,  $I_{DC}$  = DC current)

**Q.29** Consider the following rectifier circuits:

1. Half-wave rectifier without filter.
2. Full-wave rectifier without filter.
3. Full-wave rectifier with series inductance filter.
4. Full-wave rectifier with capacitance filter.

The sequence of these rectifier circuits in decreasing order of their ripple factor is

- (a) 1, 2, 3, 4                                      (b) 3, 4, 1, 2  
 (c) 1, 4, 3, 2                                      (d) 3, 2, 1, 4

**Q.30 Assertion (A)** : A rectifier with inductor filter is more efficient for high load current.

**Reason (R)** : In rectifier with inductor filter we can use a larger choke to reduce ripple, larger choke will have higher dc resistance which will result in lower dc output voltage for higher load current.

- (a) Both A and R are individually true and R is the correct explanation of A  
 (b) Both A and R are individually true but R is not the correct explanation of A  
 (c) A is true but R is false  
 (d) A is false but R is true

**Q.31** When a junction diode is used as a half-wave rectifier with purely resistive load and sinusoidal input voltage, what is the value of diode conduction angle (where  $\phi_i$  is the ignition angle corresponding to the cut-in voltage)?

- (a)  $\pi$   
 (b)  $\pi - \phi_i$   
 (c)  $\pi - 2\phi_i$   
 (d) Slightly greater than  $\pi$


**Q.32** For full wave rectification, a four diode bridge rectifier is claimed to have the following advantages over a two diode circuit:

- (1) less expensive transformer
- (2) smaller size transformer, and
- (3) suitability for higher voltage application.

Of these,

- (a) only 1 and 2 are true  
 (b) only 1 and 3 are true  
 (c) only 2 and 3 are true  
 (d) 1, 2 and 3 are true

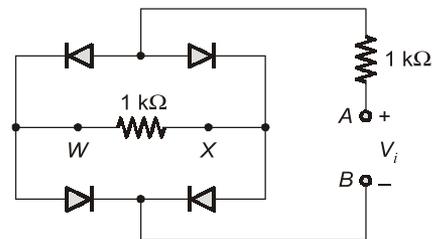**Q.33** A signal of  $25 \sin \omega t$  is applied across  $AB$  assuming ideal diodes, the output measured across  $WX$  is



- (a)  $\sin \omega t$                                       (b) 50 V  
 (c)  $|\sin \omega t|$                                       (d) 0 V

**Answers Basics of Semiconductor Diodes**

- 1. (c)      2. (c)      3. (d)      4. (a)      5. (d)      6. (c)      7. (b)      8. (b)
- 9. (a)      10. (a)      11. (c)      12. (d)      13. (4)      14. (0)      15. (d)      16. (a)
- 17. (a)      18. (c)      19. (c)      20. (a)      21. (c)      22. (d)      23. (c)      24. (b)
- 25. (b)      26. (a)      27. (d)      28. (c)      29. (a)      30. (c)      31. (c)      32. (d)
- 33. (d)      34. (b)      35. (c)      36. (b)      37. (d)      38. (c)      39. (a)      40. (b)
- 41. (a)      42. (c)      43. (d)      44. (c)      45. (b)      46. (d)      47. (b)      48. (d)
- 49. (b)      50. (a)      51. (d)      52. (b)      53. (d)      54. (b)      55. (c)      56. (d)
- 57. (b)      58. (a)      59. (a)      60. (b)      61. (d)      62. (b)      63. (b)      64. (c)
- 65. (c)      66. (c)      67. (500)      68. (1.048)      69. (b)      70. (d)      71. (b)      72. (b)
- 73. (c)      74. (d)      75. (b)      76. (a)      77. (c)      78. (b)      79. (b)      80. (d)
- 81. (d)      82. (a)      83. (d)      84. (b)      85. (b)      86. (c)      87. (d)      88. (c)
- 89. (c)      90. (b)      91. (a)      92. (b)      93. (d)      94. (c)      95. (d)      96. (b)
- 97. (c)      98. (d)      99. (d)      100. (c)      101. (b)      102. (c)      103. (a)      104. (b)
- 105. (c)      106. (a)      107. (b)      108. (a)      109. (a)      110. (c)      111. (0.12)      112. (40)
- 113. (0.5147)      114. (10)      115. (b)      116. (c,d)      117. (a,b,c,d)      118. (a,b,c,d)      119. (c,d)      120. (a,d)


**Explanations Basics of Semiconductor Diodes**

1. (c)

$$\frac{1}{r_d} = \frac{\partial I_D}{\partial V} = \frac{I_D}{V_T}$$

$r_d$ : dynamic resistance.
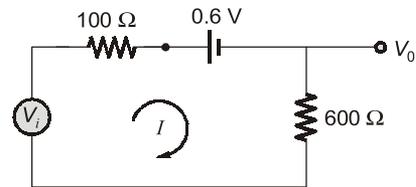
$$\therefore r_d = \frac{V_T}{I_D} = \frac{25}{4} = 6.25 \Omega$$



$$I = \frac{V_i - 0.6}{100 + 600} = \frac{10 - 0.6}{700} = 0.01343 \text{ A}$$

$$\therefore V_0 = 600 \times 0.01343 = 8.058 \text{ V}$$


For  $1 < t < 2$ , diode is OFF, there will be no current in the circuit and hence

$$V_0 = 0 \text{ V}$$

Hence output waveform can be given as shown below:



2. (c)

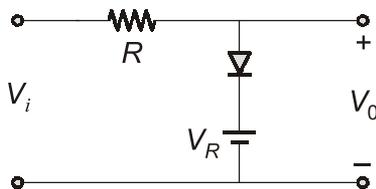

Considering ideal diode :

for  $V_i < V_R$ , diode is OFF hence there is no current through  $R$  and  $V_0 = V_i$ .

For  $V_i > V_R$ , diode is ON hence

$$V_0 = V_R$$

(as diode will act as short circuit)

3. (d)

For  $0 \leq t \leq 1$ , diode is ON

4. (a)


For  $0 < t < t_s$  diode will remain ON and hence

$$V_R + 5 = 0$$

$$\therefore V_R = -5 \text{ V}$$

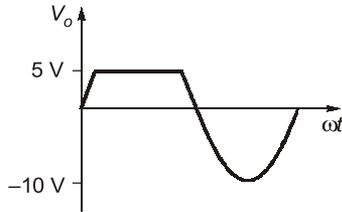
**5. (d)**

For  $0 \leq V_i < V_R = \text{diode is OFF} \Rightarrow V_o = V_i$   
 For  $V_R \leq V_i \Rightarrow \text{diode is ON} \Rightarrow V_o = 5 \text{ V}$   
 Hence output waveform can be as shown below




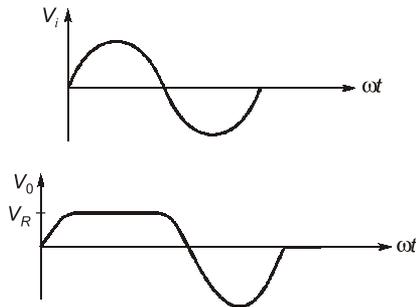**6. (c)**


For  $V_i < V_R = \text{Diode is OFF} \Rightarrow V_o = V_i$   
 For  $V_i > V_R = \text{Diode is ON} \Rightarrow V_o \approx V_R$   
 Hence for a sinusoidal input, output can be shown as below



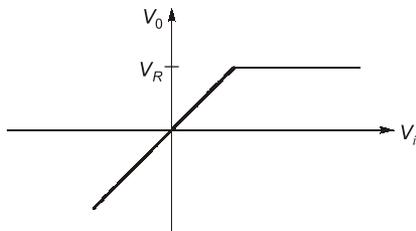Hence characteristic can be as shown below




**7. (b)**

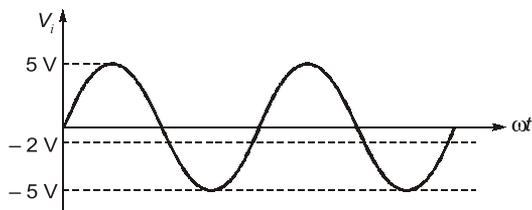


Hence given circuit acts as a clamper, sine wave clamped at  $-2 \text{ V}$ .

**8. (b)**

For positive half cycle:

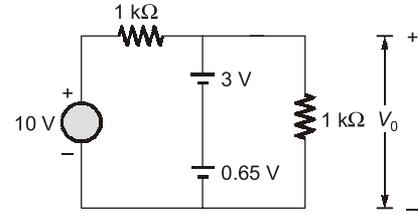

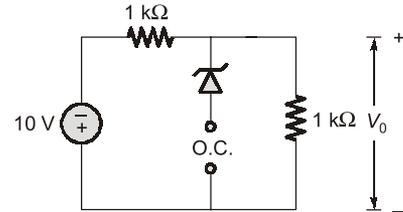
So,  $V_o = 3.65 \text{ V}$   
 In negative half cycle:



So,  $V_o = -5 \text{ V}$

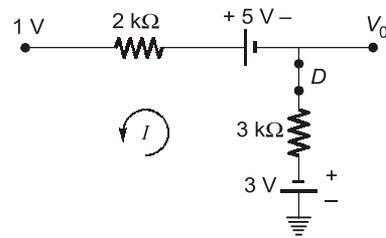**9. (a)**

$\therefore$  Diode is forward bias (short circuit)




By applying KVL,  
 $3 \text{ V} + 3 \text{ k}\Omega I - 5 \text{ V} + 2 \text{ k}\Omega I + 1 \text{ V} = 0$

$$I = \frac{1 \text{ V}}{5 \text{ k}\Omega} = \frac{1}{5} \text{ mA}$$


$$\therefore V_o = -3 - 3 \times \frac{1}{5} = -\frac{18}{5} \text{ V}$$

**10. (a)**

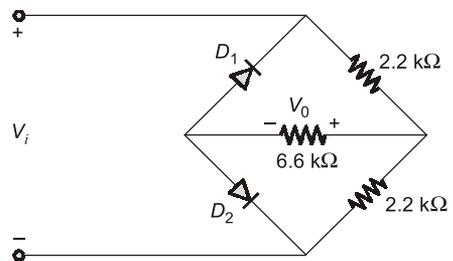


For positive half cycle of input voltage,

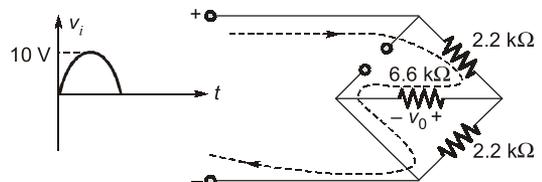$D_1 \rightarrow \text{OFF}$   
 $D_2 \rightarrow \text{ON}$




$$V_{O_{max}} = \frac{[6.6 \text{ k}\Omega \parallel 2.2 \text{ k}\Omega]}{2.2 \text{ k}\Omega + [6.6 \text{ k}\Omega \parallel 2.2 \text{ k}\Omega]} V_{i_{max}}$$
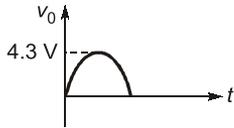
$$= \frac{0.75}{1 + 0.75} \times 10 \text{ V} = 4.3 \text{ V}$$




For negative half cycle of input voltage

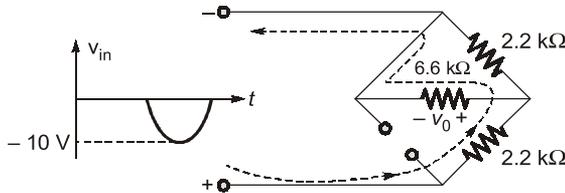


$$V_{O_{max}} = \frac{[6.6 \text{ k}\Omega \parallel 2.2 \text{ k}\Omega]}{2.2 \text{ k}\Omega + [6.6 \text{ k}\Omega \parallel 2.2 \text{ k}\Omega]} V_{i_{max}}$$
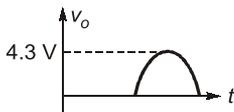
$$= \frac{0.75}{1 + 0.75} \times 10 \text{ V} = 4.3 \text{ V}$$



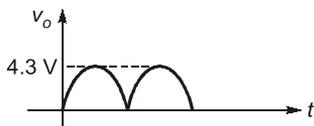Still the polarity of output voltage is in the same direction. So, net output of the circuit will be a full rectified wave.



11. (c)

The given circuit is a voltage doubler. Hence,

$$V_o = 2 V_m$$

12. (d)

When  $D_2$  is ON then the value of  $V_o$  will be

$$V_o = 3 - 0.7 \text{ V} = 2.3 \text{ V}$$


Hence,  $D_1$  will be OFF.

Thus, The current,

$$I = \frac{2.3 - (-3)}{5} \times 10^{-3}$$

$$= \frac{5.3}{5} \times 10^{-3} = 1.06 \text{ mA}$$

13. (4)

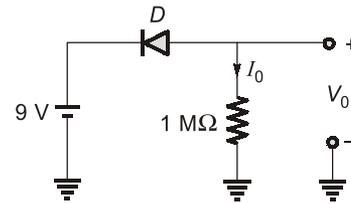

Calculating the value of reverse saturation current ( $I_{01}$ ) flowing through the diode at  $20^\circ\text{C}$   
We get,

$$I_{01} = \frac{V_o}{1 \text{ M}\Omega} = 1 \mu\text{A} \quad (\text{for } V_o = 1 \text{ V})$$

The reverse saturation current doubles for every  $10^\circ$  rise in temperature. Hence, the rise in temperature.

$$\Delta T = (40^\circ - 20^\circ)\text{C} = 20^\circ \text{C}$$


Thus,  $I_{02} = I_{01} 2^{(\Delta T/10)}$   
(where  $I_{02}$  is reverse saturation current at  $40^\circ\text{C}$ )

$$= (1 \mu\text{A}) \times 2^{(20/10)} = 4 \mu\text{A}$$

Hence,  $V_o = I_{02} \times 1 \times 10^6 = 4 \text{ V}$

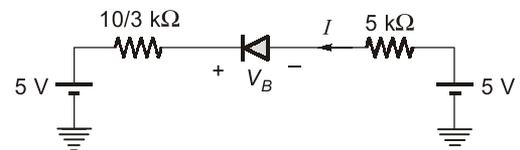14. (0)


Drawing the Thevenin equivalent circuit, we get



Applying KVL we get  $V_D = 0 \text{ V}$ , thus no current will flow through the diode  $D_1$ .

Hence,  $I = 0 \text{ A}$

15. (d)

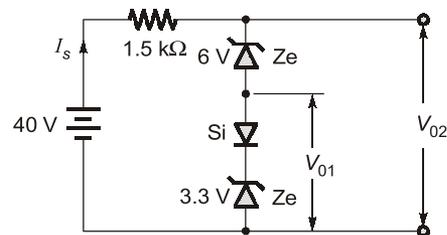

Cut in voltage of Si diode

$$= 0.7 \text{ V}$$


So  $V_{01} = 0.7 \text{ V} + 3.3 \text{ V} = 4.0 \text{ V}$

$$V_{02} = 6 \text{ V} + 4 \text{ V} = 10 \text{ V}$$

$$\therefore I_s = \frac{40 \text{ V} - 10 \text{ V}}{1.5 \text{ k}\Omega} = 20 \text{ mA}$$

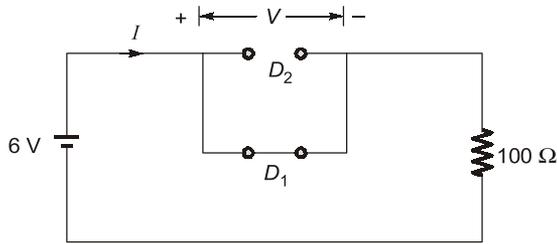**16. (a)**

In the given circuit, only the ideal germanium diode ( $D_1$ ) will be in ON state and  $D_2$  will be in OFF state. So, the equivalent circuit can be drawn as given below:



From the above equivalent circuit,  
 $V = 0 \text{ V}$

and  $I = \frac{6}{100} \text{ A} = 60 \text{ mA}$


**17. (a)**

1. A clamper clamps a signal to a different dc level.
2. The total swing of the output signal is equal to the total swing of input signal.
3. The shape of signal does not change; only dc level shifts.
4. The use of capacitor is essential in clamper circuit.

**18. (c)**

In order to rectify sinusoidal signals of millivolt range we use a precision rectifier. In precision rectifier a diode is to be inserted in the feedback loop of an OP-AMP.

**19. (c)**

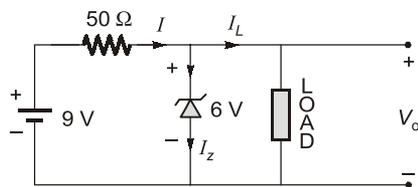

$$I = \frac{9-6}{50} = \frac{3}{50} = 60\text{mA}$$

Now when load current is maximum then

$$I_z = I_{\text{knee}}$$

$$\therefore I_{\text{knee}} + I_{L_{\text{max}}} = I$$

$$\Rightarrow 5 \text{ mA} + I_{L_{\text{max}}} = 60 \text{ mA}$$

$$\Rightarrow I_{L_{\text{max}}} = 55 \text{ mA}$$

Now maximum power dissipation in zener diode is

$$P_{Z_{\text{max}}} = V_z I_{Z_{\text{max}}}$$

$$\therefore I_{Z_{\text{max}}} = \frac{300\text{mW}}{6} = 50\text{mA}$$


When  $I_z$  is maximum, then  $I_L$  will be minimum

$$\therefore I_{Z_{\text{max}}} + I_{L_{\text{min}}} = 60 \text{ mA}$$

$$\therefore I_{L_{\text{min}}} = 60 \text{ mA} - I_{Z_{\text{max}}} = 60 - 50 = 10 \text{ mA}$$

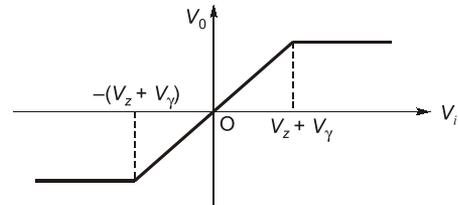**20. (a)**

The transfer characteristic of the given circuit is shown below:



Hence  $V_o = V_i$  for  $|V_i| \leq V_z + V_y$   
 $= 5 + 0.6 = 5.6 \text{ V}$

**21. (c)**

The stabilized output is dependent on zener breakdown voltage and can not be varied.

**22. (d)**

The presence of the capacitor causes the peak inverse voltage to increase from a value equal to the transformer maximum when no capacitor filter is used to a value equal to twice the transformer maximum value when the filter is used.

Hence, Maximum voltage across the diode

$$= 2 \times 10 \times \sqrt{2} = 28.28 \approx 28 \text{ V}$$

**23. (c)**

$$V_{\text{rms}} = \frac{V_m}{\sqrt{2}} = \frac{200}{\sqrt{2}} \text{ V}$$

Hence power dissipated in the load resistor is

$$P = \frac{V_{\text{rms}}^2}{R_L} = \frac{(200/\sqrt{2})^2}{50} = \frac{200 \times 200}{2 \times 50} = 400 \text{ W}$$

**24. (b)**

$$\text{Ripple factor} = \sqrt{\left(\frac{V_{\text{rms}}}{V_{\text{dc}}}\right)^2 - 1} = \sqrt{\left(\frac{I_{\text{rms}}}{I_{\text{dc}}}\right)^2 - 1}$$

**25. (b)**

