



POSTAL BOOK PACKAGE 2024

CONTENTS

INSTRUMENTATION ENGINEERING

Objective Practice Sets


Analog Electronics

1. Diode Circuit and Power Supply 2 - 16
2. BJT Biasing and Thermal Stabilization 17 - 29
3. FET and MOSFET Circuit 30 - 38
4. Frequency Response and Multistage Amplifiers 39 - 54
5. Feedback Amplifiers 55 - 61
6. Oscillators 62 - 68
7. Operational Amplifiers 69 - 85
8. Sources and Effects of Noise
and Interference in Electronic Circuits 86 - 87
9. Miscellaneous 88 - 92



Diode Circuit and Power Supply

MCQ and NAT Questions

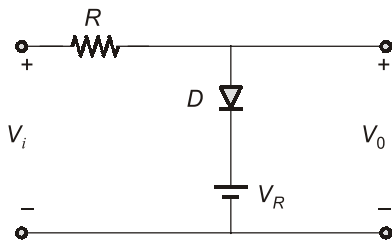
- Q.1** The voltage across diode at temperature T_1 is 0.76 V. If temperature is increased by 20°C at constant current the new voltage across diode is
 (a) 0.65 V (b) 0.81 V
 (c) 0.71 V (d) 0.7 V
- Q.2** A diode whose terminal characteristics are related as $i_D = I_s e^{V/V_T}$, where I_s is the reverse saturation current and V_T is thermal voltage ($V_T = 25\text{ mV}$), is biased at $I_D = 4\text{ mA}$. Its dynamic resistance is
 (a) $12.5\ \Omega$ (b) $50\ \Omega$
 (c) $6.25\ \Omega$ (d) $25\ \Omega$
- Q.3** In the circuit shown below the input V_i has positive and negative swings. V_o is the output.



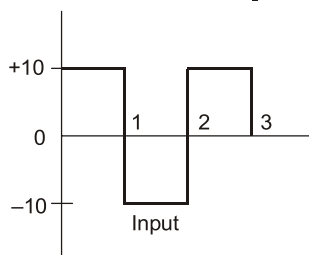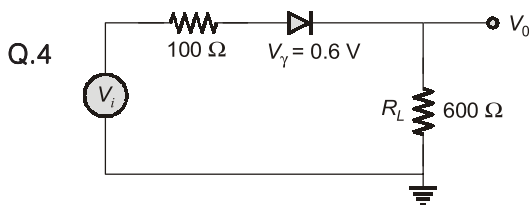
- (a) $V_o = 0$ for negative V_i
 (b) $V_o = V_R$ for positive V_i
 (c) $V_o = V_R$ for $V_i > V_R$
 (d) $V_o = V_R$ for all V_i



The output waveform is

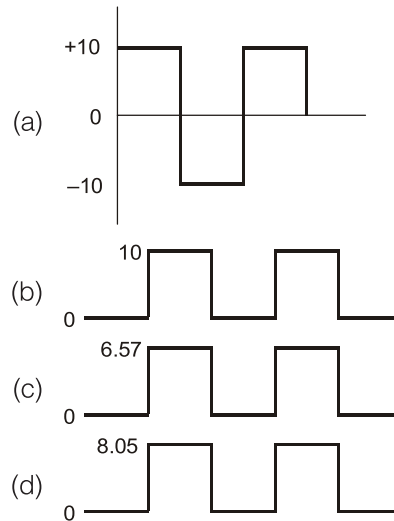


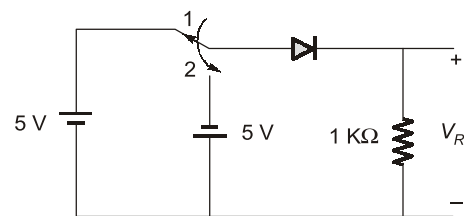
- Q.5** In the circuit shown below, the switch was connected to position 1 at $t < 0$ and at $t = 0$, it is changed to position 2. Assume that the diode has zero voltage drop and a storage time t_s . For $0 < t \leq t_s$, V_R is given by (all in Volts)






- (a) $V_R = -5$ (b) $V_R = 0$
 (c) $0 \leq V_R < 5$ (d) $-5 < V_R < 0$

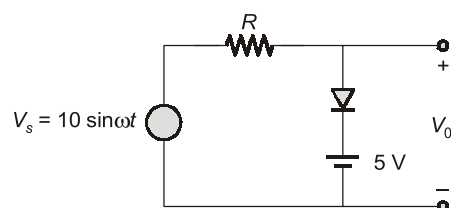- Q.6** For the circuit shown below assuming ideal diode, the output waveform V_o is




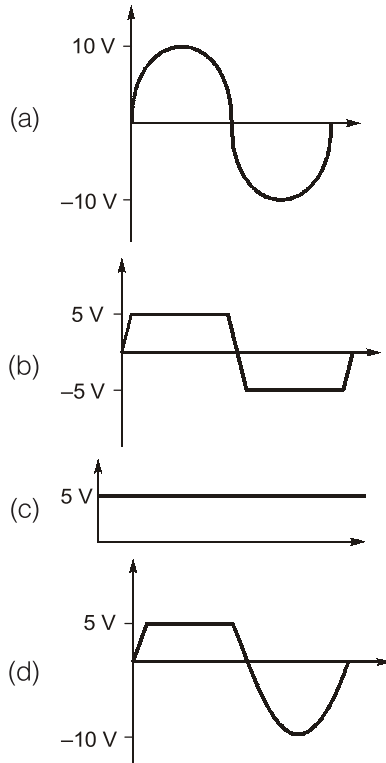

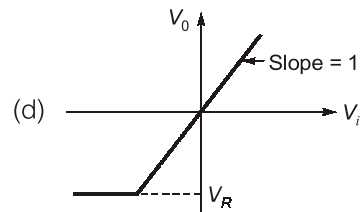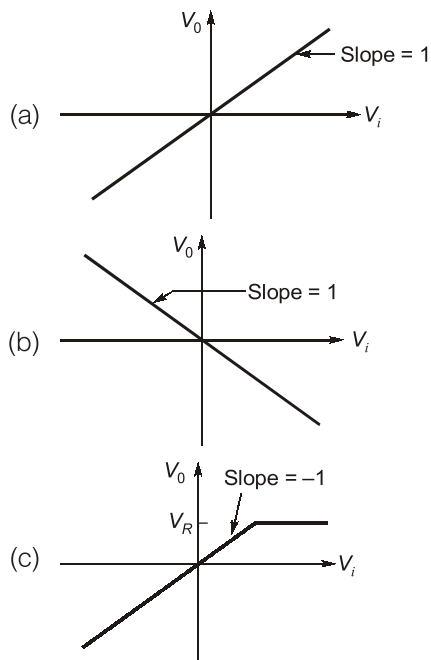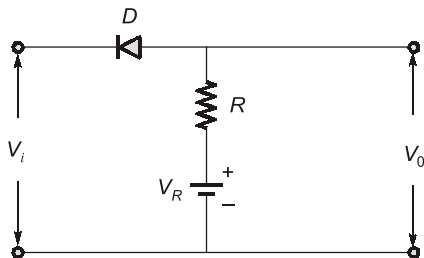Q.7 The transfer characteristic of the network shown below is represented as




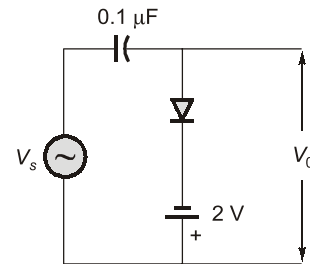Q.8 For an input of $V_s = 5 \sin \omega t$, (assuming ideal diode), circuit shown below will behave as a




- (a) clipper, sine wave clipped at -2 V
- (b) clamper, sine wave clamped at -2 V
- (c) clamper, sine wave clamped at zero volt
- (d) clipper, sine wave clipped at 2 V

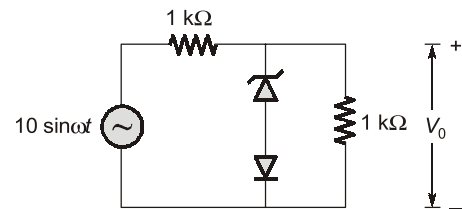Q.9 The cut-in voltage of both Zener diode D_z and D shown in figure is 0.65 V , while breakdown voltage of the Zener is 3 V . Diode is considered to be ideal. The value of peak output voltage V_o .



- (a) 3 V in the positive half cycle and 0.65 V in the negative half cycle.
- (b) 3.65 V in the positive half cycle and -5 V in the negative half cycle.
- (c) 3 V in positive half cycle and -5 V in the negative half cycle
- (d) -3.65 V in positive half cycle and 5 V in the negative half cycle

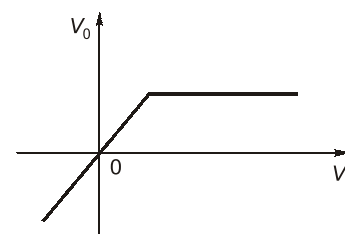Q.10 The voltage transfer characteristic as shown in the figure will relate to a




1. voltage regulator
2. half-wave rectifier
3. full-wave rectifier

Which of the above is/are correct?


- (a) 1 only (b) 2 only
(c) 1 and 2 (d) 1 and 3

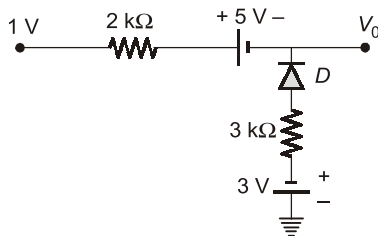Q.11 What is the output voltage V_0 for the circuit shown below assuming an ideal diode?





- (a) $-\frac{18}{5}$ V (b) $\frac{18}{5}$ V
(c) $-\frac{13}{5}$ V (d) $\frac{13}{5}$ V

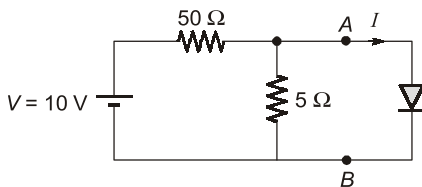Q.12 What is the value of current I through the ideal diode in the circuit?




- (a) 100 mA (b) 150 mA
(c) 200 mA (d) 250 mA

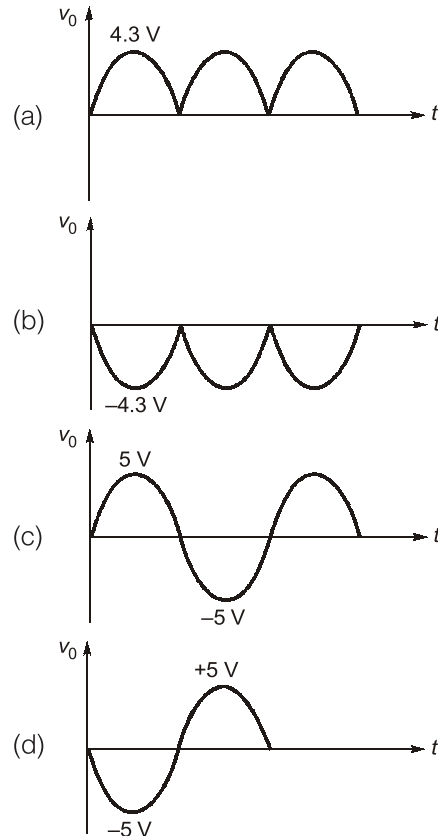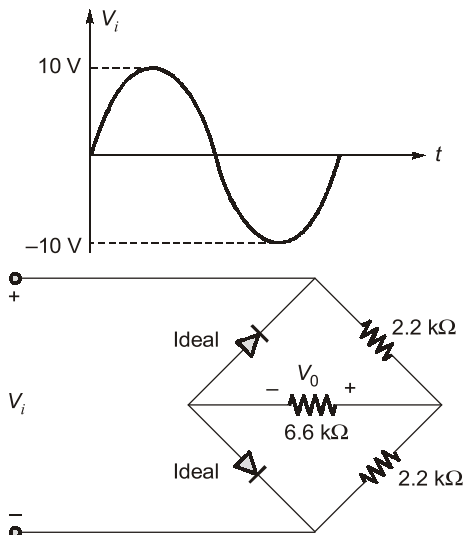Q.13 The correct waveform for output (V_0) for below network is




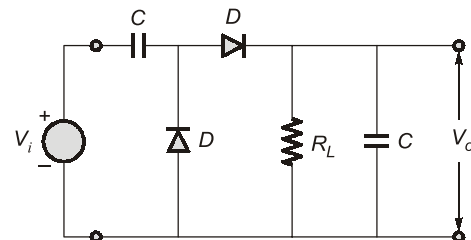Q.14 Consider the below circuit, for $V_i = V_m \sin \omega t$, the output voltage V_0 for $R_L \rightarrow \infty$ will be



- (a) Zero (b) V_m
(c) $2 V_m$ (d) $-V_m$

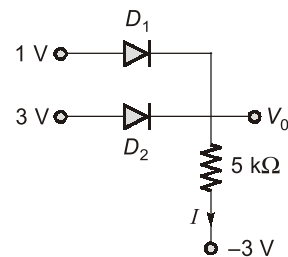
Q.15 Consider the circuit shown in the figure below



If diode D_1 and D_2 are made up of same material with the cut-in voltage $V_\gamma = 0.7$ V, then the value of current I is equal to


- (a) 0.46 mA (b) 0.99 mA
(c) 0.59 mA (d) 1.06 mA

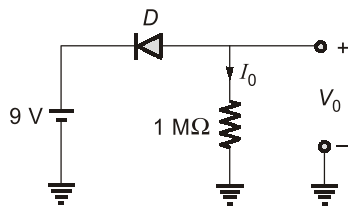Q.16 Consider the diode circuit shown in the figure below:




The diode in the circuit is a large high-current silicon device whose reverse leakage current is reasonably independent of voltage appearing on the diode. If $V_0 = 1$ V at 20°C , then the value of output voltage at 40°C is equal to _____ V.

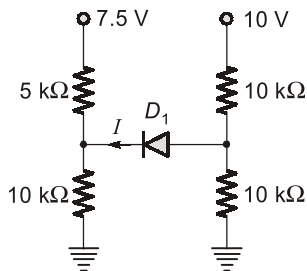Q.17 Consider the circuit shown in the figure below



If the cut-in voltage of the diode D_1 is equal to 0.7 V, then the value of current flowing through the diode is equal to _____ mA.

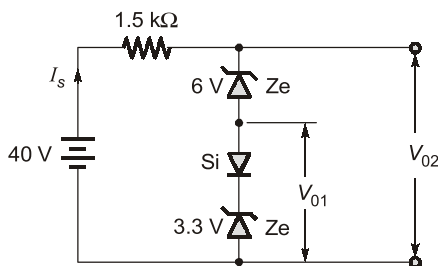Q.18 A 40 V dc supply is connected across the network comprising of Zener and Silicon diodes as shown. The regulated voltages V_{01} , V_{02} and source current I_s are




- (a) 2.4 V, 5.1 V and 21.7 mA
- (b) 3 V, 6 V and 22.7 mA
- (c) 3.3 V, 9.3 V and 20.5 mA
- (d) 4 V, 10 V and 20 mA

Q.19 A 700 mW maximum power dissipation diode at 25°C has 5 mW/ $^\circ\text{C}$ de-rating factor. If the forward voltage drop remains constant at 0.7 V, the maximum forward current at 65°C is

- (a) 700 mA
- (b) 714 mA
- (c) 1 A
- (d) 1 mA

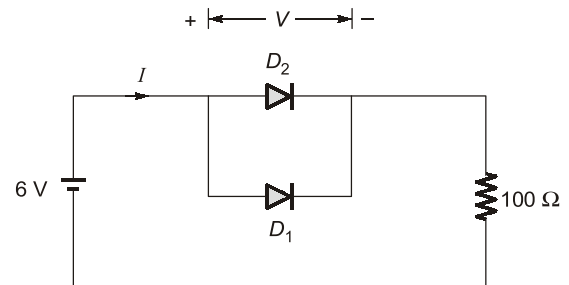Q.20 In the given circuit, D_1 is an ideal germanium diode and D_2 is a silicon diode having its cut-in voltage as 0.7 V, forward resistance as $20\ \Omega$ and reverse saturation current (I_s) as 10 nA. What are the values of I and V for this circuit, respectively?



- (a) 60 mA and 0 V
- (b) 50 mA and 0 V
- (c) 53 mA and 0.7 V
- (d) 44 mA and 1.58 V

Q.21 Consider the following statements :
A clamper circuit

1. adds/subtracts a dc voltage to/from a waveform.
2. does not change the shape of the waveform.
3. amplifies the waveform.


Of these statements

- (a) 1 & 2 are correct
- (b) 1 & 3 are correct
- (c) 2 & 3 are correct
- (d) 1, 2 & 3 are correct


Q.22 In order to rectify sinusoidal signals of millivolt range (< 0.6 V)

- (a) bridge rectifier using diodes can be employed
- (b) full-wave diode rectifier can be used
- (c) a diode is to be inserted in the feedback loop of an OP-AMP
- (d) a diode is to be inserted in the input of an OP-AMP

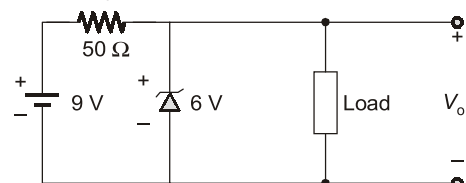Q.23 A Zener diode in the circuit shown below has a knee current of 5 mA, and a maximum allowed power dissipation of 300 mW. What are the minimum and maximum load currents that can be drawn safely from the circuit, keeping the output voltage V_o constant at 6 V?




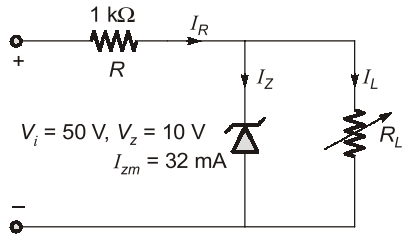- (a) 0 mA, 180 mA
- (b) 5 mA, 110 mA
- (c) 10 mA, 55 mA
- (d) 60 mA, 180 mA



- (a) $R_{L \min} = 250 \Omega$ (b) $I_{L \min} = 8 \text{ mA}$
(c) $R_{L \max} = 1.25 \text{ k}\Omega$ (d) $I_R = 40 \text{ mA}$


Q.50 For the circuit shown below :

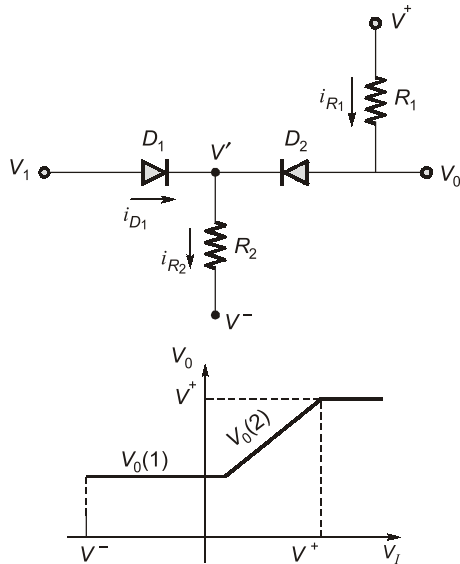

Assume the circuit parameters are $R_1 = 5 \text{ k}\Omega$, $R_2 = 10 \text{ k}\Omega$, $V_\gamma = 0.7 \text{ V}$, $V^+ = +5 \text{ V}$ and $V^- = -5 \text{ V}$

- (a) For $V_1 = 0$, $i_{R1} = 0.62 \text{ mA}$
(b) For $V_1 = 4 \text{ V}$, $i_{R1} = 0.2 \text{ mA}$
(c) For $V_1 = 4 \text{ V}$, $i_{R2} = 0.83 \text{ mA}$
(d) For $V_1 = 4 \text{ V}$, $i_{D1} = 0.63 \text{ mA}$


Q.51 For the circuit shown below :

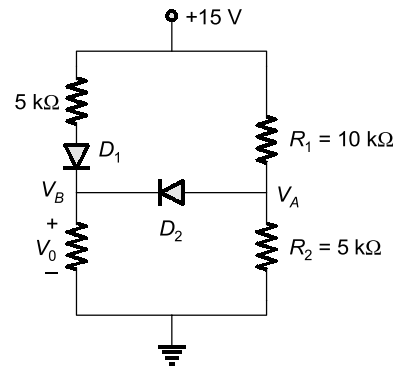

Which of the following are correct?

- (a) $V_A = 7.62 \text{ V}$ (b) $V_B = 6.92 \text{ V}$
(c) $V_A = 5 \text{ V}$ (d) $V_B = 9.53 \text{ V}$

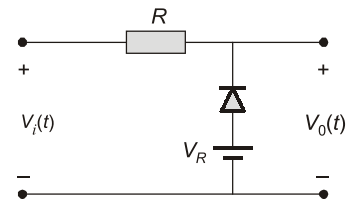Q.52 Assuming ideal diode characteristics, the input/output voltage relationship for the circuit shown in figure is



- (a) When $V_i(t) \leq V_R$: $V_0 = V_R$
(b) When $V_i(t) \leq V_R$: $V_0 = V_i(t)$
(c) When $V_i(t) > V_R$: $V_0 = V_R$
(d) When $V_i(t) > V_R$: $V_0 = V_i(t)$

■■■■

Answers Diode Circuit and Power Supply

- | | | | | | | |
|------------------|------------|------------|---------|---------|------------|------------------|
| 1. (c) | 2. (c) | 3. (c) | 4. (d) | 5. (a) | 6. (d) | 7. (c) |
| 8. (b) | 9. (b) | 10. (a) | 11. (a) | 12. (c) | 13. (a) | 14. (c) |
| 15. (d) | 16. (4) | 17. (0) | 18. (d) | 19. (b) | 20. (a) | 21. (a) |
| 22. (c) | 23. (c) | 24. (a) | 25. (c) | 26. (b) | 27. (d) | 28. (c) |
| 29. (b) | 30. (b) | 31. (a) | 32. (d) | 33. (c) | 34. (a) | 35. (c) |
| 36. (c) | 37. (d) | 38. (c) | 39. (d) | 40. (b) | 41. (c) | 42. (b) |
| 43. (d) | 44. (b) | 45. (d) | 46. (c) | 47. (c) | 48. (c, d) | 49. (a, b, c, d) |
| 50. (a, b, c, d) | 51. (c, d) | 52. (a, d) | | | | |

Explanations Diode Circuit and Power Supply

1. (c)

$$\frac{dV_D}{dT} = -2.5 \text{ mV/}^\circ\text{C}$$

$$\Delta V_D = 20 \times (-2.5 \text{ mV}) = -0.05 \text{ V}$$

$$\therefore V_D + \Delta V_D = V_2 = 0.71 \text{ V}$$


2. (c)

$$\frac{1}{r_d} = \frac{\partial I_D}{\partial V} = \frac{I_D}{V_T}$$

r_d : dynamic resistance.

$$\therefore r_d = \frac{V_T}{I_D} = \frac{25}{4} = 6.25 \Omega$$

3. (c)

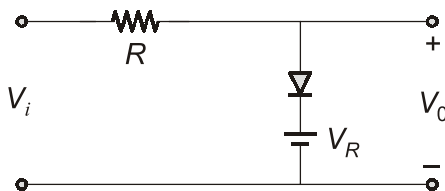

Considering ideal diode :

for $V_i < V_R$, diode is OFF hence there is no current through R and $V_0 = V_i$.


For $V_i > V_R$, diode is ON hence

$$V_0 = V_R$$

(as diode will act as short circuit)

4. (d)

For $0 \leq t \leq 1$, diode is ON

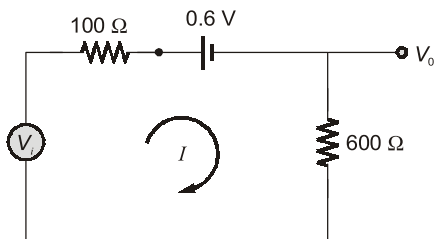

$$I = \frac{V_i - 0.6}{100 + 600} = \frac{10 - 0.6}{700}$$

$$= 0.01343 \text{ A}$$

$$\therefore V_0 = 600 \times 0.01343 = 8.058 \text{ V}$$

for $1 < t < 2$, diode is OFF, there will be no current in the circuit and hence

$$V_0 = 0 \text{ V}$$

Hence output waveform can be given as shown below:



5. (a)

For $0 < t < t_s$ diode will remain ON and hence

$$V_R + 5 = 0$$


$$\therefore V_R = -5 \text{ V}$$

6. (d)

For $0 \leq V_i < V_R$ diode is OFF $\Rightarrow V_0 = V_i$

For $V_R \leq V_i \Rightarrow$ diode is ON $\Rightarrow V_0 = 5 \text{ V}$

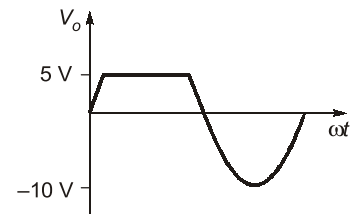Hence output waveform can be as shown below




7. (c)


For $V_i < V_R$ Diode is OFF $\Rightarrow V_0 = V_i$

For $V_i > V_R$ Diode is ON $\Rightarrow V_0 \simeq V_R$

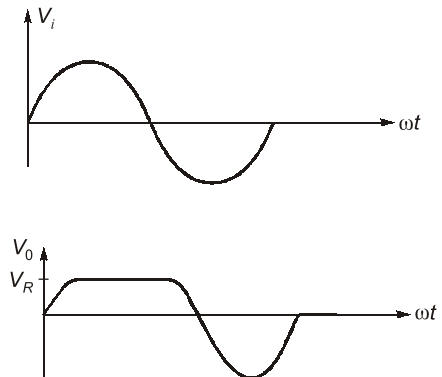
Hence for a sinusoidal input, output can be shown as below



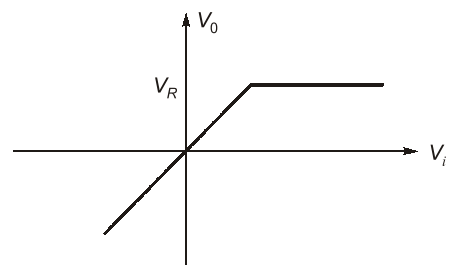Hence characteristic can be as shown below




8. (b)

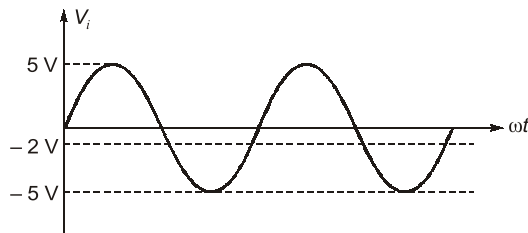

Hence given circuit acts as a clamper, sine wave clamped at -2 V .


9. (b)

For positive half cycle:

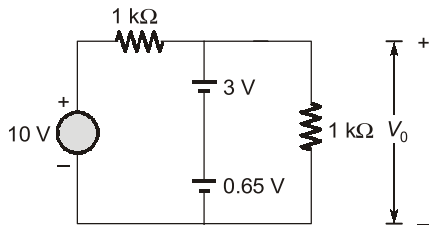

So, $V_o = 3.65\text{ V}$


In negative half cycle:

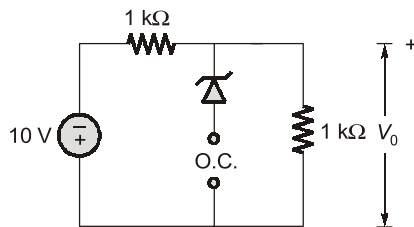

So, $V_o = -5\text{ V}$

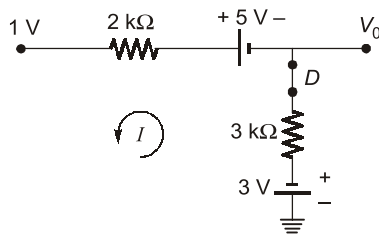11. (a)

\therefore Diode is forward bias (short circuit)



By applying KVL,

$$3\text{ V} + 3\text{ k}\Omega I - 5\text{ V} + 2\text{ k}\Omega I + 1\text{ V} = 0$$

$$I = \frac{1\text{ V}}{5\text{ k}\Omega} = \frac{1}{5}\text{ mA}$$


$$\therefore V_o = -3 - 3 \times \frac{1}{5} = -\frac{18}{5}\text{ V}$$

12. (c)

\therefore Diode is in forward bias (short circuit)

$$I = \frac{10}{50} = 0.2\text{ A} = 200\text{ mA}$$


13. (a)

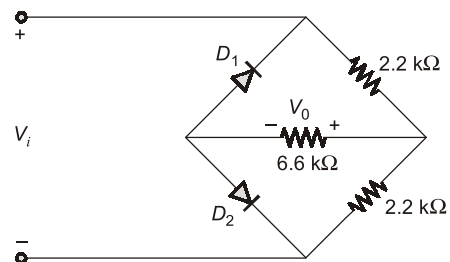

For positive half cycle of input voltage


$D_1 \rightarrow \text{OFF}$

$D_2 \rightarrow \text{ON}$

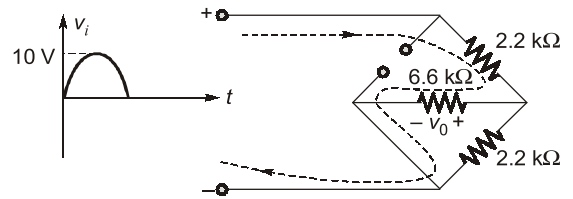


$$V_{o\max} = \frac{[6.6\text{ k}\Omega \parallel 2.2\text{ k}\Omega]}{2.2\text{ k}\Omega + [6.6\text{ k}\Omega \parallel 2.2\text{ k}\Omega]} V_{i\max}$$
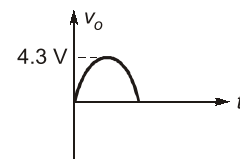
$$= \frac{0.75}{1+0.75} \times 10\text{ V} = 4.3\text{ V}$$




For negative half cycle of input voltage

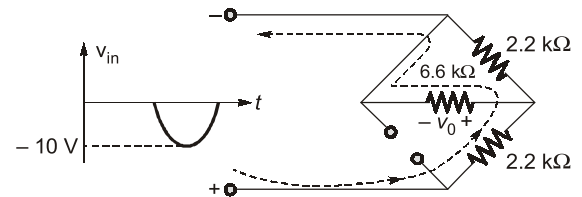

$$V_{o\max} = \frac{[6.6\text{ k}\Omega \parallel 2.2\text{ k}\Omega]}{2.2\text{ k}\Omega + [6.6\text{ k}\Omega \parallel 2.2\text{ k}\Omega]} V_{i\max}$$
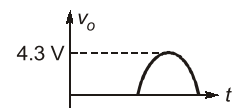
$$= \frac{0.75}{1+0.75} \times 10\text{ V} = 4.3\text{ V}$$



Still the polarity of output voltage is in the same direction. So, net output of the circuit will be a full rectified wave.

