

# INSTRUMENTATION ENGINEERING

## ANALOG ELECTRONICS



Comprehensive Theory  
*with Solved Examples and Practice Questions*





**MADE EASY Publications Pvt. Ltd.**

**Corporate Office:** 44-A/4, Kalu Sarai (Near Hauz Khas Metro Station), New Delhi-110016 | **Ph. :** 9021300500

**Email :** infomep@madeeasy.in | **Web :** www.madeeasypublications.org

## Analog Electronics

Copyright © by MADE EASY Publications Pvt. Ltd.  
All rights are reserved. No part of this publication may be reproduced, stored in or introduced into a retrieval system, or transmitted in any form or by any means (electronic, mechanical, photo-copying, recording or otherwise), without the prior written permission of the above mentioned publisher of this book.



**MADE EASY Publications Pvt. Ltd.** has taken due care in collecting the data and providing the solutions, before publishing this book. In spite of this, if any inaccuracy or printing error occurs then **MADE EASY Publications Pvt. Ltd.** owes no responsibility. We will be grateful if you could point out any such error. Your suggestions will be appreciated.

## EDITIONS

First Edition : 2015  
Second Edition : 2016  
Third Edition : 2017  
Fourth Edition : 2018  
Fifth Edition : 2019  
Sixth Edition : 2020  
Seventh Edition : 2021  
Eighth Edition : 2022  
Ninth Edition : 2023  
Tenth Edition : 2024  
**Eleventh Edition : 2025**

# CONTENTS

## Analog Electronics

### CHAPTER 1

#### Diode Circuits ..... 4-77

1.1	Introduction .....	4
1.2	Diode Circuits : DC Analysis and Models.....	4
1.3	Diode Logic Gates .....	10
1.4	Diode Equivalent Circuits .....	12
1.5	DC Power Supply .....	15
1.6	Rectifier .....	16
1.7	Half-wave Rectifier .....	16
1.8	Centre-Tapped Full-wave Rectifier .....	25
1.9	Bridge Rectifier .....	32
1.10	Comparison of Rectifier Circuits with Resistive Load.....	35
1.11	Filter.....	35
1.12	Inductor Filter .....	36
1.13	Capacitor Filter .....	37
1.14	LC Filter (L-Section Filter) .....	40
1.15	CLC Filter (II-Section Filter) .....	43
1.16	Voltage Regulators.....	44
1.17	Zener Diode Shunt Regulator .....	45
1.18	Op-amp Controlled Series Regulator .....	47
1.19	Transistorized Series Regulator .....	48
1.20	Fixed Voltage IC Regulators .....	51
1.21	Wave Shaping .....	52
1.22	Clipper .....	52
1.23	Linear Wave Shaping.....	59
1.24	Clamper.....	65
1.25	Voltage Multiplier .....	69
	Objective Brain Teasers.....	71
	Conventional Brain Teasers.....	75

### CHAPTER 2

#### Bipolar Junction Transistors-Characteristics and Biasing.....78-97

2.1	Introduction .....	78
2.2	Transistors Current Components .....	80
2.3	Early Effect.....	84
2.4	BJT Configuration .....	85
2.5	The Common Base Configuration .....	86
2.6	The Common-Emitter Configuration .....	89
2.7	The Common-Collector Configuration.....	91
	Objective Brain Teasers.....	92
	Conventional Brain Teasers.....	95

### CHAPTER 3

#### Transistor Biasing and Thermal Stabilization .....98-131

3.1	Introduction .....	98
3.2	The Operating Point .....	98
3.3	Instability in Collector Current.....	100
3.4	BJT Biasing .....	103
3.5	Fixed Bias Circuit.....	104
3.6	Collector to Base Bias Circuit.....	105
3.7	Self-Bias, Emitter Bias, or Voltage-Divider Bias.....	106
3.8	Bias Compensation .....	110
3.9	Thermal Runaway.....	112
3.10	BJT Biasing in Integrated Circuits (ICs).....	116
3.11	Constant Current Source (Basic Current Mirror).....	117
3.12	Widlar Current Source.....	119
3.13	Current Repeaters.....	121
3.14	Wilson Current Source .....	123
	Objective Brain Teasers.....	124
	Conventional Brain Teasers.....	127

**CHAPTER 4****BJT as an Amplifier ..... 132-172**

4.1	Introduction .....	132
4.2	Graphical Analysis of BJT Amplifier.....	133
4.3	Transistor Hybrid Model.....	134
4.4	Analysis of Transistor Amplifier Circuit Using h-Parameters .....	136
4.5	Small Signal Hybrid- $\Pi$ Equivalent Circuit of BJT .....	141
4.6	Hybrid- $\Pi$ -Equivalent Circuit, by Considering Early Effect .....	143
4.7	Basic Transistor Amplifier Configurations.....	144
4.8	Common-Emitter Amplifiers .....	145
4.9	Common-Collector (Emitter-Follower) Amplifier.....	153
4.10	Common-Base Amplifier.....	158
4.11	Multistage Amplifiers.....	160
	<i>Objective Brain Teasers</i> .....	164
	<i>Conventional Brain Teasers</i> .....	167

**CHAPTER 5****Basic FET Amplifiers ..... 173-194**

5.1	Introduction .....	173
5.2	The Common-Source Amplifier.....	173
5.3	Common-Drain (Source Follower) Amplifier .....	179
5.4	The Common-Gate Configuration.....	183
	<i>Objective Brain Teasers</i> .....	189
	<i>Conventional Brain Teasers</i> .....	192

**CHAPTER 6****Frequency Response ..... 195-225**

6.1	Introduction .....	195
6.2	Amplifier Frequency Response.....	195
6.3	Miller's Theorem.....	202
6.4	Frequency Response : BJT .....	204
6.5	High Frequency Response of Common-Emitter and Common-Source Circuits.....	209

6.6	High Frequency Response of Common-Base.....	213
6.7	High Frequency Response of Emitter.....	216
	<i>Objective Brain Teasers</i> .....	219
	<i>Conventional Brain Teasers</i> .....	222

**CHAPTER 7****Differential Amplifiers..... 226-238**

7.1	Introduction .....	226
7.2	The Differential Amplifier .....	226
7.3	Basic BJT Differential Amplifier .....	227
7.4	FET Differential Amplifiers.....	232
7.5	Constant Current-Bias.....	233
7.6	Level Translator.....	236
	<i>Objective Brain Teasers</i> .....	237

**CHAPTER 8****Feedback Amplifiers ..... 239-259**

8.1	Introduction .....	239
8.2	Basic Feedback Concepts .....	239
8.3	General Block Diagram of Feedback Amplifier.....	243
8.4	Four Basic Feedback Topologies .....	246
8.5	Series-Shunt Configuration .....	246
8.6	Shunt-Series Configuration .....	249
8.7	Series-Series Configuration.....	250
8.8	Shunt-Shunt Configuration .....	251
8.9	Summary of Results.....	252
	<i>Objective Brain Teasers</i> .....	255
	<i>Conventional Brain Teasers</i> .....	258

**CHAPTER 9****Operational Amplifier ..... 260-302**

9.1	Introduction.....	260
9.2	Block Diagram Representation of A Typical Op-Amp ...	260
9.3	Schematic Symbol .....	261

9.4	Operational Amplifier Characteristics .....	261
9.5	DC Characteristics .....	262
9.6	AC Characteristics .....	264
9.7	Characteristics of Ideal Op-Amp.....	267
9.8	Ideal Voltage Transfer Curve .....	267
9.9	Inverting Amplifier .....	268
9.10	Summing Amplifier .....	273
9.11	Non-inverting Amplifier .....	275
9.12	Voltage Follower .....	277
9.13	Current-to-Voltage Converter .....	278
9.14	Voltage-to-Current Converter .....	279
9.15	Differential Amplifier .....	279
9.16	Integrator and Differentiator .....	282
9.17	Instrumentation Amplifier .....	284
9.18	Log Amplifier .....	286
9.19	Antilog or Exponential Amplifier.....	288
9.20	Analog Multiplier IC's (Modulator).....	289
9.21	Analog Divider IC's (De-Modulator) .....	289
9.22	Precision Diode.....	290
9.23	Half-Wave Rectifier .....	291
9.24	Full-Wave Rectifier .....	292
	<i>Objective Brain Teasers</i> .....	293
	<i>Conventional Brain Teasers</i> .....	298

## CHAPTER 10

### Signal Generators and Waveform Shaping Circuits..... 303-341

10.1	Introduction.....	303
10.2	Oscillators .....	303
10.3	The Phase-Shift Oscillator.....	306
10.4	Wien Bridge Oscillator.....	312
10.5	LC Oscillators .....	315
10.6	Crystal Oscillators.....	320
10.7	Comparison between LC Oscillators and Crystal Oscillators.....	322

10.8	Comparator .....	323
10.9	Zero-Crossing Detector .....	324
10.10	Sample-And-Hold Circuits .....	326
10.11	Basic Inverting Schmitt Trigger.....	327
10.12	Schmitt Trigger Oscillator .....	329
10.13	Monostable Multivibrator.....	331
10.14	The 555 Circuit .....	332
	<i>Objective Brain Teasers</i> .....	339

## CHAPTER 11

### Active Filters and VCO..... 342-369

11.1	introduction .....	342
11.2	Classification of Active Filters.....	342
11.3	Butterworth Filter .....	344
11.4	Band Pass Filters.....	348
11.5	Band Stop Filter .....	351
11.6	All Pass Filter .....	353
11.7	Sallen-Key (VCVS) Filters .....	357
11.8	Voltage-Controlled Oscillators.....	365
11.9	Mathematical Model of VCOs.....	366

## CHAPTER 12

### Sources and Effects of Noise and Interference in Electronic Circuits..... 370-394

12.1	Noise .....	370
12.2	Statistical Characteristics of Noise.....	370
12.3	Representation of Noise in Circuits.....	379
12.4	Noise in Single-Stage Amplifiers.....	386
12.5	Noise in Differential Pairs.....	390
12.6	Noise-Power Trade-Off .....	392
12.7	Noise Bandwidth .....	393
12.8	Problem of Input Noise Integration .....	394

■■■■

# ANALOG ELECTRONICS

## Introduction to Analog Electronics

After studying the basic electronic devices and their characteristics, now we shall deal with more complex analog circuits, of which amplifiers is a very significant category. We shall start our analysis with applications of diode, a very fundamental component, in various circuit configurations such as clipper, clamper, regulator etc. Further, we shall proceed to applications of BJT and FET, particularly as an amplifier.

The other complex analog circuits, including circuits that form operational amplifiers, are also part of this book. These circuits are composed of fundamental configurations, such as differential amplifier, constant-current source, active load, and output stage, all of which have been discussed in detail.

The major emphasis throughout the book is on developing the reader's understanding for analyzing and designing various fundamental circuits, which are always an integral part of various competitive examinations. Throughout the book, a very sequential and comprehensive approach has been used, so that a beginner can also utilize the book in very efficient manner.

# Prelude to Analog Electronics

## ELECTRONICS


Electronics is defined as the science of motion of charges in a gas, vacuum, or semiconductor. Note that the charge motion in a metal is excluded from this definition.

This definition was used early in the 20<sup>th</sup> century to separate the field of electrical engineering, which dealt with motors, generators, and wire communications, from the new field of electronic engineering, which at that time dealt with the vacuum tubes.
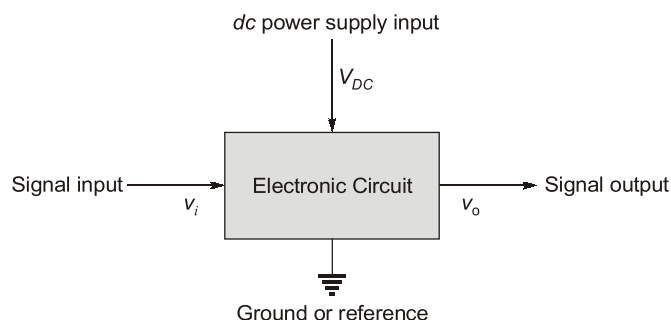
## ELECTRONIC CIRCUITS

A circuit which consists of at least one electronic device (e.g. amplifier, rectifier, oscillator etc.) is known as an electronic circuit.



In most of the electronic circuits there are two inputs. One input is from power supply which provides dc voltages and currents to establish proper biasing for transistors. The second input is a signal that can be amplified by the circuit. Although the output signal can be larger than the input signal but the output power can never exceed the dc input power. Therefore, the magnitude of dc power supply is one limitation to the output signal response.



## ANALOG AND DIGITAL SIGNALS

- The voltage signal shown graphically in Figure (a) is called an analog signal. The magnitude of an analog signal may have any value ; that is, the amplitude may vary continuously with respect to time. Electronic circuits that process such signals are called analog circuits.

- An alternative signal is at one of two distinct levels and is called a digital signal (shown in figure (b)). Because the digital signal has discrete values, it is said to be quantized. Electronic circuits that process digital signals are called digital circuits.

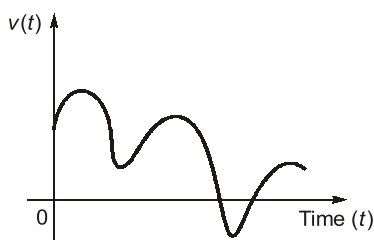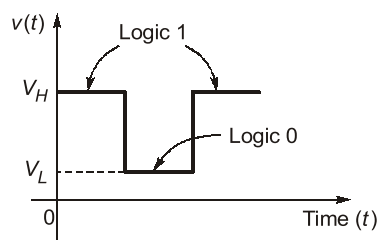**Figure (a)****Figure (b)**

### Advantages of Analog Circuits

- Majority of signals in the “real world” are analog; so these signals can be directly processed in analog circuits whereas digital processing requires analog to digital and digital to analog conversion.
- Analog circuits can be designed to operate even at higher power levels.

### Disadvantages of Analog Circuits

- Loss of information due to effect of noise is more.
- Lower quality signals than digital signals.

### Advantages of Digital Circuits

- In digital circuits effect of noise is less.
- Digital circuits can be programmed.
- Digital data can be stored.

### Disadvantages of Digital Circuits

- Expensive.
- Operate on digital signals only.
- High operational power is required.

◆◆◆◆◆



# Diode Circuits


## 1.1 INTRODUCTION

The simplest and most fundamental non-linear circuit element is a diode. Just like a resistor, the diode has two terminals; but unlike the resistor which has a linear (straight-line) relationship between the current flowing through it and the voltage appearing across it, the diode has non-linear i-v characteristics. The analysis of non-linear electronic circuits is not as straight-forward as the analysis of linear electric circuits. However, there are electronic functions that can be implemented only by non-linear circuits. Examples include the generation of dc voltages from sinusoidal voltages and the implementation of logic functions.

## 1.2 DIODE CIRCUITS : DC ANALYSIS AND MODELS

Mathematical relationships, or **models**, that describes the current-voltage characteristics of electrical elements allow us to analyze and design circuits without having to fabricate and test them in the laboratory. An example is Ohm's law, which describes the properties of a resistor. In this section, we will develop the dc analysis and modelling techniques of diode circuits.


To begin to understand diode circuits, consider an **ideal diode**. It is a two terminal device having the circuit symbol and the i-v characteristics shown in figure below.

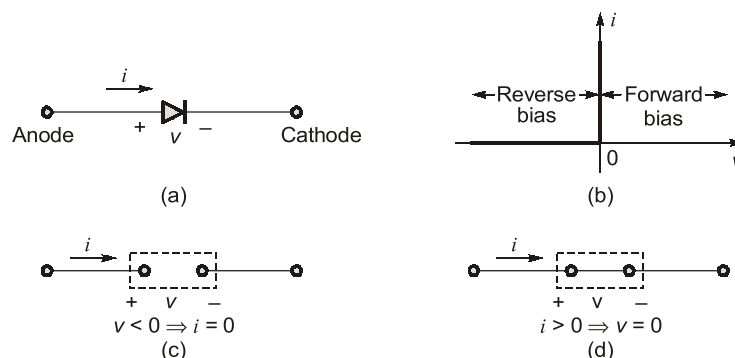

**Figure:** The ideal diode: (a) Diode circuit symbol; (b) i-v characteristics; (c) Equivalent circuit in the reverse direction (d) Equivalent circuit in the forward direction.

The terminal characteristics of the ideal diode can be interpreted to follows:


- If a negative voltage is applied to the diode, no current flows and the diode behaves as an **open circuit** [as shown in Figure (c)]. Diodes operated in this mode are said to be **reverse biased**.
- On the other hand, if a positive current is applied to the ideal diode, zero voltage drop appears across the diode. In other words the ideal diode behaves as a **short circuit** in the forward direction [as shown in Figure (d)]. Diodes operated in this mode are said to be **forward biased**

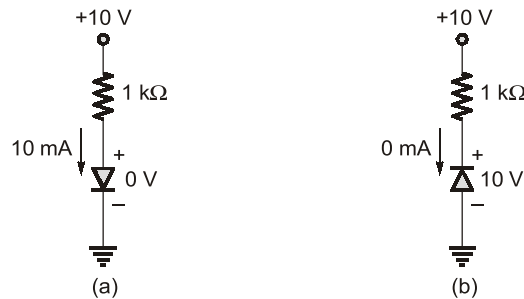

**Figure:** The two modes of operation of ideal diodes and the use of external circuit to limit  
(a) the forward current and (b) the reverse voltage

From the above description it should be noted that the external circuit must be designed to limit the forward current through a conducting diode, and the reverse voltage across a cut-off diode to predetermined values. Above figure shows two diode circuits that illustrate this point. In the circuit of Figure (a) the diode is obviously conducting. Thus its voltage drop will be zero, and the current through it will be determined by the +10 V supply and the 1 k $\Omega$  resistor as 10 mA. The diode in the circuit is obviously cut-off, and thus its current will be zero which in turn means that the entire 10 V supply will appear as reverse bias across the diode.


For practical diodes,  $i-v$  characteristics is shown in figure. When the practical diode characteristics are compared to the ideal diode characteristics, one considers the only major difference is that, during forward biased condition. Voltage drop across the diode is 0.7 V (for silicon diode) rather than 0 V, and during reverse biased condition current flows across the diode is approximately  $I_o$  (reverse saturation current in  $\mu A$ ) rather than 0 A.

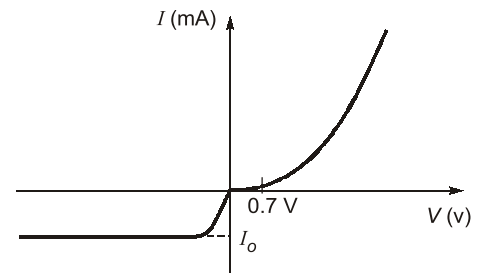

**Figure :** Practical characteristics of diode


### 1.2.1 Load-Line Analysis

The circuit of below figure is the simplest of diode configurations. Solving the circuit is all about finding the current and voltage levels that will satisfy both the characteristics of the diode and the chosen network parameters at the same time.

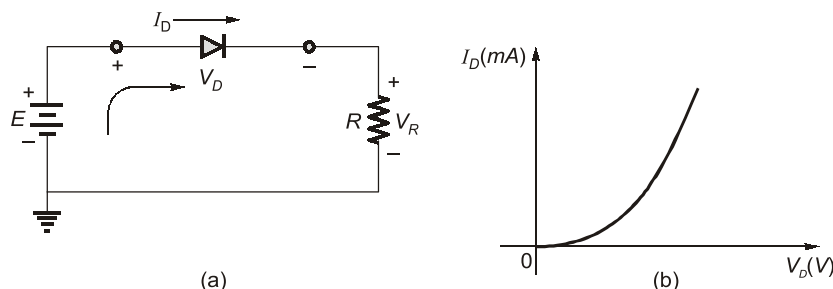

**Figure:** Series diode configuration (a) Circuit (b) Characteristics

In below figure the diode characteristics are placed on the same set of axis as a straight line defined by the parameters of the network. The straight line is called a **load line** because the intersection of the vertical axis is defined by the applied load  $R$ . The analysis to follow is therefore called **load-line analysis**. The intersection of the two curves will define the solution for the network and define the current and the voltage levels for the network.

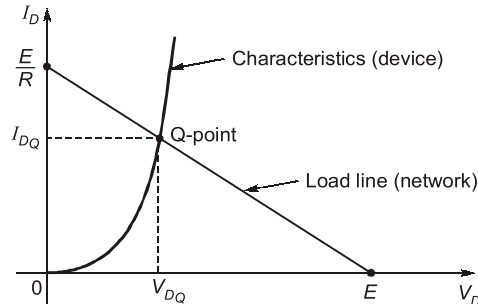

**Figure:** Drawing the load line and finding the point of operation

- A straight line drawn between the two points will define the load line as depicted in Figure. Change the level of  $R$  (the load), which will lead to the change in the intersection on the vertical axis. This will be resulted into the change in the slope of the load line and different point of intersection between the load line and the device characteristics.
- Now, we have a load line defined by the network and a characteristic curve defined by the device. The point of intersection between the two is the point of operation for this circuit.
- By simply drawing a line down to the horizontal axis, we can determine the diode voltage  $V_{DQ}$ , whereas a horizontal line from the point of intersection to the vertical axis will provide the level of  $I_{DQ}$ . The point of operation is usually called the **quiescent point** (abbreviated "**Q-point**") to reflect its "still, unmoving" qualities as defined by a dc network.
- The solution obtained at the intersection of the two curves is the same as would be obtained by a simultaneous mathematical solution of

$$I_D = \frac{E}{R} - \frac{V_D}{R} \quad [\text{Derived from equation 1.1}]$$

and

$$I_D = I_0(e^{V_D/\eta V_T} - 1) \quad [\text{Diode equation}]$$


### 1.2.2 Series Diode Configuration

The approximate models will now be used to investigate a number of series diode configurations with dc inputs. This will establish a foundation in diode analysis that will carry over into the sections and chapters to follow. The procedure described below, can infact be applied to the networks with any number of diodes in variety of configurations.

- For each configuration, firstly the state of each diode must be determined. Which diodes are "**on**" and which are "**off**"? Once determined, the appropriate equivalent can be substituted and the remaining parameters of the network can be determined.
- For the conduction region the only difference between the silicon diode and the ideal diode is the vertical shift in the characteristics, which is accounted for in the equivalent model by a dc supply of 0.7 V opposing the direction of forward current through the device. For voltages less than 0.7 V for a silicon diode and 0 V for the ideal diode the resistance is so high compared to the other elements of the network that its equivalent is the open circuit.
- **In general, a diode is in the "on" state if the current established by the applied sources is such that its direction matches that of the arrow in the diode symbol, and  $V_D \geq 0$  V for ideal**


diode,  $V_D \geq 0.3 \text{ V}$  for germanium diode,  $V_D \geq 0.7 \text{ V}$  for silicon diode, and  $V_D \geq 1.2 \text{ V}$  for gallium arsenide diode.

The below circuit of will be used to demonstrate the approach described in the above paragraphs.

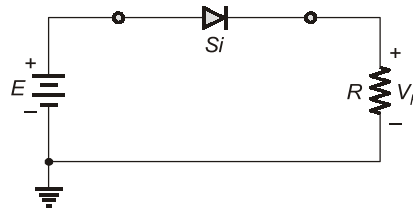

**Figure:** Series diode configuration


The state of the diode is first determined by mentally replacing the diode with a resistive element as shown in Figure (a). The resulting direction of  $I$  is a match with the arrow in the diode symbol, and since  $E > V_Y$  (cut-in voltage of diode), the diode is in the “on” state. The network is redrawn as shown in Figure (b) with the appropriate equivalent model for the forward biased silicon diode.

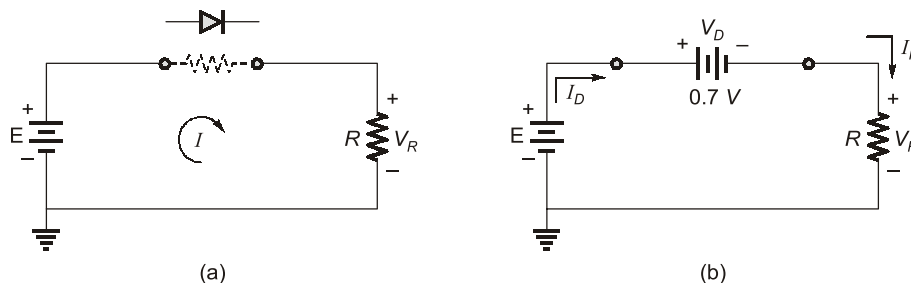

**Figure:** Series diode circuit analysis in forward bias

Following are the resulting voltage and current levels:

$$\begin{aligned} V_D &= V_Y \\ V_R &= E - V_Y \\ I_D &= I_R = \frac{V_R}{R} \end{aligned} \quad \dots(1.4)$$

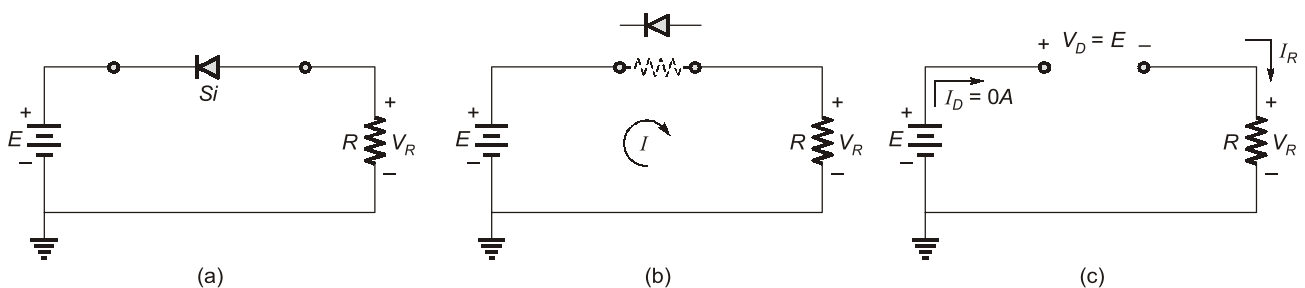

**Figure:** Series diode circuit analysis in reverse bias


When reverse bias is applied to diode then mentally replace the diode with a resistive element as shown in Figure (b) will reveal that the resulting current direction does not match the arrow in the diode symbol. The diode is in the “off” state, resulting in the equivalent circuit of Figure (c). Due to the open circuit, the diode current is 0 A and the voltage across the resistor  $R$  is the following:

$$V_R = I_R R = I_D R = (0 \text{ A}) R = 0 \text{ V}$$


The fact that  $V_R = 0 \text{ V}$  will establish  $E$  volts across the open circuit defined by Kirchhoff's voltage law. Always keep in mind that under any circumstances i.e. either DC or AC—**Kirchhoff's voltage law must be satisfied!**

**EXAMPLE : 1.1****[Single Branch Diode Circuits]**

Assuming the diodes to be ideal, find the values of  $I$  and  $V$  in the circuits shown below:

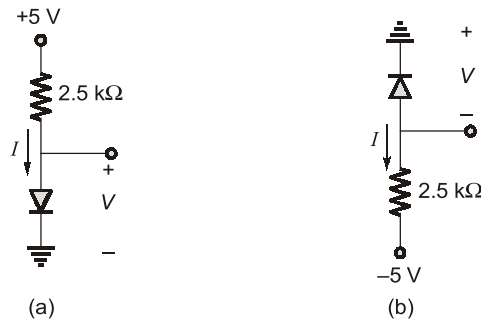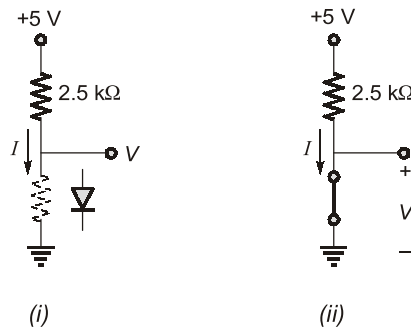**Solution :**

In Fig. (a) replacing the diode with a resistive element as shown below in **Fig. (i)**:



The resulting direction of  $I$  is a match with the arrow in the diode symbol, hence the diode is in the “on” state. Now the network can be redrawn as shown in **Fig. (ii)**.

The resulting voltage and current levels are the following:

$$V = 0 \text{ V} \quad [\text{as diode is ideal so } V_y = 0 \text{ V}]$$

and

$$I = \frac{5-0}{2.5 \text{ k}} = 2 \text{ mA}$$

In Fig. (b) replacing the diode with a resistive element as shown below in **Fig. (iii)**:

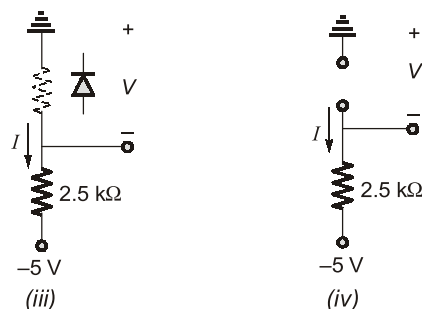


Fig. (iii) reveals that the resulting direction of current  $I$  does not match the arrow in the diode symbol. The diode is in the “off” state resulting in the equivalent circuit as shown in **Fig. (iv)**:

Resulting current and voltage can be calculated as below:


$$I = 0 \text{ A} \quad [\text{Since diode is open circuit}]$$

Now applying KVL in the circuit

$$\begin{aligned} V + 2.5I - 5 &= 0 \\ \Rightarrow V + 2.5 \times 0 - 5 &= 0 \\ \Rightarrow V &= 5 \text{ V} \end{aligned}$$

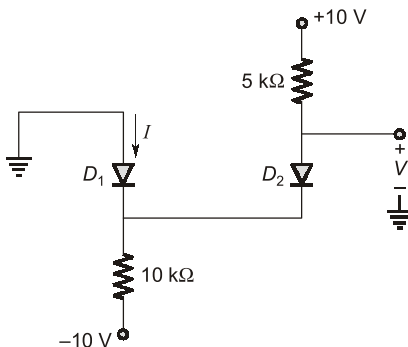**EXAMPLE : 1.2**

Assuming diodes to be ideal, find the values of  $I$  and  $V$  in the following circuit:



**Solution:**

If we assume that both diodes are conducting then  $V_B = 0 \text{ V}$  and  $V = 0 \text{ V}$ . The current in  $D_2$  is obtained from

$$I_{D_2} = \frac{10 - 0}{5\text{k}} = 2 \text{ mA}$$

The node equation at B is

$$I + 2 \text{ mA} = \frac{0 - (-10)}{10\text{k}}$$


$$\Rightarrow I = -1 \text{ mA}$$

$I = -1 \text{ mA}$ , is not possible as  $I$  does not match with arrow direction of the diode  $D_1$  so our original assumption is not correct. We start again, assuming that  $D_1$  is off and  $D_2$  is on. The current  $I_{D_2}$  is given by

$$I_{D_2} = \frac{10 - (-10)}{10\text{k} + 5\text{k}} = 1.33 \text{ mA}$$

and the voltage at node B is,  $V_B = -10 + 10\text{k} \times 1.33 \text{ mA} = +3.3 \text{ V}$

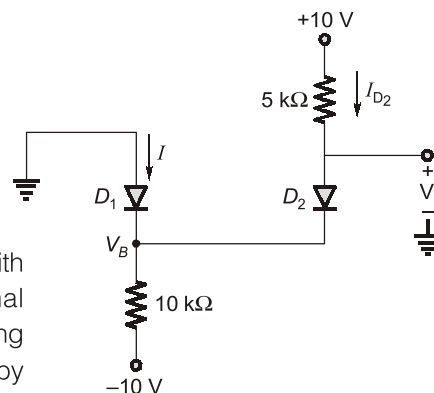
Thus  $D_1$  is reverse biased as assumed, and the final result is  $I = 0 \text{ A}$  and  $V = 3.3 \text{ V}$ .



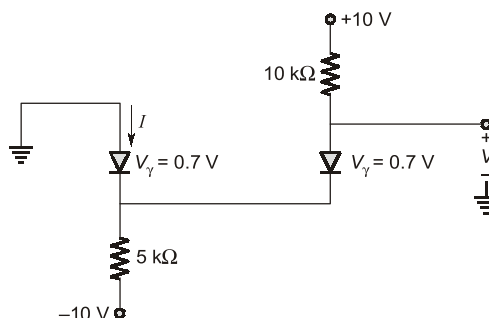**EXAMPLE : 1.3**

[Practical diode circuit]


Find  $I$  and  $V$  for the circuit shown below:






**OBJECTIVE  
BRAIN TEASERS**

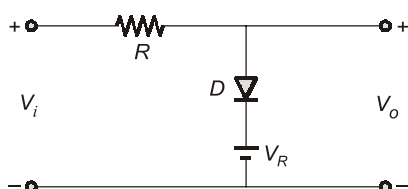- Q.1** In the circuit shown below the input  $v_i$  has positive and negative swings and  $v_o$  is the output then



- (a)  $v_o = 0$  for negative  $v_i$   
(b)  $v_o = V_R$  for positive  $v_i$   
(c)  $v_o = V_R$  for  $v_i > V_R$   
(d)  $v_o = V_R$  for all  $v_i$

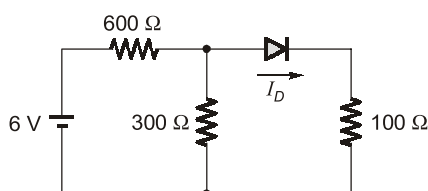
- Q.2** In the *Si* diode circuit shown below, a diode current of 6.7 mA is flowing.



Assuming diode is ideal one. Its forward resistance and cut-in voltage are


- (a)  $2\ \Omega, 0.7\text{ V}$       (b)  $0\ \Omega, 0.7\text{ V}$   
(c)  $0\ \Omega, 0\text{ V}$       (d)  $4\ \Omega, 0\text{ V}$

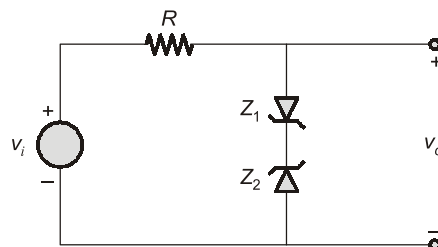- Q.3** In the circuit shown below the Zener voltage  $V_{Z1} = V_{Z2} = 5\text{ volts}$ ,  $V_Y = 0.6\text{ V}$ ,  $v_o$  is the output then




- (a) For  $|v_i| \leq 5.6\text{ volts}$ ,  $v_o = v_i$   
(b) For  $|v_i| \leq 10\text{ volts}$ ,  $v_o = v_i$   
(c) For  $|v_i| > 5.6\text{ volts}$ ,  $v_o = v_i$   
(d)  $v_o = 5.6\text{ volts}$  for all  $v_i$

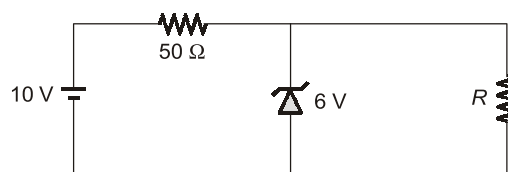
- Q.4** The 6 V Zener diode shown in figure has zero Zener resistance and a knee current of 5 mA. The minimum value of  $R$  so that the voltage across it does not fall below 6 V is



- (a)  $1200\ \Omega$       (b)  $80\ \Omega$   
(c)  $50\ \Omega$       (d)  $10\ \Omega$

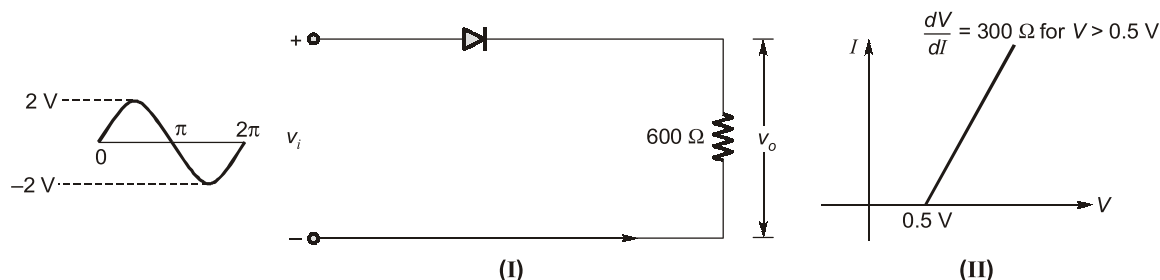- Q.5** Consider the circuit shown in Figure (I). If the diode used here has the V-I characteristic as in Figure (II), then the output waveform  $v_o$  is




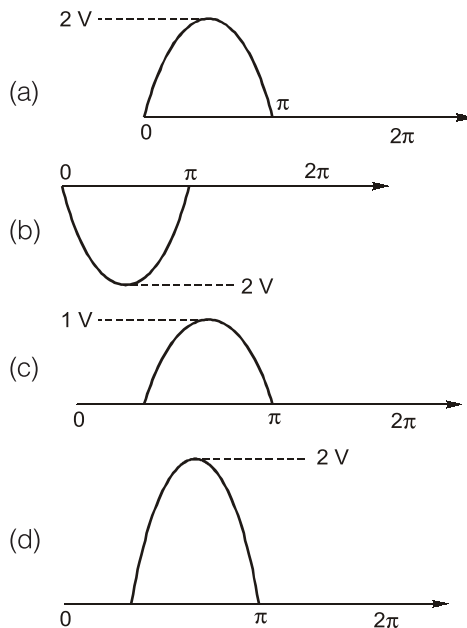

**Q.6** A diode is very useful for rectifier circuits due to its


- (a) ability to conduct current only in one direction
- (b) ability to give current in both directions
- (c) zero resistance in both directions
- (d) none of these

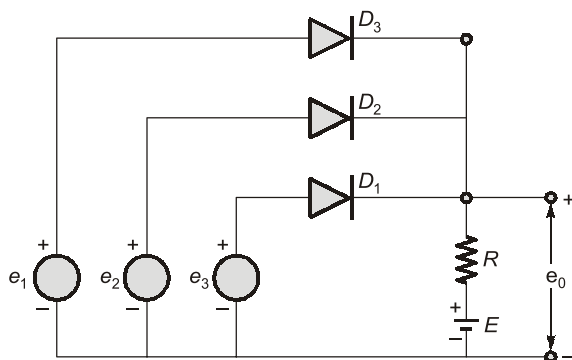**Q.7** In the circuit shown below, if  $e_1 = 2\text{ V}$ ,  $e_2 = 5\text{ V}$ ,  $e_3 = 1\text{ V}$  and  $E = 2\text{ V}$ , then which one of the diodes will be conducting and what will be the  $e_0$ ?




- (a)  $D_3 : 1\text{ V}$
- (b)  $D_1 : 2\text{ V}$
- (c)  $D_2 : 5\text{ V}$
- (d)  $D_1 : 5\text{ V}$

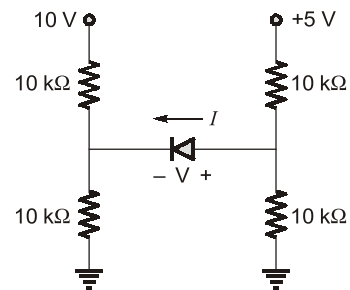**Q.8** Assuming diode in the circuit is ideal one. Find the current and voltage shown in the figure.



- (a)  $0\text{ mA}, 2\text{ V}$
- (b)  $0\text{ mA}, -2.5\text{ V}$
- (c)  $1\text{ mA}, 2\text{ V}$
- (d)  $1\text{ mA}, 2.5\text{ V}$

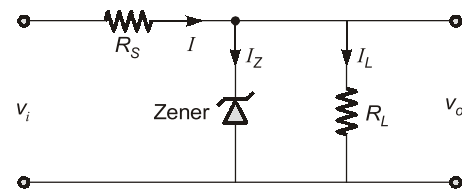**Q.9** Consider the following statements regarding the circuit given in the figure, where the output voltage is constant:



1.  $v_i >$  the voltage at which the Zener breaks down.
2.  $I_L <$  the difference between  $I$  and  $I_Z$ , the current at which the Zener breaks down.
3.  $R_S <$  the Zener nominal resistance.

Of these statements:

- (a) 1, 2 and 3 are correct
- (b) 1 and 2 are correct
- (c) 2 and 3 are correct
- (d) 1 and 3 are correct

**Q.10** The ideal characteristics of a voltage stabilizer is

- (a) constant output voltage with low internal resistance
- (b) constant output current with low internal resistance
- (c) constant output voltage with high internal resistance
- (d) constant internal resistance with variable output voltage

### ANSWERS KEY

- 1. (c)    2. (c)    3. (a)    4. (b)    5. (c)
- 6. (a)    7. (c)    8. (b)    9. (b)    10. (a)




### HINTS & EXPLANATIONS

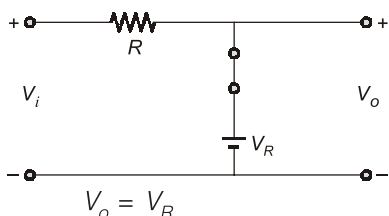
#### 1. (c)

The given circuit is a positive clipper.

For  $V_i > V_R$ , the diode is forward biased and acts as short-circuit.




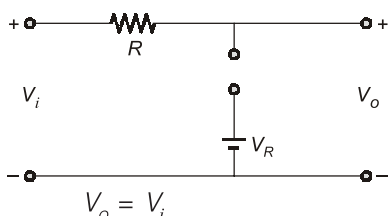For  $V_i < V_R$ , diode is reverse-biased and acts as open-circuit.



Hence, 
$$V_o = \begin{cases} V_R & \text{for } V_i \geq V_R \\ V_i & \text{for } V_i < V_R \end{cases}$$

#### 2. (c)

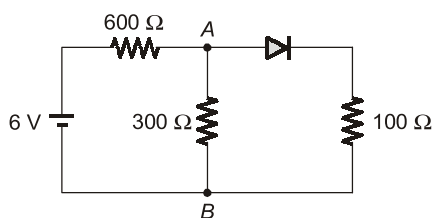


Calculating Thevenin equivalent across terminals A-B,

$$V_{AB} = \frac{6 \times 300}{300 + 600} = 2 \text{ V}$$

$$R_{AB} = \frac{600 \times 300}{600 + 300} = 200 \Omega$$

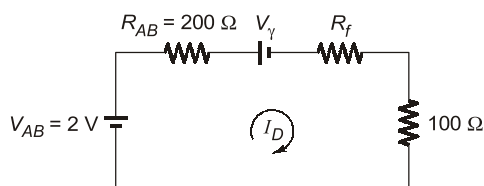Since, the diode is forward-biased, the equivalent circuit can be drawn as below:



$$I_D = \frac{V_{AB} - V_Y}{200 + R_f + 100}$$

where,  $V_Y$  is the cut-in voltage and  $R_f$  is the forward resistance of diode,

$$6.7 \times 10^{-3} = \frac{2 - V_Y}{300 + R_f}$$

The above condition is satisfied for option (c):

$$V_Y = 0 \text{ and } R_f = 0$$

#### 3. (a)

For  $V_i > V_Y + V_{Z1} = 5.6 \text{ V}$ , Zener diode  $Z_1$  will be forward-bias and  $Z_2$  will be in break-down region.

Hence,  $V_o = V_Y + V_{Z1} = 5.6 \text{ V}$ ; for  $V_i > 5.6 \text{ V}$

For  $V_i < -V_Y - V_{Z2} = -5.6 \text{ V}$ ,  $Z_2$  will be forward-bias and  $Z_1$  will be in break-down region. Hence,


$V_o = -V_Y - V_{Z2} = -5.6 \text{ V}$ ; for  $V_i < -5.6 \text{ V}$

For  $-5.6 \text{ V} \leq V_i \leq 5.6 \text{ V}$ , the reverse-biased Zener diode is not in break-down region and hence, doesn't conduct current

$$V_o = V_i \text{ for } -5.6 \leq V_i \leq 5.6 \text{ V}$$

$$V_o = V_i \text{ for } |V_i| \leq 5.6 \text{ V}$$

#### 4. (b)

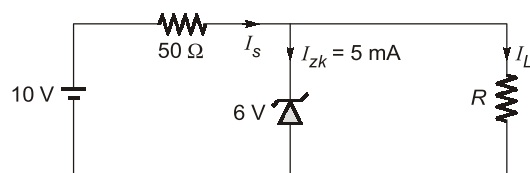

In the above regulator circuit,

$$I_s = \frac{10 - 6}{50} = 0.08 \text{ A} = 80 \text{ mA}$$

When the minimum current (knee current passes through the diode), then maximum current passes through load resistance  $R$ . Hence,

$$I_{L(\max)} = I_s - I_{zk} = 80 \text{ mA} - 5 \text{ mA}$$


$$\frac{6}{R_{s(\min)}} = 75 \times 10^{-3} \Rightarrow R_{s(\min)} = 80 \Omega$$

#### 5. (c)

From the given  $V$ - $I$  characteristics of diode,

$$V_Y = 0.5 \text{ V}, R_f = 300 \Omega$$

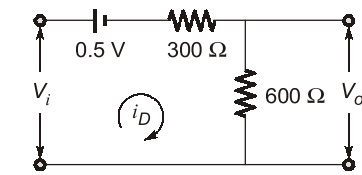In the given circuit, diode is forward-biased for  $V_i > 0.5 \text{ V}$ . Hence, the equivalent circuit can be drawn as below:




$$i_D = \frac{V_i - 0.5}{900} \text{ A}$$

$$V_o = 600i_D = 600 \left( \frac{V_i - 0.5}{900} \right) = \frac{2}{3} (V_i - 0.5)$$

For  $V_i < 0.5 \text{ V}$ , diode is reverse-biased and acts as open-circuit. Hence,

$$V_o = 0$$

$$V_o = \begin{cases} \frac{2}{3}(V_i - 0.5) & ; \text{ for } V_i > 0.5 \text{ V} \\ 0 & ; V_i < 0.5 \text{ V} \end{cases}$$

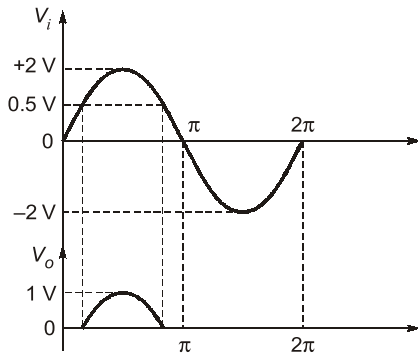**6. (a)**

The diodes allow the current only in one direction and block the current flow into the other. The above property of diode is used to convert bidirectional voltage into unidirectional voltage in a rectifier.

**7. (c)**

If either of diodes  $D_1$  or  $D_3$  is conducting, then  $D_2$  will also conduct and two voltages will try to superimpose at  $e_o$  which is violation of Kirchhoff's law.

When diode  $D_2$  conducts,  $e_o = 5 \text{ V}$  and both the diodes  $D_1$  and  $D_3$  are reverse-biased. Hence,  $D_2$  conducts :  $e_o = 5 \text{ V}$


**8. (b)**

Using the voltage division rule,  
Voltage on  $n$ -side of diode,

$$V_n = 10 \left( \frac{10}{10 + 10} \right) = 5 \text{ V}$$


Voltage on  $p$ -side of diode,
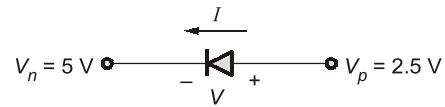
$$V_p = 5 \left( \frac{10}{10 + 10} \right) = 2.5 \text{ V}$$



Since,  $V_n > V_p$ . Hence, the diode is reverse-biased and  $I = 0$ . The diode acts as open-circuit.

$$\therefore V = 2.5 - 5 = -2.5 \text{ V}$$

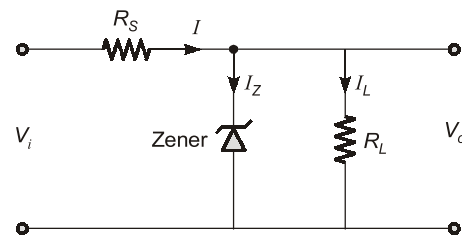**9. (b)**

1.  $V_i = V_z + IR_s$ . Hence,  $V_i > V_z$ .  
Therefore, statement 1 is correct.

2. We have,  $I = I_z + I_L$   
Here,  $I_{L(\max)} = I - I_{zk}$ , where  $I_{zk}$  is the current at which Zener break-down.

$$I_{L(\min)} = I - I_{z(\max)}$$


$$\text{Therefore, } I_L < I - I_{zk}$$

Hence, statement 2 is correct.

3. The Zener nominal resistance is very small and less than the resistance  $R_s$ . Hence, statement 3 is incorrect.

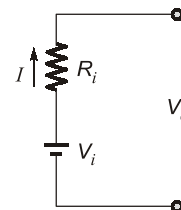**10. (a)**

Voltage stabilizer must provide a constant output voltage.



$$V_o = V_i - IR_i$$

For  $V_o \approx V_i$ ,  $R_i$  should be very low.

Hence, the voltage stabilizer must have constant output voltage with low internal resistance.



## CONVENTIONAL BRAIN TEASERS

- Q.1** A light-emitting diode (LED) has a greater forward voltage drop than that of common signal diode. A typical LED can be modeled as a constant forward voltage drop  $v_D = 1.6$  V. Its luminous intensity  $I_V$  varies directly with forward current and is described by  $I_V = 40i_D$  millicandela (mcd).  
A series circuit consists of a LED, a current-limiting resistor  $R$ , and a 5-V DC source  $V_s$ . Find the value of  $R$  such that the luminous intensity is 1 mcd.

**1. (Sol.)**

With a 5 V DC source, LED is forward-biased and can be modelled as a constant forward voltage drop  $V_D = 1.6$  V. The equivalent circuit can be drawn as below:


$$\therefore i_D = \frac{5 - 1.6}{R}$$

The luminous intensity,  $I_V$  is defined as


$$I_V = 40i_D (\text{mcd})$$

$$\Rightarrow 1 \text{ mcd} = 40 \left( \frac{5 - 1.6}{R} \right)$$

$$\Rightarrow R = 136 \, \Omega$$

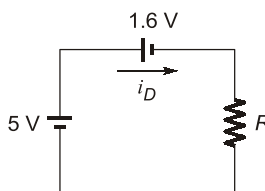

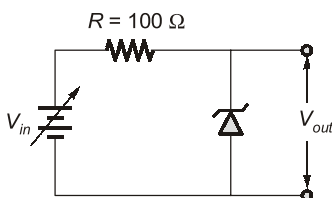- Q.2** Determine the maximum and the minimum input voltages that can be regulated by the Zener diode of circuit shown in figure. Take  $V_{\text{out}} = 5.1$  V, at  $I_z = 49$  mA,  $I_{zk} = 1$  mA,  $R_z = 7 \, \Omega$  at  $I_z$  power dissipation = 1 Watt.



**2. (Sol.)**

The equivalent circuit with Zener diode in breakdown region can be drawn as below:

**Given:**  $V_{\text{out}} = 5.1$  V at  $I_z = 49$  mA


At  $I_{zk} = 1$  mA, the output voltage is

$$\begin{aligned} V_{\text{out}} &= 5.1 \text{ V} - (I_z - I_{zk}) R_z \\ V_{\text{out}} &= 5.1 - (49 - 1) \times 7 \times 10^{-3} \\ V_{\text{out}} &= 4.76 \text{ V} \end{aligned}$$

Hence, the minimum voltage that can be regulated is

$$\begin{aligned} V_{\text{in}(\text{min})} &= I_{zk} \times R + V_{\text{out}} \\ V_{\text{in}(\text{min})} &= 1 \times 10^{-3} \times 100 + 4.76 = 4.86 \text{ V} \end{aligned}$$

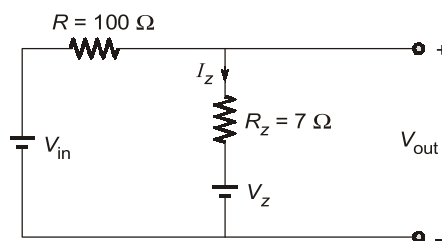To find the maximum input voltage, we first calculate the maximum Zener current. For power dissipation of 1 Watt,



$$I_{Z(\max)} = \frac{P_{D(\max)}}{V_Z} = \frac{1\text{ W}}{5.1\text{ V}} = 196\text{ mA}$$

At  $I_{Z(\max)}$ , the output voltage is


$$V'_{\text{out}} = 5.1\text{ V} + (I_{Z(\max)} - I_Z) R_Z$$

$$V'_{\text{out}} = 5.1 + (196 - 49) \times 7 = 5.1 + 1.03 = 6.13\text{ V}$$


Hence, the maximum output voltage that can be regulated is

$$V_{\text{in}(\max)} = I_{Z(\max)} \cdot R + V'_{\text{out}} = 196 \times 10^{-3} \times 100 + 6.13 = 25.73\text{ V}$$

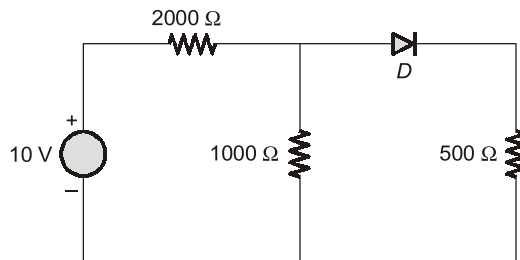**Q.3** In the circuit shown below, the diode has a forward resistance  $R_f = 15\ \Omega$  and a cut-in voltage  $V_\gamma = 0.5\text{ V}$ . Determine the current in the diode.



**3. (Sol.)**

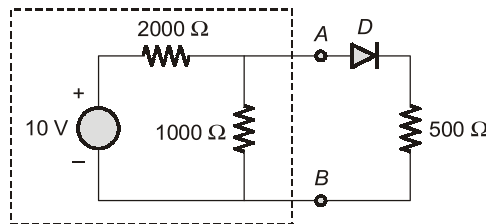


Calculating the Thevenin voltage and resistance across the terminals  $AB$ , we get,

$$V_{\text{Th}} = 10 \times \left( \frac{1000}{1000 + 2000} \right) = \frac{10}{3}\text{ V}$$

$$R_{\text{Th}} = 1000\ \Omega \parallel 2000\ \Omega = \frac{1000 \times 2000}{1000 + 2000} = \frac{2000}{3}\ \Omega$$

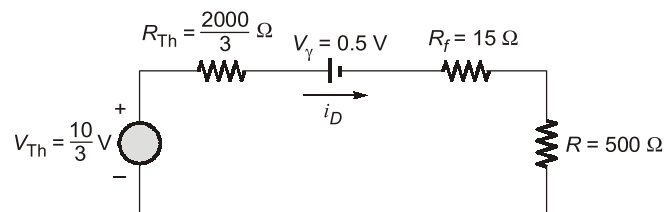The simplified Thevenin equivalent circuit can be drawn as below:



Current through diode,

$$i_D = \frac{V_{\text{Th}} - V_\gamma}{R_{\text{Th}} + R_f + R} = \frac{\frac{10}{3} - 0.5}{\frac{2000}{3} + 15 + 500} = \frac{3.33 - 0.5}{666.67 + 515} = 2.39\text{ mA}$$