

UPPSC-AE

2021

Uttar Pradesh Public Service Commission

Combined State Engineering Services Examination
Assistant Engineer

Electrical Engineering

Power Systems

Well Illustrated **Theory** *with*
Solved Examples and Practice Questions



MADE EASY
Publications

Note: This book contains copyright subject matter to MADE EASY Publications, New Delhi. No part of this book may be reproduced, stored in a retrieval system or transmitted in any form or by any means. Violators are liable to be legally prosecuted.

Power Systems

Contents

| UNIT | TOPIC | PAGE NO. |
|------|---|-----------|
| 1. | Line Parameters and Performance of Transmission Lines | 3 - 39 |
| 2. | Voltage Control and Concepts of FACTS | 40 - 52 |
| 3. | Distribution System, Mechanical Design of OH Lines and Cables | 53 - 76 |
| 4. | Load Flow Studies | 77 - 90 |
| 5. | Fault Analysis | 91 - 115 |
| 6. | Power System Stability | 116 - 128 |
| 7. | Switchgear & Protection | 129 - 167 |
| 8. | Electricity Generation & Economic Operations | 168 - 187 |
| 9. | Recent Trends in Power Systems | 188 - 199 |



Line Parameters and Performance of Transmission Lines



1.1 Introduction

An “Electric power system” is a network of electrical components used to supply, transmit and use electric power. An example of an electric power system is the network that supplies a region’s home and industry with power for sizable regions, this power system is called “the grid” and can be broadly divided into the generators that supply the power, the transmission system that carries the power from the generating stations to study the load centers and the distribution system that feeds the power to nearby homes and industries.

This chapter deals with fundamentals of power systems which includes polyphase AC circuits in order to study the characteristics of transmission lines. An electric transmission line can be represented by series combination of resistance, inductance and shunt combination of conductance and capacitance. This chapter thus deals with the series line parameters and shunt line parameters of a transmission line.

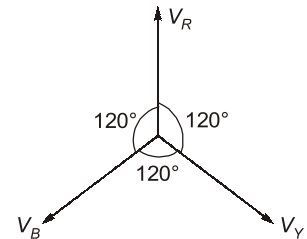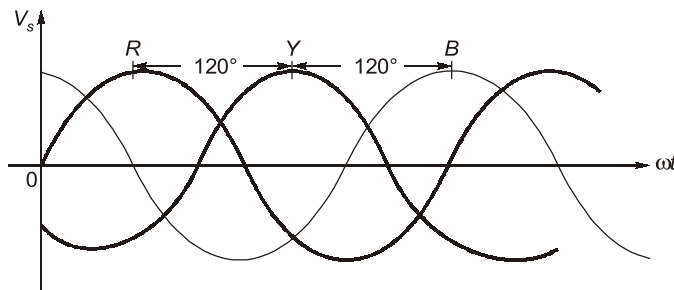1.2 Three-Phase AC Systems

- A 3- ϕ circuit has an ac voltage generator (alternator) that produces three sinusoidal voltages that are identical except for a phase angle difference of 120° electrical.



Here,

Phase sequence = RYB

$$V_R = V_m \sin \omega t = V \angle 0^\circ \text{ Volt}$$

$$\begin{aligned} V_Y &= V_m \sin(\omega t - 120^\circ) \\ &= V \angle -120^\circ \text{ Volt} \end{aligned}$$

$$\begin{aligned} V_B &= V_m \sin(\omega t - 240^\circ) \\ &= V \angle -240^\circ \text{ Volt} \\ &= V \angle +120^\circ \text{ Volt} \end{aligned}$$

NOTE: In general for a n -phase systems, phase difference is $360^\circ/n$.

1.2.1 Phase Sequence

- It is the order by which the phase voltages attains their peak value. The phase sequence may be positive, negative or zero (no particular sequence).
- RYB is a universally adopted phase sequence.

- For a 3- ϕ system phase sequence must be defined.
 - Positive phase sequence: i.e. RYB, YBR, BRY
 - Negative phase sequence: i.e. RBY
 - Zero phase sequence: No particular order of phase sequence
- For balanced 3- ϕ system: $I_R + I_Y + I_B = 0$
For unbalanced 3- ϕ system: $I_R + I_Y + I_B \neq 0$


**NOTE**

- Phase voltage (V_p): It is the voltage between any one of the phase and neutral.
- Line voltage (V_L): Voltage measured between any two phases is known as line voltage.
- Phase current (I_p): The current flowing in any one phase is called phase current.
- Line current (I_L): The current flowing in the line is line current.

1.2.2 Types of Three-Phase Connections

There are basically two types of 3-phase connections:

- Star (Y) connection
- Delta (Δ) connection

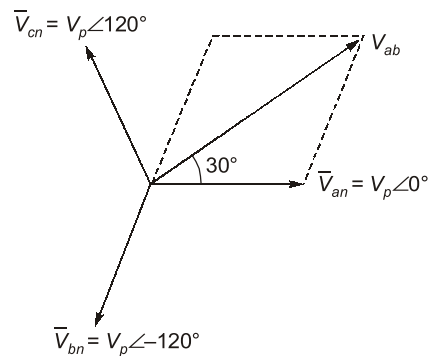(a) Star (Y) connection:**Phase and Magnitude Relations between the Phase and Line Voltage of a Y-Connection**

- The set of voltage V_{ab} , V_{bc} and V_{ca} are called the **line voltages**, and the set of voltages V_{an} , V_{bn} and V_{cn} are referred as the **phase voltages**.
- For a balanced system, each phase voltage has the same magnitude

$$|V_{an}| = |V_{bn}| = |V_{cn}| = V_p$$

where V_p denotes the effective magnitude of the phase voltage

$$V_{ab} = \sqrt{3} V_p \angle 30^\circ$$

$$V_{bc} = \sqrt{3} V_p \angle -90^\circ$$


$$V_{ca} = \sqrt{3} V_p \angle 150^\circ$$

**NOTE**

- The line voltages (V_L) constitute a balanced three-phase voltage system whose magnitudes are $\sqrt{3}$ times the phase voltages (V_p); $V_L = \sqrt{3} V_p$.
- The line current (I_L) and the phase current (I_p) have the same magnitude; $I_L = I_p$
- With star connected system, protection can be provided by connecting a protective device between neutral and earth for earth fault detection.

(b) Delta (Δ) connection:

For phase sequence (abc):

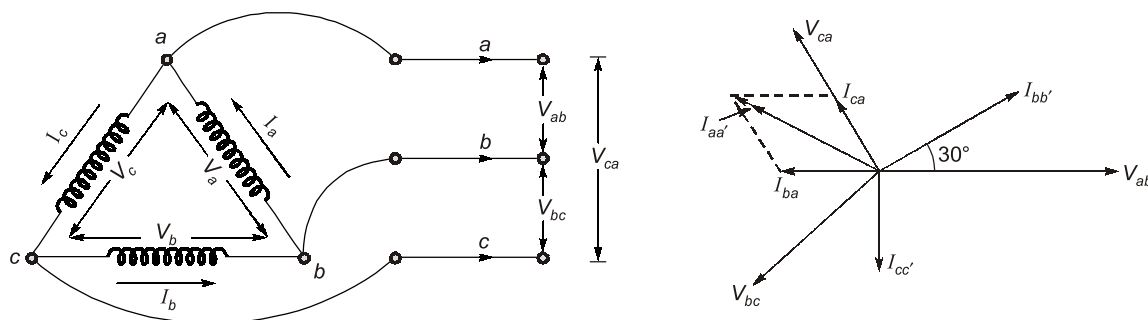

Relations between Phase and Line Currents in a Δ -Connection



NOTE

- The line and phase voltages have the same magnitude;

$$|V_L| = |V_p|$$

- A set of balanced three phase currents yields a corresponding set of balanced line currents that are $\sqrt{3}$ times the phase value;

$$I_L = \sqrt{3} I_p$$

Power Calculations

- Single phase power, $P_{1-\phi} = V_{Ph} I_{Ph} \cos \phi$
- Three phase power, $P_{3-\phi} = 3 V_{Ph} I_{Ph} \cos \phi$
- Three phase power in star connection,

$$P_{3-\phi(Y)} = 3 \cdot \frac{V_L}{\sqrt{3}} \cdot I_L \cos \phi = \sqrt{3} V_L I_L \cos \phi$$

- Three phase power in delta connection,

$$P_{3-\phi(\Delta)} = 3 \cdot V_L \cdot \frac{I_L}{\sqrt{3}} \cos \phi = \sqrt{3} V_L I_L \cos \phi$$

- Three phase reactive power,

$$P_{(Y)} \text{ or } P_{(\Delta)} = \sqrt{3} V_L I_L \sin \phi$$

- Total apparent power, $S = \sqrt{3} V_L I_L$



Example -1.1 Three equal impedances ($R + jX$) connected in delta carry a balanced line current of I_L . The total active and reactive power drawn by these are

- (a) $I_L^2 R$ and $I_L^2 X$ respectively (b) $3 I_L^2 R$ and $3 I_L^2 X$ respectively
(c) $I_L^2 R/3$ and $I_L^2 X/3$ respectively (d) $I_L^2 X$ and $I_L^2 R$ respectively

[UPPSC]

Solution: (a)

Per phase impedance,

$$Z = R + jX$$

Given,

$$\text{Line current} = I_L$$

For delta connection,

$$I_P = \frac{I_L}{\sqrt{3}}$$


Total active power,

$$P_T = 3(I_P)^2 R = 3 \left(\frac{I_L^2}{3} \right) R = I_L^2 R$$

Similarly total reactive power drawn will be $I^2 X$.

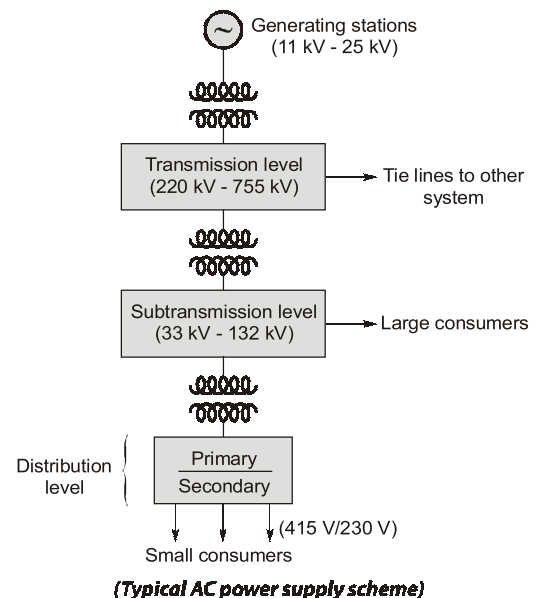1.3 Electric Supply System

- The conveyance of electric power from a power station to consumer's premises is electric supply system.
- An electric supply system consists of three principles components i.e. power station, the transmission and the distribution system.
- Now-a-day, 3-phase 3-wire ac system is universally adopted for generation and transmission of electric power.
- However, distribution of electric power is done by 3-phase 4-wire ac system.
- Schematic diagram depicting power system structure.



Generating Station

- Station where the electric power is produced.
- The usual generation voltage is from (11-25 kV).
- Due to several advantages of high voltage transmission, the generation voltage is stepped up at the generating station.

Primary Transmission

- Generally the primary transmission is carried at 66 kV, 132 kV, 220 kV, 400 kV or 765 kV with help of 3-phase 3-wire overhead system from power plant after stepping up voltage to above mentioned voltage levels to receiving stations at the outskirts of city.

Secondary Transmission

- The primary transmission lines terminate at receiving station and here the voltage is reduced to 33 kV/66 kV for further distribution, by step down transformers.

Primary Distribution

- The secondary transmission line terminates at the substation (ss) where the voltage is reduced from 33 kV to 11 kV, 3-phase, 3-wire system.
- Large consumers are generally supplied power at 11 kV for further handling with their own substations.

Secondary Distribution

- The electric power from primary distribution line (11 kV) is delivered to distribution substations (DS).

- The substations near consumer step down the voltage to 415 V, 3-phase 4-wire for secondary distribution.
- Various voltage levels in power system:

| Voltage Level | Voltage Lines |
|------------------------------|--------------------------------------|
| (a) Low voltage | 230 V(1- ϕ), 400 V(3- ϕ) |
| (b) High voltage | 11 kV, 33 kV |
| (c) Extra high voltage (EHV) | 66 kV, 132 kV, 220 kV |
| (d) Modern EHV | 400 kV |
| (e) Ultra high voltage | 765 kV and above |

**NOTE**

- The voltage at the point of commencement of supply shall not vary by more than
 - $\Rightarrow \pm 6\%$ in the case of the low voltage (upto 250 V) and medium voltage (upto 650 V).
 - $\Rightarrow +6\%$ to -9% in the case of high voltage (i.e. upto 33 kV).
 - $\Rightarrow \pm 12\frac{1}{2}\%$ in the case of extra high voltage (i.e. exceeding 33 kV).
- An ideal transmission line has 0% regulation.


1.3.1 Effect of System Voltage on Transmission

- Power loss in the line is inversely proportional to the system voltage and power factor both.
- Percentage voltage drop in resistance decreases with the increase in the system voltage.
- Weight of the conductor material for the line will decrease with the increase in supply voltage and power factor.
- Efficiency of transmission, increases with the increase of supply voltage and power factor.
- Higher supply voltages also enhance the system stability.
- The problems encountered with high voltages are the insulation of the equipment, corona, radio and television interference.
- The voltage level of a system is therefore governed by the amount of power to be transmitted and the length of the line.

1.4 Introduction to Transmission Lines


- The performance of a transmission line is governed by its four parameters namely series resistance R and inductance L , shunt capacitance C and conductance G .
- The resistance R is due to the fact that every conductor offers opposition to the flow of current.
- The inductance L is due to the fact that the current carrying conductor is surrounded by the magnetic lines of force. The capacitance of the line is due to the fact that the voltage which is always at lower potential than the conductor and the air between them forms a dielectric medium.
- The shunt conductance is mainly due to flow of leakage currents over the surface of the insulators.
- The line resistance causes voltage drop (IR volts) and power loss (I^2R watts) in the line, line inductance causes voltage drop ($2\pi fLI$ volts), line capacitance produces a current called "charging current".
- The performance of the transmission line can be determined by following two parameters:

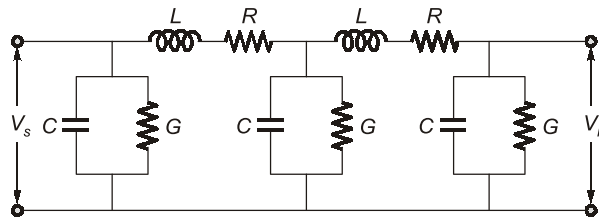- (a) Percentage efficiency
- (b) Percentage regulation
- Resistance, R is due to the fact that every conductor offers opposition to the flow of current.
- Inductance, L is due to the fact that the current carrying conductor has surrounding magnetic lines of force.
- Capacitance, C results due to potential difference between the conductors and the air serving as a dielectric medium between them.
- Shunt conductance G , which is due to leakage over line insulators is almost neglected in overhead transmission lines.



(A transmission line model)

- The line resistance causes voltage drop (IR) and power loss (I^2R) in the transmission line, line inductance causes voltage drop ($IX_L = \omega LI$), line capacitance produces a charging current (I_C).

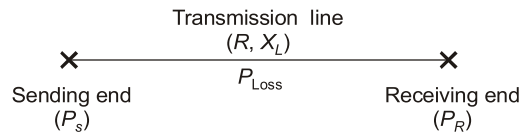(a) Efficiency of a Transmission Line

- Let a transmission line with R and X_L as series parameters and P_S , P_R respectively are sending and receiving end powers. Losses in the line is $P_{Loss} = P_S - P_R$
- Efficiency of a transmission line is defined as the ratio of power delivered at the receiving end to the power sent from the sending end.
- Percentage efficiency of transmission line is given by,

$$\% \eta = \frac{P_R}{P_S} \times 100 = \frac{P_S - P_{Loss}}{P_S} \times 100 = \frac{P_R}{P_R + P_{Loss}} \times 100$$

**NOTE**

- Higher the efficiency of transmission line, better is the performance of the transmission line.
- An ideal transmission line has 100% efficiency (i.e. zero losses) which is not possible practically.

(b) Voltage Regulation of a Transmission Line

- It is defined as the rise in voltage at the receiving end expressed as percentage of full load voltage, when full load at a specified power factor is thrown off i.e.

$$\% \text{regulation} = \frac{V_{RNL} - V_{RFL}}{V_{RFL}} \times 100$$

where, V_{RNL} = Magnitude of no-load receiving end voltage

V_{RFL} = Magnitude of full load receiving end voltage

- This is basically a voltage drop in the line due to resistance and inductance of the line.



NOTE

- An ideal transmission line has 0% regulation.
- Lower the voltage regulation, better is the performance of transmission line.

ABCD Parameters:

- Sending end quantities V_s, I_s can be represented in terms of receiving end quantities V_r, I_r by the following equations,



- $V_s = AV_r + BI_r$
 $I_s = CV_r + DI_r$
where A, B, C, D are the parameters of transmission on line.

- In matrix form,
$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_r \\ I_r \end{bmatrix}$$

- Calculation of A, B, C, D :

$$A = \left. \frac{V_s}{V_r} \right|_{I_r=0} \quad C = \left. \frac{I_s}{V_r} \right|_{I_r=0}$$

$$B = \left. \frac{V_s}{I_r} \right|_{V_r=0} \quad D = \left. \frac{I_s}{I_r} \right|_{V_r=0}$$


1.4.1 Classification of Transmission Lines

- Transmission lines are classified based on three criterion and they are:
 - (a) Length of transmission line
 - (b) Operating voltage
 - (c) Effect of capacitance
- On the basis of length of transmission line, transmission lines are classified as:
 - (i) Short transmission line
 - (ii) Medium transmission line
 - (iii) Long transmission line


| Transmission lines | Length of transmission lines | Operating voltage | Effect of capacitance(C) |
|--------------------------|------------------------------|-------------------|-----------------------------|
| Short transmission line | (0 – 80) km | (0 – 20) kV | Neglected |
| Medium transmission line | (80 – 160) km | (20 – 100) kV | C is lumped or concentrated |
| Long transmission line | (> 160) km | (> 100) kV | C is distributed |

(A) Short Transmission Line

- **Equivalent circuit:**

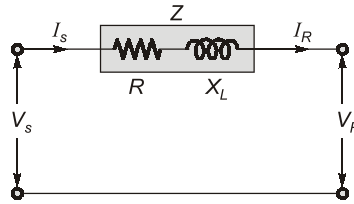

- **Phasor diagram:**

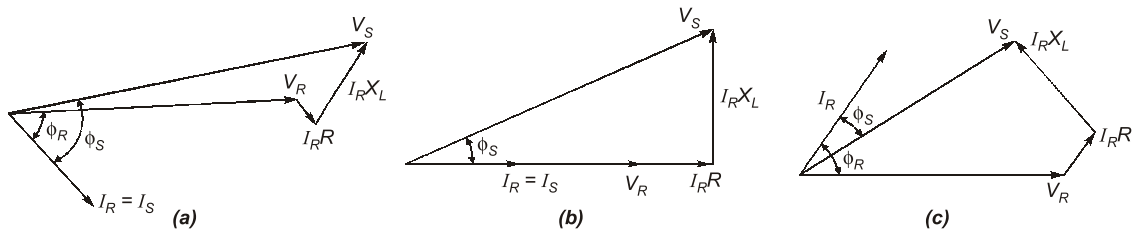

(Phasor diagrams of a short transmission line for same V_R and I_R)

(a) Lagging p.f. (0.7 lag), (b) unity p.f. and (c) leading p.f.

- **Sending end parameters:**

$$I_S = I_R$$

$$V_S = V_R + I_R Z$$

where, Z is $z l$, the total series impedance of the line (l being the total length of the line).

- **In matrix form:**

$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$

where, $ABCD$ parameters are $A = D$, $B = Z$, $C = 0$

**NOTE**

- $AD - BC = 1$, hence short line is also a reciprocal network.
- For a short transmission line, conductance and capacitance are neglected.
- For short line, line parameters are assumed to be lumped.
- In general, product of physical length (l) and frequency (f) for short transmission line:

$$f l < 4000 \text{ Hz km}$$

- In general, product of F and l is greater than 12000 Hz km for long transmission line.

- % Voltage regulation = $\frac{|V_s| - |V_R|}{|V_R|} \times 100$

where V_s is sending end voltage or no load receiving end voltage and V_R is full load rated receiving end voltage.

Further, using phasor diagram (a) and (c),

$$V_s = V_R + |I_R| R \cos \phi_R + |I_R| X_L \sin \phi_R \quad \dots (\text{For lagging p.f.})$$

$$V_s = V_R + |I_R| R \cos \phi_R - |I_R| X_L \sin \phi_R \quad \dots (\text{For leading p.f.})$$

For lagging p.f.:
$$\%V.R. = \frac{|I_a|R \cos \phi_R + |I_a|X_L \sin \phi_R}{|V_a|} \times 100$$

For leading p.f.:
$$\%V.R. = \frac{|I_a|R \cos \phi_R - |I_a|X_L \sin \phi_R}{|V_R|} \times 100$$

Condition for zero voltage regulation:

- This is possible at leading p.f. load.
- For zero VR: $I_R R \cos \phi_R - I X_L \sin \phi_R = 0$

$$\Rightarrow \boxed{\tan \phi_R = \frac{R}{X_L}}$$

or,
$$\phi = \tan^{-1} \left(\frac{R}{X_L} \right)$$

Condition for maximum voltage regulation:

- Maximum regulation occurs at lagging power factor load.

i.e. $\frac{d}{d\phi_R} [\text{Voltage regulation}] = 0$

$$\Rightarrow \boxed{\tan \phi_R = \frac{X_L}{R}}$$

or,
$$\phi_R = \tan^{-1} \left(\frac{X_L}{R} \right)$$

Condition for negative voltage regulation:

- This occurs at leading p.f.
- Condition is, $\tan \phi_R > \frac{R}{X_L}$ (leading)
- Zero regulation and maximum regulation coincides when $\theta = 0.45^\circ$. i.e. $\cos(45^\circ) = 0.707$ (lag)
- Power factor has a great influence on voltage regulation, for lagging power factor the regulation is positive and for leading power factors may even be negative.

Efficiency: It is given by

$$\% \eta = \frac{\text{Power received at receiving end}}{\text{Power received at receiving end} + \text{losses}} \times 100$$


$$\% \eta = \frac{P}{P + 3I_r^2 R} \times 100$$

where, P = Power received at receiving end

R = Resistance per phase of the line

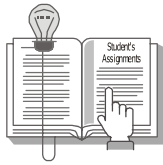(B) Medium Transmission Line

- In medium transmission lines, the shunt admittance (usually capacitance) is not neglected.
- Basically these lines can be modelled into two basic circuits:
 - (i) Nominal π -circuit
 - (ii) Nominal-T circuit



Student's Assignment

- Q.1** For a 500 Hz, frequency excitation, a 50 km long power line will be modelled as
 (a) short line (b) medium line
 (c) long line (d) data insufficient
- Q.2** An ACSR conductor has a diameter of 2 cm has internal inductance of 0.05 mH/km. If this ACSR is replaced with another having a diameter of 8 cm then it's internal inductance is
 (a) 0.2 mH/km (b) 0.05 mH/km
 (c) 1 mH/km (d) 0.025 mH/km
- Q.3** The surge impedance of a 50 km long underground cable is 50 ohm. For a 25 km length it will be
 (a) 25 ohm (b) 50 ohm
 (c) 100 ohm (d) none of the above
[UPPSC]
- Q.4** The radio interference in power line and communication lines are produced by
 (a) electromagnetic induction
 (b) electrostatic induction
 (c) both (a) and (b)
 (d) None of the above
- Q.5** Skin effect depends on
 (a) frequency
 (b) conductivity
 (c) relative permeability
 (d) all of the above
- Q.6** The main consideration for higher and higher voltage of transmission is to
 (a) increase the efficiency of transmission line
 (b) reduce power losses
 (c) increase power transmission capability
 (d) both (a) and (b) above
[UPPSC]
- Q.7** In EHV transmission lines, bundled conductors
 (a) increases inductance
 (b) decreases inductance
 (c) decreases capacitance
 (d) both (a) and (c)
- Q.8** Apart from the skin effect the non-uniformity of the current distribution is also caused by
 (a) ferranti effect
 (b) proximity effect
 (c) stroboscopic effect
 (d) any of the above
- Q.9** In an open ended line, the reflection coefficient of current is
 (a) 0 (b) 1
 (c) -1 (d) 2
[UPPSC]
- Q.10** What is the approximate value of the surge impedance loading of a 400 kV, 3 phase, 50 Hz overhead single circuit transmission line?
 (a) 230 MW (b) 400 MW
 (c) 1000 MW (d) 1600 MW
[UPPSC]
- Q.11** Increasing the length of transmission line will _____ the charging current.
 (a) increases (b) decreases
 (c) not effect (d) none of these
- Q.12** In triangular configuration, inductance and capacitance values with comparison to horizontal configuration are respectively
 (a) lesser and lesser
 (b) lesser and higher
 (c) higher and lesser
 (d) higher and higher
- Q.13** The self GMD of a conductor with three strands each of radius ' r ' and touching each other is
 (a) $r(0.7788 \times 2 \times 2)^{1/3}$
 (b) $r(0.7788 \times 2 \times 2 \times 2)$
 (c) $r(0.7788 \times 2 \times 2 \times 2)^3$
 (d) $r(0.7788 \times 2 \times 2)^3$
- Q.14** The time interval needed for a surge to travel to the end of a 450 km long overhead line is
 (a) 2 ms (b) 1.5 ms
 (c) 3 ms (d) 4.5 ms

Q.15 The $ABCD$ constants of 3 phase line are
 $A = D = 0.9 \angle 1^\circ$, $B = 185 \angle 82^\circ \Omega$,
 $C = 0.001 \angle 90.5^\circ \Omega^{-1}$. For the sending end
voltage of 400 kV, the magnitude of receiving
end voltage under no load condition is

- (a) 415 kV (b) 400 kV
(c) 444 kV (d) 765 kV

Q.16 SIL of a transmission line can be reduced by

- (a) reducing the resistance of line
(b) increasing the voltage level
(c) addition of lumped capacitance in series
(d) addition of lumped inductance in series.

Q.17 A 3-phase transmission line has its conductors
at the corners of an equilateral triangle with side
4 m. The diameter of each conductor is 1.72 cm.
The inductance of line per phase per km is

- (a) 1.278 mH (b) 1.178 mH
(c) 2.15 mH (d) 2.356 mH

Q.18 A loss less transmission line segment has
characteristic impedance $Z_0 = 100 \Omega$
electromagnetic wave propagation velocity in the
transmission line $v = 0.8$ times velocity of light
in vacuum. The frequency of the electromagnetic
wave transmitted is 100 MHz. The phase
constant is β and $\beta l = \pi$ rad, then what is the
length of the transmission line segment l ?

- (a) 24 m (b) $\frac{12\pi}{10}$ m
(c) $\frac{10\pi}{12}$ m (d) 1.2 m

Q.19 The propagation constant of a transmission line
is $0.15 \times 10^{-3} + j1.5 \times 10^{-3}$.

The wavelength of the travelling wave is

- (a) $\frac{1.5 \times 10^{-3}}{2\pi}$ m (b) $\frac{2\pi}{1.5 \times 10^{-3}}$ m
(c) $\frac{1.5 \times 10^{-3}}{\pi}$ m (d) $\frac{\pi}{1.5 \times 10^{-3}}$ m

Q.20 Which one of the following statement is correct?
Corona loss increases with

- (a) decrease in conductor size and increase in
supply frequency.
(b) increase in both conductor size and supply
frequency.

(c) decrease in both conductor size and supply
frequency.

(d) increase in conductor size and decrease in
supply frequency.

Q.21 The velocity of a travelling wave through a cable
of relative permittivity of 9 is

- (a) 9×10^8 m/sec (b) 3×10^8 m/sec
(c) 1×10^8 m/sec (d) 2×10^8 m/sec

[UPPSC]

ANSWER KEY

STUDENT'S ASSIGNMENT

- | | | | | |
|---------|---------|---------|---------|---------|
| 1. (c) | 2. (b) | 3. (b) | 4. (c) | 5. (d) |
| 6. (d) | 7. (b) | 8. (b) | 9. (c) | 10. (b) |
| 11. (a) | 12. (b) | 13. (a) | 14. (b) | 15. (c) |
| 16. (d) | 17. (a) | 18. (d) | 19. (b) | 20. (a) |
| 21. (c) | | | | |

HINTS & SOLUTIONS

STUDENT'S ASSIGNMENT

1. (c)

$$\therefore f \times l = 500 \times 50 = 25000 \text{ Hz km}$$

Clearly $fl > 12000 \text{ Hz km}$, hence the power line
will be modelled as long transmission line.

2. (b)

Internal inductance,

$$L_{\text{int}} = \frac{\mu}{8\pi} \text{ H/m}$$

where $\mu = \mu_0 \cdot \mu_r$

Thus $L_{\text{int}} \propto \mu_r$, where μ_r = relative permeability.

So, internal inductance is independent of size and
depends only on permeability of the medium.

$$\text{i.e., } L_{\text{int}2} = L_{\text{int}1} = 0.05 \text{ mH/km}$$

3. (b)

Surge impedance of T -line is independent of
length of the line. Hence for 25 km length, it will
be 50 ohm.

4. (c)

(i) **Electromagnetic induction:** Current flowing in
the power line produces magnetic flux linkage

with the communication line conductor or power line conductor induces an emf in nearby telecommunication line.

- (ii) **Electrostatic induction:** Due to earth effect electric field is produced by charges of earth induces voltage in between the conductors of lines.

Both effects causes interference to the telecommunication signals which is called radio interference.

5. (d)

- Skin effect is inversely proportional to skin depth.

- Skin effect $\propto \frac{1}{\sqrt{\pi f \mu \sigma}}$

where, f = frequency, $\mu = \mu_0 \cdot \mu_r$

μ_r = relative permeability, σ = conductivity.

7. (b)

With use of bundled conductors, self GMD/GMR is increased and hence inductance is reduced while capacitance increases.

$$\therefore L \propto \ln \left(\frac{\text{Mutual GMD}}{\text{Self GMD}} \right)$$

9. (c)

Reflection coefficient of current when receiving end is open circuited is $\rho_I = -1$.

10. (b)

Value of Z_s is 400Ω for single circuit overhead line.

$$\text{Hence, surge impedance loading (SIL)} = \frac{V_L^2}{Z_s}$$

$$\text{i.e., SIL} = \frac{(400 \times 10^3)^2}{400} = 400 \text{ MW}$$

11. (a)

Charging current,

$$I_c = \frac{V}{X_C}$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C_l l}$$

$$\text{i.e., } X_C \propto \frac{1}{l}$$

$$\text{So, } I_c = \omega C_l l V$$


12. (b)

$$\text{Inductance, } L = \frac{\mu_0}{\pi} \ln \left(\frac{d}{r'} \right) \text{ H/m}$$

$$\text{Capacitance, } C = \frac{\pi \epsilon_0}{\ln(d/r)} \text{ F/m}$$

In triangular configuration, distance between the conductors (d) is smaller than in horizontal configuration, hence inductance is less while capacitance is higher.

13. (a)

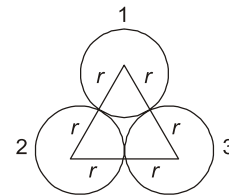

$$\text{Self GMD} = [(\text{Self GMD})_1 \times (\text{Self GMD})_2 \times (\text{Self GMD})_3]^{1/3}$$

$$\begin{aligned} \text{Now, } (\text{Self GMD})_1 &= (\text{Self GMD})_2 = (\text{Self GMD})_3 \\ &= (0.7788 r \times 2r \times 2r)^{1/3} \\ &= r (0.7788 \times 2 \times 2)^{1/3} \end{aligned}$$

$$\begin{aligned} \text{So, self GMD of given configuration} \\ &= \text{Self GMD of any one strand} \\ &= r (0.7788 \times 2 \times 2)^{1/3} \end{aligned}$$

14. (b)

$$\text{Time} = \frac{\text{Length}}{\text{Velocity}}$$

As speed of surge is the speed of light i.e., $3 \times 10^8 \text{ m/s}$

$$\begin{aligned} \text{Hence, } t &= \frac{450 \times 10^3}{3 \times 10^8} \\ &= 1.5 \times 10^{-3} \text{ s} = 1.5 \text{ ms} \end{aligned}$$

15. (c)

Under no load condition, $I_R = 0$

$$\therefore V_S = AV_R + BI_R$$

$$\text{Given, } V_S = 400 \text{ kV}$$

$$A = 0.9 \angle 1^\circ$$

$$V_R = ?$$

$$\Rightarrow V_S = AV_R$$